

(DEE 224)

B. Tech. DEGREE EXAMINATION, MAY - 2015

(Examination at the End of Second Year)

Electricals and Electronics Engineering

Paper - IV : NETWORK ANALYSIS - II

Time : 3 Hours

Maximum Marks : 75

Answer question No.1 compulsory

(15 × 1 = 15)

Answer any ONE question from each unit


(4 × 15 = 60)

- 1) a) Define path.
- b) Define Co-Tree.
- c) Write expressions for hybrid Parameters.
- d) Write expressions for Y Parameters.
- e) Write expression for transformed impedance of Capacitance 'C'.
- f) Draw waveform of pulse function.
- g) Define zero.
- h) Draw 'pie' network.
- i) Define mutual self inductance.
- j) Define Faraday's first law.
- k) Draw high pass filter.
- l) Draw constant K low pass filter.
- m) Write any two disadvantages of three phase system.

- n) Write expression for power using 2 – wattmeter method.
- o) Write the relation between line and phase quantities of 3 phase star system.


UNIT - I

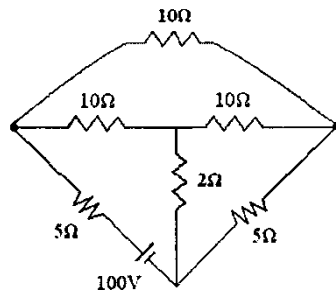- 2) a) Write the properties of tree with example.
- b) For the network shown in figure, write a tie set schedule.




OR

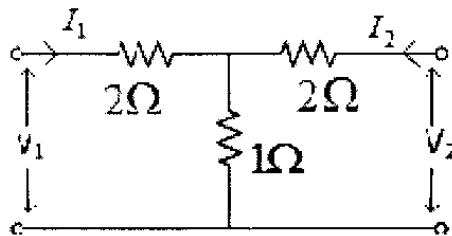- 3) a) State and derive the expression for ABCD parameters.
- b) Obtain Z parameters.



UNIT - II

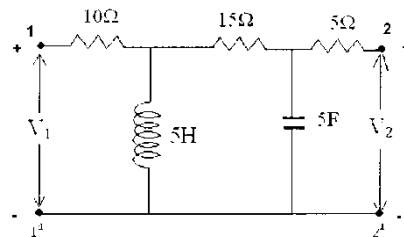- 4) a) Explain ABCD parameters in terms of transformed networks.
- b) Find ABCD parameters for the network shown in below.



OR

- 5) a) State and derive expressions for hybrid parameters in terms of transformed variables.
- b) State and derive expressions for Z parameters in terms of transformed variables.

UNIT - III

6) Clearly explain Low Pass Filter.

OR

- 7) a) Define coefficient of coupling. In which type of circuits it is minimum and in which type of circuits it is maximum?
- b) Two coupled coils with respect to self inductances $L_1 = 0.6\text{H}$, $L_2 = 0.4\text{H}$ having a $k = 0.4$. Coil 2 has 100 turns. The current in coil 1 is $i_1 = 10\sin 200t$ A. Determine the voltage at coil 2 and maximum flux set by coil 1.

UNIT - IV

- 8) a) Derive the relation between phase and line values of a 3-phase balanced delta connected system.
- b) Three impedances each of $(5 + j12)$ ohm are connected in star to a 220V, 3-phase, 50 Hz supply. Calculate the line currents.

OR

- 9) Two watt meters are used to measure the power input in a 3 phase circuit indicate 1000 W and 500 W respectively. Find the power factor of the circuit : when i) when both wattmeter readings are positive. ii) When the latter is obtained by reversing the current coil connections. Derive the expression for power factor.

