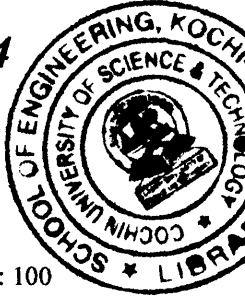




**B.Tech. Degree IV Semester Examination April 2014**

**EE 1404 CIRCUITS, SIGNALS AND SYSTEMS II**  
(2012 Scheme)



Time : 3 Hours


Maximum Marks : 100

**PART A**  
(Answer ALL questions)

(8 × 5 = 40)

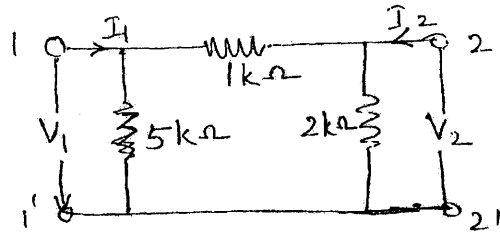- I. (a) Represent the following signals. (i)  $10u(4-t)$  (ii)  $u(t)-u(10-t)$   
 (b) Define static and dynamic systems with one example each and check whether the given system is static or dynamic.  

$$\frac{dy(t)}{dt} + 5y(t) = 2x(t).$$
  
 (c) Define  $h$  parameters and express it in terms of  $Z$  parameters.  
 (d) Calculate the  $Y$  parameters and draw the equivalent circuit.



- (e) Explain the classification of filters.  
 (f) Design a constant  $K$  high pass filter ( $\pi$ ) having cut off frequency 1kHz with terminal load resistance of  $600\Omega$ .  
 (g) Obtain the impulse response of the system  

$$y(n) = x(n) + 2x(n-1) - 4x(n-2) + x(n-3)$$
  
 (h) Obtain the initial and final value of  $X(z) = \frac{1}{1-z^{-2}}$ .

**PART B**


(4 × 15 = 60)

- II. (a) Represent the following signals. (7)  
 (i) Unit impulse (ii) Unit step  
 (iii) Unit ramp (iv) real exponential  
 (v) Complex exponential  
 How is the impulse function related to step and ramp?  
 (b) Define LTI system and verify whether the system is linear and time invariant (8)  

$$3\frac{dy(t)}{dt} + 5y(t) = x(t).$$


**OR**

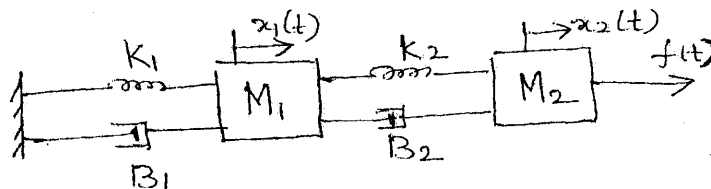- III. (a) What is meant by BIBO stable system. Determine the stability of (7)  
 (i)  $y(t) = e^{4t}u(t-3)$   
 (ii)  $y(t) = e^{-2t}\sin 2t u(t)$   
 (b) Write the differential equations for the system. (8)



(P.T.O.)

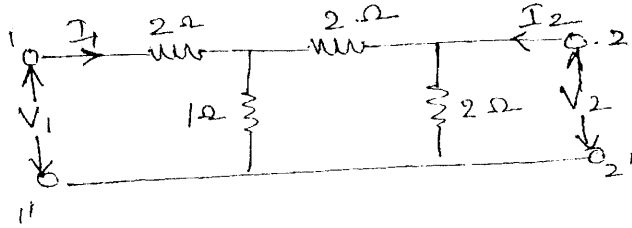
- IV. (a) Calculate the open circuit impedance parameters of the given network and draw the equivalent circuit. (9)



- (b) Define image impedance and obtain the formula for the characteristic impedance of a T Network. (6)

OR

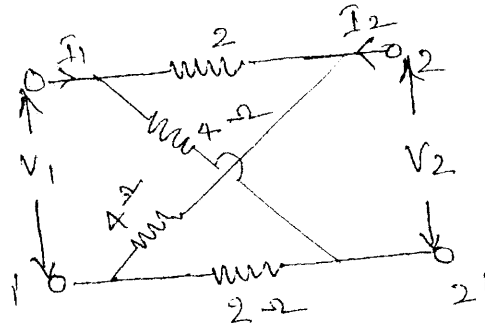- V. (a) Obtain the transmission parameters of the given network. (9)



- (b) Obtain the equivalent ABCD parameters when two networks are cascaded. (6)

- VI. (a) Explain how the band, attenuation constant and phase constant are affected when  $\frac{Z_1}{4Z_2}$  of a (6)

filter varies from  $-\infty$  to  $+\infty$  with (i)  $Z_1$  and  $Z_2$  are similar type and (ii)  $Z_1$  and  $Z_2$  are opposite type.

- (b) Design an  $m$  derived low pass filter ( $T$  and  $\pi$  section) having design resistance  $R_0 = 500\Omega$ , (9)  
cut off frequency  $f_c = 1500\text{Hz}$  and infinite attenuation frequency  $f_\infty = 2000\text{Hz}$ .

OR

- VII. (a) Discuss the properties of positive real functions. (6)  
(b) Determine the 1<sup>st</sup> Foster form of the driving point impedance (9)

$$Z(s) = \frac{5(s+1)(s+4)}{(s+3)(s+5)}$$

- VIII. (a) Explain sampling and aliasing. (6)  
(b) Obtain the  $z$  transform of (9)

(i)  $x(n) = [\sin \omega_0 n]u(n)$

(ii)  $x(n) = \{1, 2, -1, 2, 3\}$

(iii)  $x(n) = na^{n-1} \uparrow$

OR

- IX. (a) Explain the linearity, time reversal and convolution properties of  $z$  transform. (6)  
(b) Determine the inverse  $z$  transform of (9)

(i)  $X(z) = \frac{4}{z-5}$

(ii)  $X(z) = \frac{z-4}{(z-1)(z-2)^2}$

\*\*\*