

(3 Hours)

[Total Marks : 100

N.B. : Question No. 1 is compulsory. Solve any four from rest six.

1. Answer the following questions: Each question carries 5 marks. 20
- (a) Construct Hamming code for BCD 0111. Use even parity.
- (b) Construct an EX-OR gate using universal gates.
- (c) Draw the circuit of 2-input TTL NAND gate.
- (d) Explain with example self-complementing codes
2. (a) Simplify the following 4 variable Boolean expression using Quine-McCluskey method 10
 $F = \sum m(0,1,3,7,9,15) + d(8,11)$
- (b) For the expression $Y = (P + Q)(Q' + R')$
- i) Convert to standard POS 4
- ii) Reduce using K-map 4
- iii) Construct circuit using NOR gates only 2
3. (a) Implement the following expression using IC 74138, 3:8 active low decoder and additional gates 10
 $F(A,B,C,D) = \pi M(0,6,7,8,12,13,14,15)$
- (b) Find the reduced SOP form using K-map 5
 $F(A,B,C,D) = \sum M(0,6,7,8,12,13,14,15)$
 Implement using only NAND gates
- (c) Explain the term "noise margin" and its values for TTL and CMOS families. 5

4. (a) Design and explain 8 bit binary adder using IC 7483 10
- (b) Design an clocked MN flip-flop using JK flip-flop. The function table of MN flip-flop is as follows: 10
- | M | N | Q_{n+1} |
|---|---|-----------|
| 0 | 0 | Q_n' |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | Q_n |
5. (a) Explain and draw MOD – 10 asynchronous counter using T- FF. Draw output waveforms and show where glitches occur. 10
- (b) A parking lot has 4 parking slots. A car requires 1 empty slot, a tempo requires 2 empty adjacent parking slots and a truck requires 3 empty adjacent parking slots. Each slot has a sensor which indicates a '1' when slot is full and indicates a '0' when slot is empty. Generate 3 outputs: car, tempo and truck which indicate which vehicle should be allowed to park. 10
6. (a) Construct a ring counter using IC 74194 and draw the output waveforms. 10
- (b) Consider the expression $Y = AD' + BD$. Find out whether any hazard exists in the hardware implementation. If yes, eliminate the hazard. 10
7. (b) Draw and explain a 9 - bit even parity checker using IC 74180 10
- (a) Implement the function using single IC 74151 and some gates 10
- $F = \sum m(1,2,4,7,10,13,14)$
-