

BE | ETRX | VII (REV) 26/11/12  
 Filter Design

25 2nd half-12 (b) JIP

Con. 8390-12.


KR-1029

(3 Hours)

[ Total Marks : 100

- N.B.:** (1) Question No. **I** is **compulsory**.  
 (2) Attempt any **four** questions from remaining **six** questions.  
 (3) Assume **suitable** data wherever **necessary**.

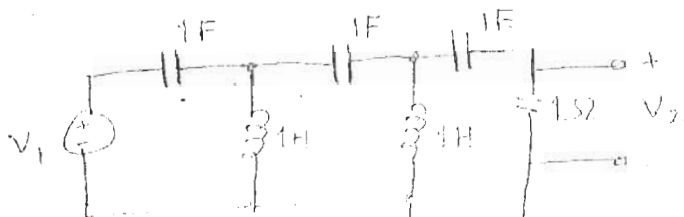1. (a) Give difference between Butterworth, Chebyshev and elliptic filters. 5  
 (b) Describe basic principles of working of switched capacitor filter with example. 5  
 (c) What is adaptive filter, explain with the help of suitable example. 5  
 (d) Explain multirate signal processing. Why antialiasing / antiimaging filter required? 5
  
2. (a) Design an analog bandpass filter for following specifications :— 15  
     (i) Passband 200 rad/s — 800 rad/s  
     (ii) Stopband 0 rad/s — 100 rad/s and  
         1600 rad/s — onwards  
     (iii) Passband attenuation 3dB  
     (iv) Stopband attenuation 10 dB  
     (v) Chebyshev filter.  
 (b) Explain basic Weiner filter. 5
  
3. Design a Butterworth, digital lowpass filter for following specifications. Plot pole-zero 20  
 plot also. Use bilinear transformation (BLT) method :  
     (i) Passband 0 – 1 KHz  
     (ii) Stopband 3 KHz – onwards  
     (iii) Passband attenuation 2.3 dB  
     (iv) Stopband attenuation 18 dB  
     (v) Sampling frequency 12 KHz  
     (vi) Low-pass filter  
     (vii) Plot pole-zero plot of analog filter only.
  
4. (a) What is inductance simulation, explain. 5  
 (b) Realize/synthesize following passive network using synthetic (simulated) inductor. 5




[ TURN OVER

Con. 8390-KR-1029-12.

2

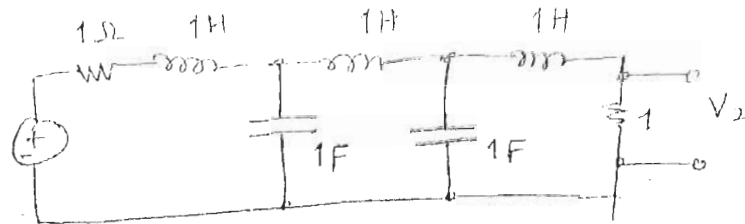- (c) Explain Leap frog realization technique with suitable example. 5
- (d) Realize following passive network using FDNR (frequency dependent negative resistor). 5



5. (a) Design a FIR filter for  $\delta_p = 0.01$ ,  $\delta_s = 0.1$ ,  $W_p = 0.2$ ,  $W_s = 0.6$  using any suitable window. 10
- (b) Design a frequency sampling filter for following specification  $|H(k)| = \{1, 1, 0, 0, 0, 1\}$ . 10
6. (a) For input sampling rate of 50 KHz and output sampling rate of 1 KHz, give 2-stage decimation scheme. Compare the filter order required for antialiasing filters of two stage implementation with single stage implementation. Comment on the results. 10
- (b) Explain with suitable example polyphase interpolation. comment/compare with single phase interpolation. 10
7. Write short notes on (a) and (b). Attempt any **three** :-
- (a) MMSE criterion in adaptive filter 6
- (b) LMS and RLS algorithm in adaptive filtering 7
- (c) Design an active lowpass, second order filter for  $W_n = 1$  KHz and  $Q = 0.707$ . 7
- (d) What is subband coding and quadrature mirror filtering, explain. 7