



Name :

Roll No. :

Invigilator's Signature :

CS/B.Tech(O)/SEM-1/EC-101/2012-13

2012

BASIC ELECTRONICS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following :

10 × 1 = 10

i) Barrier potential of Ge diode is

- a) 0.3V b) 0.7V
- c) 0.4V d) 0V.

ii) A differential amplifier has a differential gain of 20,000. CMRR=80dB. The common mode gain is given by

- a) 2 b) 1
- c) 0.5 d) 0.

iii) With both junction reverse biased the transistor operates in

- a) active region b) cut-off region
- c) saturation region d) inverted region.



- iv) If a register has the colour code (red-black-brown), the value of the register equals
 - a) 1000Ω
 - b) $10 \text{ k}\Omega$
 - c) 110Ω
 - d) 100Ω .
- v) The operating state that distinguishes an SCR from diode is
 - a) forward conduction state
 - b) forward blocking state
 - c) reverse conduction state
 - d) reverse blocking state.
- vi) When the gate to source voltage V_{GS} of n -channel JFET is made more negative, the drain current
 - a) increases
 - b) decreases
 - c) remains constant
 - d) may increase or decrease.
- vii) The closed loop-gain of an Op-Amp inverting amplifier is
 - a) always larger than unity
 - b) always equal to unity
 - c) always less than unity.
- viii) For an emitter-follower, the voltage gain is
 - a) unity
 - b) greater than unity
 - c) less than unity.



- ix) JFET is a
- a) current control device
 - b) voltage control device
 - c) temperature control device
 - d) none of these.
- x) Which one is used as a reference voltage source ?
- a) Junction diode
 - b) Zener diode
 - c) Transistor
 - d) Op-amp.
- xi) UJT is used as
- a) rectifier
 - b) voltage follower
 - c) relaxation oscillator
 - d) none of these.

GROUP – B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

2. What is the importance of forbidden energy gap in material science ? What are the forbidden energies of Si and Ge ?
3. How does the depletion layer width change with doping concentration of a $p-n$ junction diode ? Draw the ideal diode characteristic curve.
4. What is ripple factor ? Give an expression for the ripple factor.
5. What are effects of 'early effect' ? Define "punch through" in "early effect".



GROUP – C

(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

6. a) Explain the operation of a full-wave Bridge Rectifier with the help of circuit diagram. 10
b) Obtain a mathematical expression for the efficiency of a full-wave rectifier and show that its ripple factor is 0.482. 5
7. a) Discuss the two-transistor analogy of an SCR. 5
b) Explain the working principle of SCR. 7
c) Draw the forward and reverse characteristics. 3
8. a) For a rectifier circuit using diodes, define
(i) rectification frequency
(ii) ripple factor
(iii) PIV.
b) Each of two diodes in a full-wave rectifier circuit has a forward resistance of 50Ω . The DC voltage drop across a load resistance of 1.2Ω is 30 V. Find the primary to total secondary turns ratio of the centre-tapped transformer, primary being fed from $220 V_{rms}$. 9
9. Write short notes on any *three* of the following : 3×5
a) UJT
b) Clamping circuit
c) Barkhausen criterion
d) Advantages of negative feedback amplifier
e) Lissajous figures.