

Roll No .....

**EX-405 (Old)**

**B.E. IV Semester**

Examination, June 2016

**Electronic Devices and Circuits - II**

*Time : Three Hours*

*Maximum Marks : 70*

- Note:* i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.  
 ii) All parts of each question are to be attempted at one place.  
 iii) All questions carry equal marks, out of which part A and B (Max. 50 words) carry 2 marks, part C (Max. 100 words) carry 3 marks, part D (Max. 400 words) carry 7 marks.  
 iv) Except numericals, Derivation, Design and Drawing etc.

**Unit - I**

1. a) Write the characteristics of ideal and practical op-amp.
- b) Define slew rate and off-set voltage of op-amp.
- c) Describe logarithmic amplifier using op-amp.
- d) Explain frequency compensation techniques of operational amplifier.

OR

Find  $V_0$  for the adder-subtractor shown in figure 1.1.

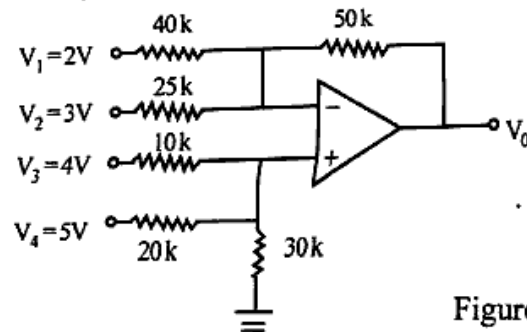


Figure 1.1

[2]

**Unit - II**

2. a) Draw frequency response of active LPF and HPF.
- b) Compare higher order and lower order filters.
- c) Explain 555 timer and its applications.
- d) Explain phase locked loop.

OR

Design a second order low pass filter at a high cut off frequency of 1 kHz.

**Unit - III**

3. a) Define Acoustics.
- b) Explain the working of moving coil microphone.
- c) Explain noise figure and sensitivity.
- d) Write a short note on sound recording systems.

OR

Explain cross over network and its frequency characteristics.

**Unit - IV**

4. a) State the limitations of conventional tubes.
- b) What is GUN effect?
- c) Discuss the high frequency limitations of transistors.
- d) Write the short notes on Klystron amplifier and magnetrons.

OR

Explain

- i) MASER and LASER
- ii) IMPATT and TRAPATT
- iii) TUNETT

**Unit - V**

5. a) Explain transistor as a switch.
- b) Compare ECL and TTL.
- c) What are the advantages of CMOS circuits?
- d) Explain TTL and its characteristics.

OR

Discuss the rise and fall time in CMOS gates.

\*\*\*\*\*