

**B.E. / B. TECH (PART TIME) REGULAR EXAMINATIONS APRIL / MAY 2014**  
**ANNA UNIVERSITY CHENNAI**  
**PTEC8101 CIRCUIT THEORY**  
**DEPT. OF ECE**  
**SEMESTER I, REGULATIONS 2013**

Time: 3 hours

Max Marks: 100

**ANSWER ALL QUESTIONS**

**PART-A**



**(10x2=20 marks)**

- For the current  $i = 3te^{-100t}$  mA and  $v = (0.006 - 0.6t)e^{-100t}$  V, determine the power absorbed by the circuit element at  $t = 5$  ms and energy delivered to the element in the interval  $0 < t < \infty$ .
- A 100 W light bulb, a 60 W light bulb and a 40 W light bulb are connected in parallel to each other and to a 230 V supply. Compute the current flowing through each light bulb and the total current delivered by the voltage supply.
- Three  $30 \Omega$  resistors are connected in a delta connection, determine the wye equivalent circuit.
- Define duality with an example.
- A voltage of  $8 \angle -50^\circ$  is applied to a 4H inductor. Determine the phasor current and time domain current.
- Find the average power and an expression for the instantaneous power that result when the corresponding phasor voltage  $V = 4 \angle 0^\circ$  V is applied across an impedance  $Z = 2 \angle 60^\circ \Omega$ .
- Determine the quality factor for resonant circuit containing components  $20 \Omega$ , 50 mH and  $10\mu\text{F}$  connected in parallel.
- Write the expression for half power frequencies of a series resonant circuit.
- Define the coefficient of coupling for the coupled circuit.
- Define cotree with an example.

**PART-B**

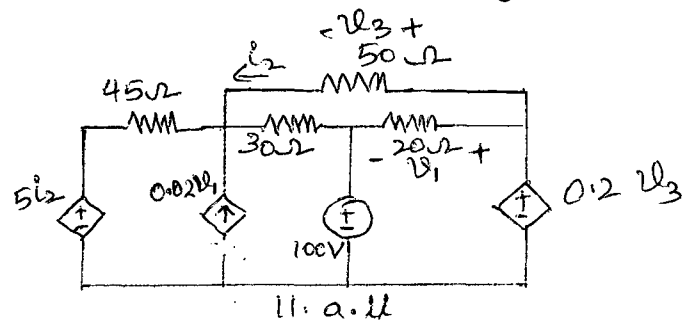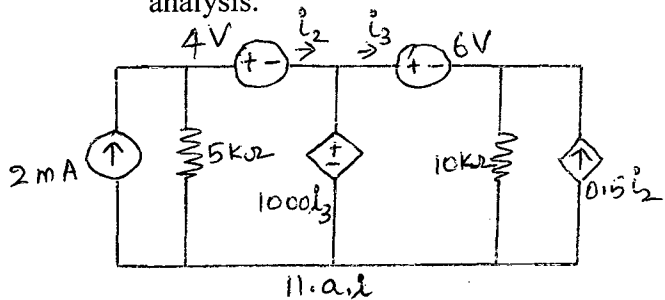**(5x16 = 80 marks)**



- 11 i). Determine the power generated by each of the sources in the circuit shown using mesh analysis.



- ii). Find  $v_1$  and  $i_2$  using nodal analysis in the circuit shown.



- 12a i). Find the voltage across the current source using superposition theorem.

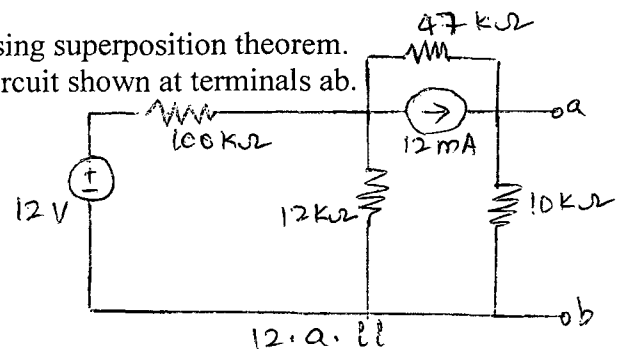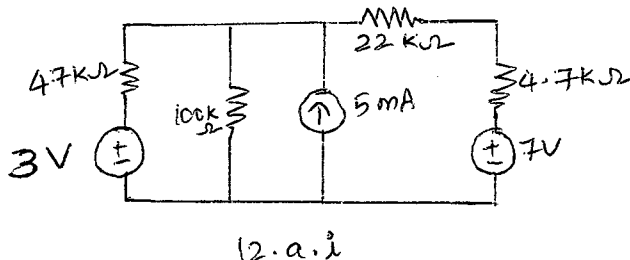- a ii). Determine the Thevenin equivalent of the circuit shown at terminals ab.




OR

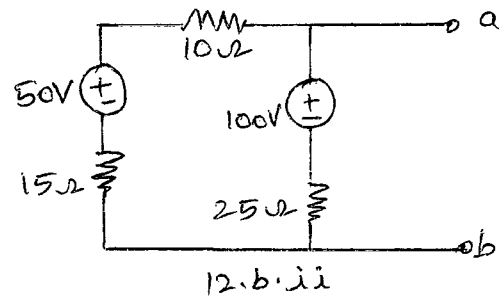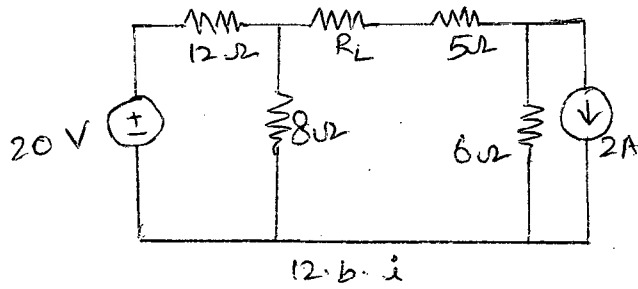12.b.(i) Determine the maximum power that could be dissipated in  $R_L$  in the circuit shown.




b.ii). Determine the power delivered to a  $50\ \Omega$  resistor connected to terminals a and b of the circuit shown.

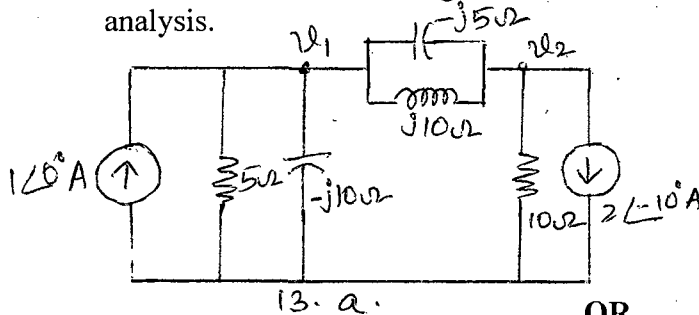13.a. Determine the nodal voltages in the circuit shown and verify the answer using mesh analysis.





OR

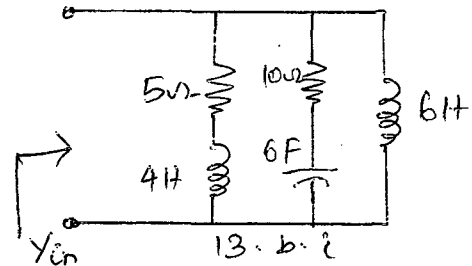


- b.i). Determine the input admittance for  $\omega = 60$  rad/seconds in the circuit shown.  
 ii). Determine the average power, reactive and complex power when a 60 V rms is applied to a load of  $1 + j5\ \Omega$ . Also, draw the power triangle.

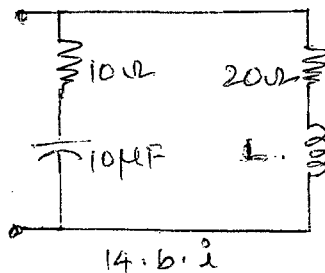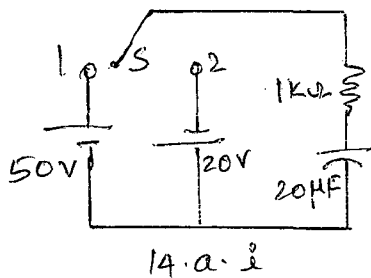14.a.(i) The switch is closed on position 1 at  $t = 0$  and after one time constant, it is moved to position 2 in the circuit shown. Determine the complete expression for the current.



OR

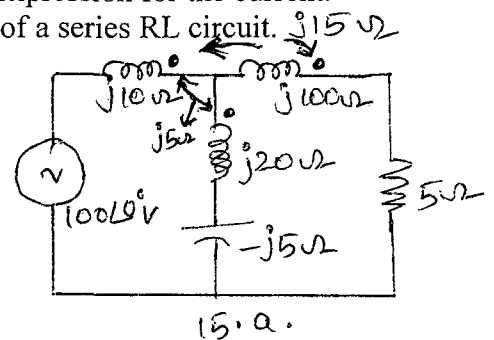

- b. (i) Determine the value of  $L$  for which the circuit shown is resonant at 200Hz..  
 (ii) A series RLC circuit with  $R = 3000$  ohms,  $L = 10$  H and  $C = 200\ \mu\text{F}$  has a constant voltage  $V = 50$  volts applied at  $t = 0$ . Find the current transient.

15a. Determine the voltage across the  $5\ \Omega$  for the coupled circuit shown.

OR

- b. Explain how incidence matrix is derived from a graph with suitable example and express the branch current in terms of loop current using tie-set matrix.