

USN

--	--	--	--	--	--	--	--	--	--



06ELN15/25

First/Second Semester B.E. Degree Examination, May/June 2010
Basic Electronics

Time: 3 hrs.

Max. Marks:100

- Note:** 1. Answer any FIVE full questions, choosing at least two questions from each part.
 2. Answer all objective type questions only on OMR sheet page 5 of the answer booklet.
 3. Answer to objective type questions on sheets other than OMR will not be valued.

PART – A

- 1 a. Choose the correct answer from the following :
- i) Semiconductor materials have _____ bonds.
 A) Covalent B) Mutual C) Metallic D) Ionic.
- ii) Junction breakdown occurs with
 A) Forward bias B) Reverse bias C) Active bias D) under high temperature.
- iii) In a silicon diode, reverse current is usually
 A) Zero B) Very large C) Very small D) In the breakdown region.
- iv) In a Zener diode
 A) Forward voltage rating is high
 B) Negative resistance characteristic exists
 C) Sharp breakdown occurs at low reverse voltage
 D) None of the above. (04 Marks)
- b. With diagram and waveform, explain the working principle of full wave rectifier. (08 Marks)
- c. A half wave rectifier is used to convert 230 V AC in to DC across a load of 1 k Ω . The transformer used is 230 V/12 volts. The DC resistance of the transformer used is 12 Ω and the resistance of the diode is 22 Ω . Compute :
- i) DC output voltage
 ii) The rms value of the output voltage
 iii) Ripple factor
 iv) Rectification efficiency. (08 Marks)
- 2 a. Choose the correct answer from the following :
- i) The DC – Loadline of a transistor circuit
 A) Is a curved line B) Has a–ve slope
 C) Does not contain Q point D) Gives graphical relation between I_C and I_B .
- ii) The correct relationship between α and β is.
 A) $\beta = \frac{\alpha}{1-\alpha}$ B) $\alpha = \frac{\beta}{1+\beta}$ C) $\alpha = \frac{\beta}{1-\beta}$ D) $1-\alpha = \frac{1}{1+\beta}$.
- iii) In the base region of p-n-p transistor, the main stream of current is
 A) Hole current B) Electron current C) Saturation current D) Breakdown current.
- iv) The transistor operating point is chosen along the
 A) X-axis B) Load line C) Resistance line D) Characteristic. (04 Marks)
- b. Draw the current components which flow in a transistor. Also derive the equation for I_C in terms of α_{dc} , I_{CBO} and I_B . (08 Marks)
- c. Draw the input and output characteristics of CE circuit. Explain active, saturation and cut off regions. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines or remaining blank pages.
 2. Any revealing identification, appeal to evaluator and /or equations written on eg, 42+8 = 50, will be treated as malpractice.

- 3 a. Choose the correct answer from the following :
- A transistor is a
 - Two terminal device
 - Reverse biased device
 - Three terminal device
 - Modulated device.
 - Biasing means
 - Heating the junction
 - Applying voltages
 - Discharging
 - Destroying.
 - Stability factor for a fixed bias circuit is
 - $1 + \alpha$
 - $1 - \alpha$
 - $1 + \beta$
 - $1 - \beta$.
 - The operating point must be ___ for proper operation of the transistor
 - High
 - Increasing
 - Stable
 - Decreasing.
- (04 Marks)
- b. Give the circuit for i) Collector to base bias ii) emitter current bias. Also compare basic bias circuits. (08 Marks)
- c. For the circuit shown in Fig. Q3(c) using Si transistor with $\beta = 50$, draw the d.c loadline and determine the operating point. (08 Marks)


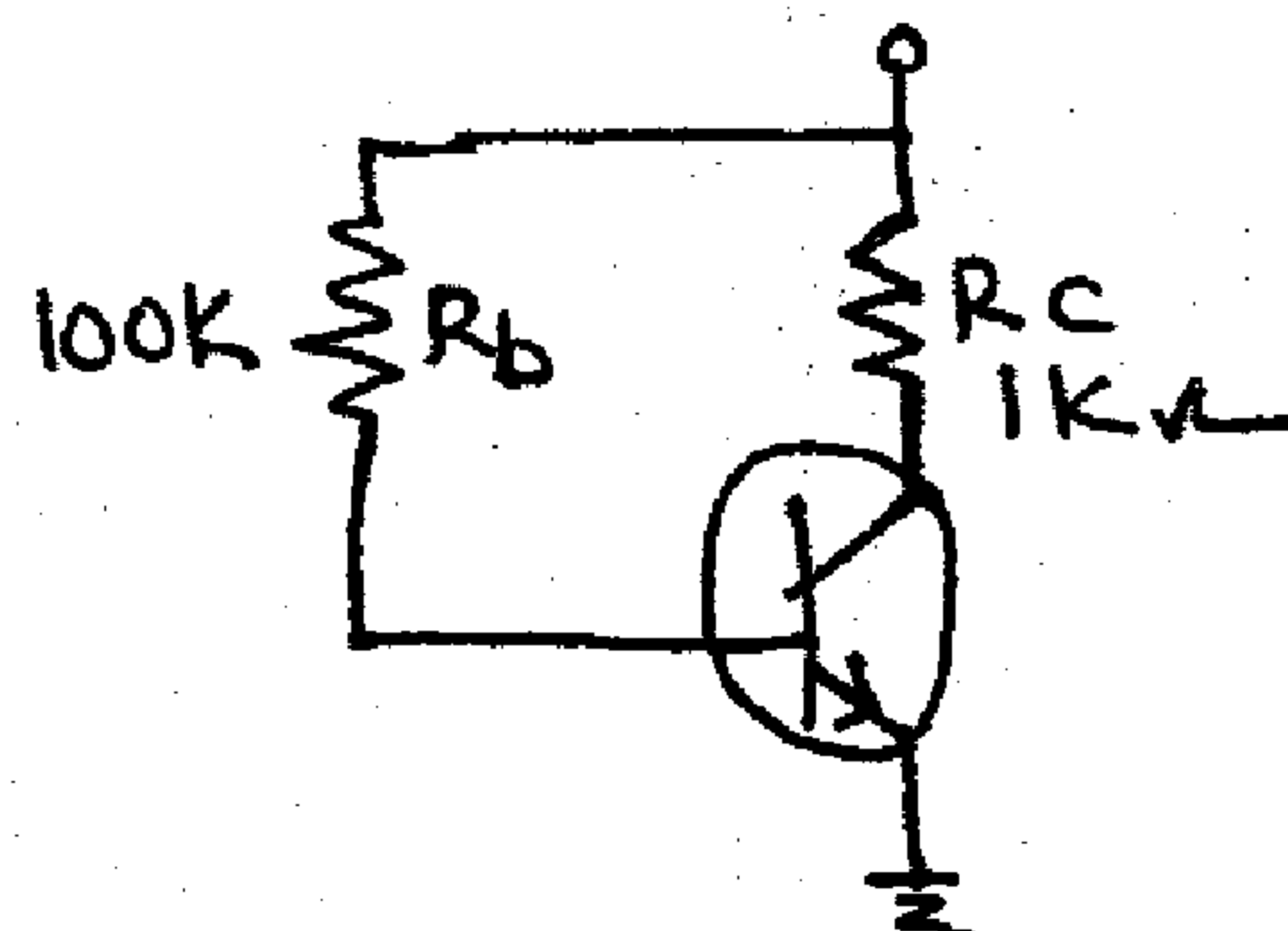


Fig. Q3(c)

- 4 a. Choose the correct answer from the following :
- The situation of drain current becoming just saturated is called
 - Forward bias
 - Saturation
 - Pinch off
 - Cutoff.
 - An SCR is a ___ device
 - Amplifying
 - Switching
 - Negative
 - Blocking.
 - The minimum point in VI characteristic of UJT is known as ___ point
 - Negative
 - Valley
 - Latching
 - Conducting.
 - The factor η of UJT is known as ___ ratio.
 - ON
 - Pulse
 - Negative
 - Intrinsic stand-off.
- (04 Marks)
- b. With the help of equivalent circuit and characteristics, explain the working principle of UJT. (08 Marks)
- c. Draw two transistor equivalent circuit of SCR. Also plot V-I characteristic and explain various regions of operation. (08 Marks)

PART - B

- 5 a. Choose the correct answer from the following :
- The criteria for producing Oscillations are known as ___ criteria.
 - Doppler
 - Bark housen
 - Miller
 - Band width.
 - A quartz crystal may be represented by an equivalent circuit consisting of a series ___ circuit.
 - RC
 - LC
 - RLC
 - RL.
 - The oscillating circuit is also called as
 - Differential
 - Tank
 - Logic
 - CRT.
 - Unit of gain in logarithmic scale is called
 - Watt
 - Joul
 - Bel
 - Decibel.
- (04 Marks)
- b. With circuit, explain the working of BJT RC phase shift oscillator. (08 Marks)
- c. With circuit, explain the working of two stage RC coupled amplifier and draw its frequency response. (08 Marks)

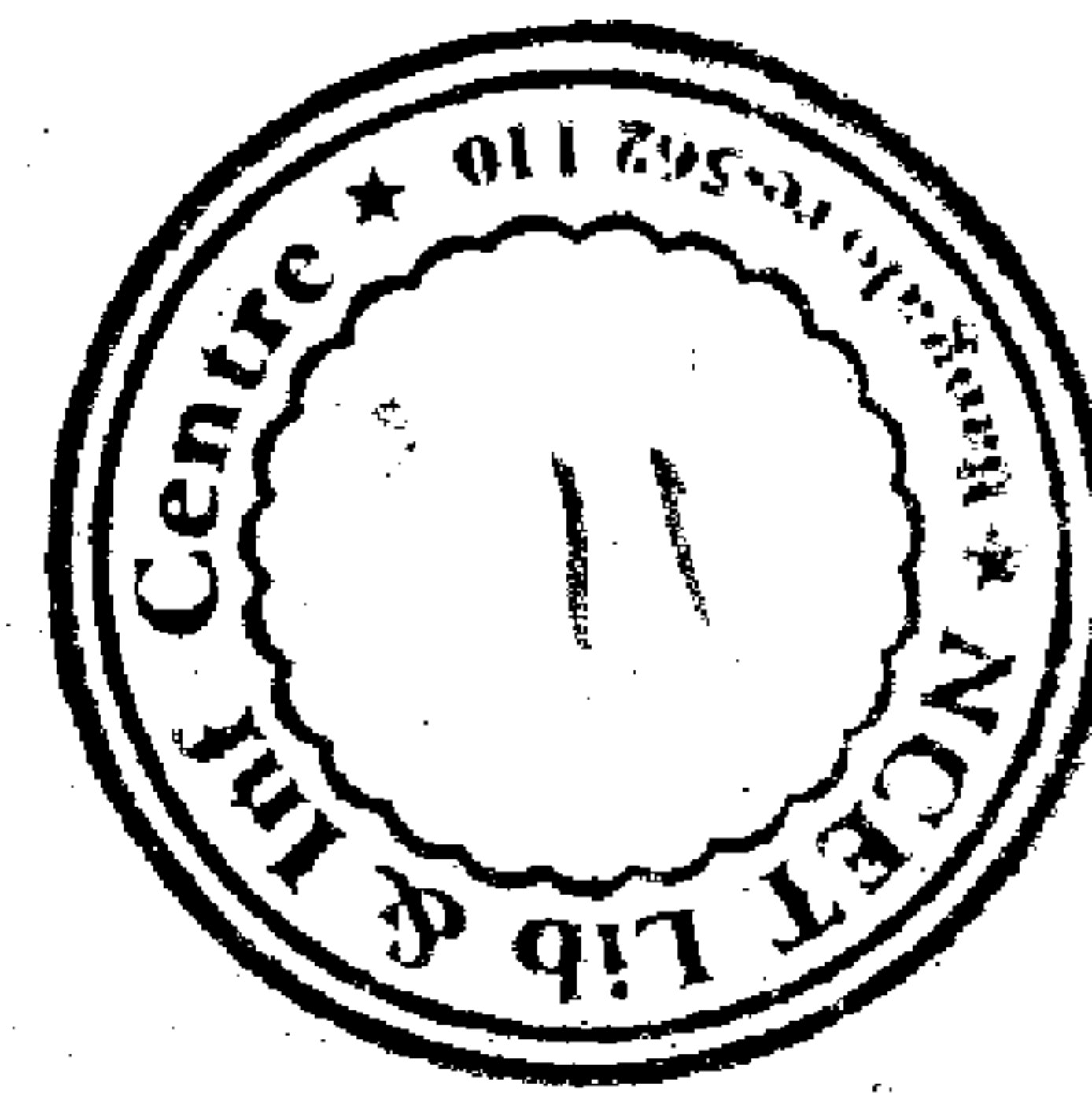

- 6 a. Choose the correct answer from the following :
- An inverting amplifier is one that produces _____ phase shift between its input and output voltage.
A) 45° B) 90° C) 360° D) 180° .
 - An op-amp shorted between inverting terminal and output terminal is called
A) Adder B) Integrator C) Voltage-follower D) inverter.
 - The op-amp can amplify
- A) AC signals only B) DC signals only C) both AC and DC signals D) None of these.
 - The op-amp integrator uses
A) Inductors B) Miller effect C) Sinusoidal inputs D) Hysteresis. (04 Marks)
- b. Draw the circuit, using op-amp, for
i) Integrator ii) Differentiator iii) Adder iv) Voltage follower. (08 Marks)
- c. With diagram, explain main parts of CRT. (08 Marks)
- 7 a. Choose the correct answer from the following :
- The 1's complement of 1010 gives
A) 1111 B) 0001 C) 0010 D) 1110.
 - The number 12 in octal is equivalent to decimal
A) 20 B) 12 C) 10 D) 4.
 - In binary numbers, shifting the binary point one place to the right
A) Divides by 2 B) decreases by 10 C) Increases by 10 D) Multiplies by 2.
 - To represent 35 in binary, number of bits required is
A) 6 B) 5 C) 4 D) 33. (04 Marks)
- b. Explain the need for modulation. (08 Marks)
- c. perform the following :
- $240_{10} = \underline{\hspace{2cm}}_2$
 - $0.2315_{10} = \underline{\hspace{2cm}}_2$
 - $3312_8 = \underline{\hspace{2cm}}_2$
 - $32198_{10} = \underline{\hspace{2cm}}_{BCD}$. (08 Marks)
- 8 a. Choose the correct answer from the following :
- The expression for half adder carry C with inputs A and B is given by
A) $A + B$ B) AB C) $\overline{A} \overline{B}$ D) None of these.
 - $A + AB =$
A) AB B) A C) B D) $1 + A$.
 - universal gates are _____ and _____
A) NOT and NOR B) AND and OR C) NAND and NOR D) EXOR and EXNOR.
 - $A + AB + A =$
A) AB B) $A + B$ C) A D) 0 . (04 Marks)
- b. i) Implement $Y=ABCD$ using two input NAND gates
ii) Simplify $Y = (A + B) (\overline{A} + C) (\overline{B} + C)$. (08 Marks)
- c. With a circuit, explain the working principle of parallel binary adder. (08 Marks)
