

--	--	--	--	--	--	--	--

A

B.Tech. Degree I & II Semester (Combined) Examination June 2014

**IT/CS/CE/SE/ME/EE/EB/EC/EI/FT 1107 BASIC ELECTRICAL AND
ELECTRONICS ENGINEERING
(2012 Scheme)**

Time : 3 Hours

Maximum Marks : 100

SECTION A – ELECTRICAL ENGINEERING

PART A

(Answer *ALL* questions)


(4 × 5 = 20)

- I (a) Explain (i) Circuit breakers (ii) GFCI (iii) Fuses
 (b) State and explain Kirchhoff's laws for an electric circuit.
 (c) Define RMS and average value of a waveform. What do you mean by form factor?
 (d) Distinguish between star and delta connection in three phase circuits.

PART B


(2 × 15 = 30)

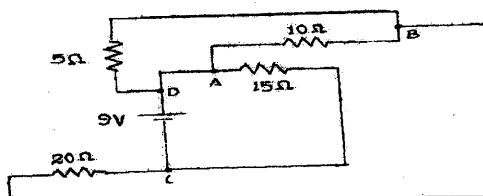- II. (a) Explain resistor color coding. (5)
 (b) Find the effective resistance and current through each resistance. (10)



OR

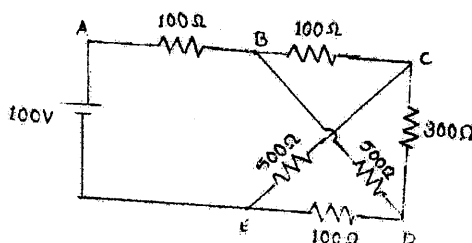- III. (a) Derive capacitance equation (5)
 (b) Determine the current supplied by the battery in the given circuit by using Kirchhoff's law. Also find out the current through 300Ω resistance. (10)



- IV. (a) With the aid of a Phasor diagram obtain the relationship between the line and phase values of voltage and current in a three phase star connected system. (7)
 (b) Two impedances $z_1 = 6 - j8$ ohms and $z_2 = 16 + j12$ ohms are connected in parallel. (8)
 If the total current of the combination is $(20 + j10)$ amperes, find the branch currents.

OR

- V. (a) Explain the working principle of an energy meter with a neat diagram. (6)
 (b) Write short notes on hydro electric power station. Explain with figure. (9)

(P.T.O.)

SECTION B – ELECTRONICS ENGINEERING

PART A (Answer *ALL* questions)

(4 x 5 = 20)

- VI. (a) What is the working principle of varactor diode? Give one application?
 (b) Explain the operation of transistor as a switch.
 (c) What is frequency modulation? Explain with relevant waveforms.
 (d) What is the concept of frequency reuse in mobile communication?

PART B

(2 x 15 = 30)

- VII. (a) Explain the working of a bridge rectifier with a neat circuit diagram. Also derive the equations for rms value of current and ripple factor. What PIV rating is required for diodes in a bridge rectifier that produces a peak o/p voltage of 50V? (10)
 (b) Explain the working principle of capacitor filter. (5)
- OR**
- VIII. (a) Explain how a zener diode can be used as voltage regulator. Define line regulation and load regulation. (6)
 (b) Draw the common emitter configuration of a transistor and explain its operation. Sketch i/p and o/p characteristics and show how dynamic resistance and current gain is calculated. (9)
- IX. (a) Explain the working principle of CRO with the help of block diagram. (10)
 (b) Give one example of a force sensor and explain its working. (5)
- OR**
- X. Explain satellite communication with the help of block diagram. (15)
