



M 25934

Reg. No. :

Name :

**Third Semester B.Tech. (Reg./Sup./Imp. – Including Part Time) Degree Examination, November 2014
(2007 Admn. Onwards)**

PT2K6/2K6EC/AEI 305 : NETWORK THEORY

Time : 3 Hours

Max. Marks : 100

Instructions : Answer all questions.
Assume missing data.

- I. a) Distinguish between a first order and second order system with the help of examples. 5
- b) Find the value of 'R' in the circuit such that maximum power transfer occurs. 5

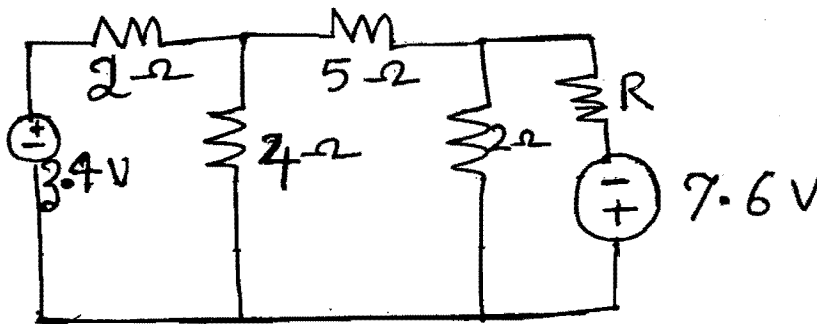


Fig. 1-b

- c) Give any 3 properties of driving point functions. 5
- d) $F(S) = \frac{(S+5)}{S^2 + 6S + 8}S$, find $f(t)$. 5
- e) Compare the features of M-derived and prototype filters. 5
- f) Draw the pole zero diagram for the network function $V(S) = \frac{S}{(S+1)(S+3)}$.
And also obtain $v(t)$. 5

P.T.O.



- g) Give any 3 properties of positive real functions. 5
 - h) Check whether the given polynomial is Hurwitz. Why? 5
- $H(S) = (S + 3)(S + 5 + 5j)(S + 5 - 5j)$ (8×5=40)

II. a) Determine the current I in the circuit given below using superposition theorem. 15

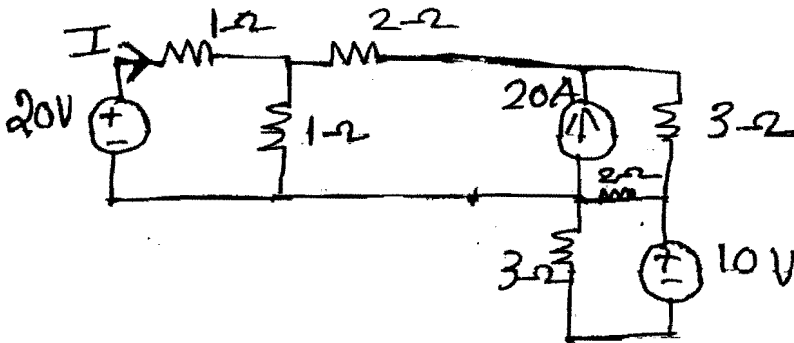


Fig. 2a

OR

b) Use Thevenin's theorem to find current through 10Ω resistor. 15

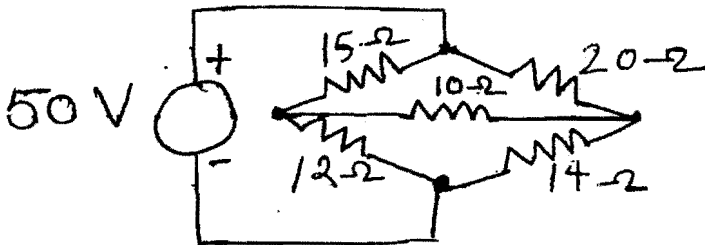


Fig. 2b

III. a) Find out the current i for $t \geq 0$, if $i(0) = 1$, for the given circuit. 15

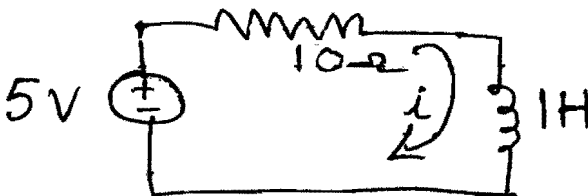


Fig. 3a

OR

b) Derive the expression for coefficient of coupling, for a pair of mutually coupled circuits. 15



IV. a) Find the hand Y-parameters for the network given below : 15

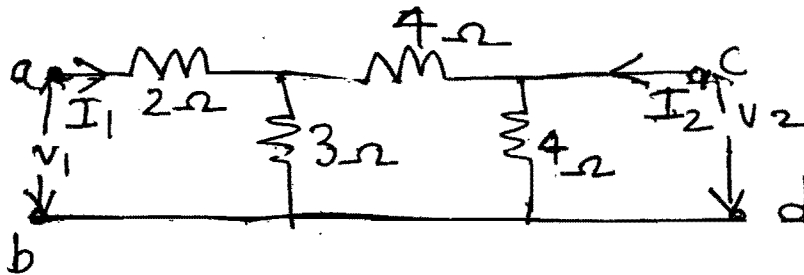


Fig. IV-a

OR

b) Design a M-derived LPF (I and II Section), having $R_o = 300\Omega$ $f_c = 2\text{KHz}$ and infinite attenuation frequency $f_\alpha = 3.5\text{KHz}$. 15

V. a) Find the first Caur form and second Foster form of the network with driving point admittance $Y(S) = \frac{3(S+2)(S+5)}{S(S+3)}$. 15

OR

b) Explain the significance of Hurwitz polynomial. What are its properties ? 15
