

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**B.E / B.Tech (Part Time) DEGREE END SEMESTER EXAMINATIONS, APRIL / MAY 2014**

Electronics and Communication Engineering

First Semester

**PTEC9152 Circuit Analysis / PTEC182 Circuit Analysis / PTEC142 Circuit Analysis**

(Regulation 2009, 2005 & 2002)

Time: 3 Hours

Answer ALL Questions

Max. Marks 100

**PART-A (10 x 2 = 20 Marks)**

1. Consider three resistors of  $500\ \Omega$ ,  $1000\ \Omega$  and  $2000\ \Omega$  are connected in series and the combination is powered by a 3V DC source. Then calculate the current and power derived from the source.
2. Complete the blanks in the following statements. The algebraic sum of voltages across the elements present in a closed loop is \_\_\_\_\_. It is called as \_\_\_\_\_.
3. Draw the dual of voltage source.
4. State superposition theorem with an example.
5. Draw the phasor diagram of a RL circuit.
6. Across a  $1\ \Omega$  resistor, a voltage source  $v(t) = 2 \sin(100\pi t)$  is connected. Then calculate the instantaneous power and average power delivered by the source.
7. Define time constant of RC network.
8. Draw the circuit of series RLC circuit and write equation used to compute the resonance frequency of the circuit.
9. What is ideal transformer? And what is its power efficiency?
10. What is tree in a network topology? And illustrate with an example.

**Part – B ( 5 x 16 = 80 marks)**

11. Consider the circuit shown in Figure Q.11. (i) Apply the mesh analysis to circuit to estimate the power dissipated by  $12\ \Omega$  resistor and (ii) verify the same using nodal analysis.

Roll No.

--	--	--	--	--	--	--	--	--	--

12. a) Use superposition on the circuit shown in Figure Q.12a to find the estimate the power dissipated by the  $30\Omega$  resistor.

(OR)

- b) In the circuit shown in Figure Q.12b, find the value of  $R_L$  to derive maximum power from the network. Also calculate the maximum power dissipated by  $R_L$ .

13. a) Find the Thevni's equivalent circuit for the circuit shown in Figure Q.13a. Calculate the voltage across load connected between 'a' and 'b' while the load is (i)  $100\Omega$ , (ii)  $j100\Omega$  and (iii)  $-j100\Omega$ .

(OR)

- b) Determine the average power supplied by the dependent source in the circuit shown in Figure Q.13b

14. a) After being open for a long time, the switch in the circuit of Figure Q.14a is closed at time  $t=0$ . For  $t>0$ , find  $v_c(t)$  and  $i_{sw}(t)$

(OR)

- b) Consider the circuit shown in the Figure Q.14b. (i) Plot the frequency behavior of  $|Z_{in}(\omega)|$ , (ii) derive the expression to estimate the resonance frequency and (iii) calculate the value of  $Z_{in}(\omega)$  at resonance frequency. (8 + 6 + 2)


15. a) Consider the circuit shown in Figure Q.15a. Find (i)  $I_L(j\omega)/V_s(j\omega)$ , (ii)  $i_L(t)$  while  $v_s(t) = 100 u(t)$ .

(OR)

- b) Find  $H(j\omega) = V_o(j\omega)/V_s(j\omega)$  for the circuit shown in Figure Q.15b

-----xxxx-----

Figures:

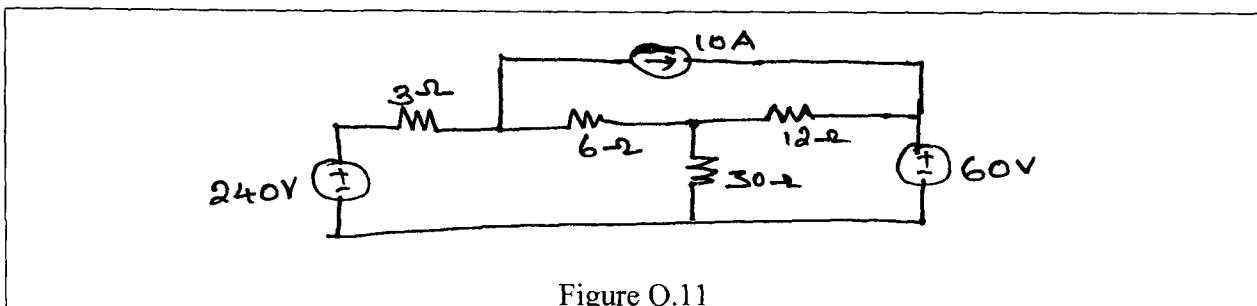

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

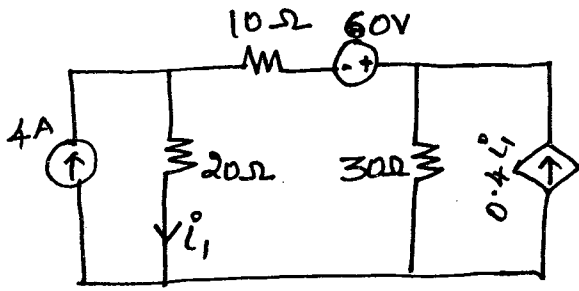


Figure Q.12a

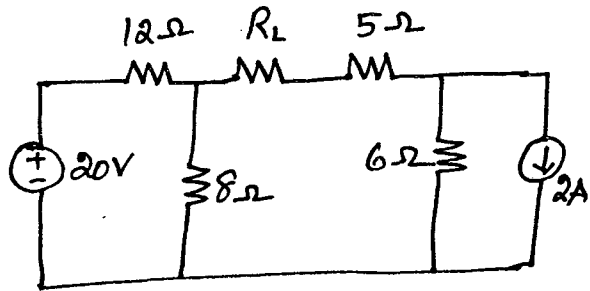


Figure Q.12b

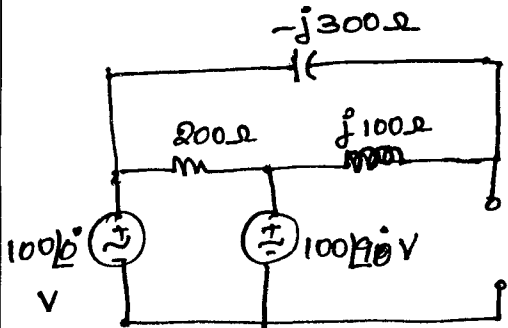


Figure Q.13a

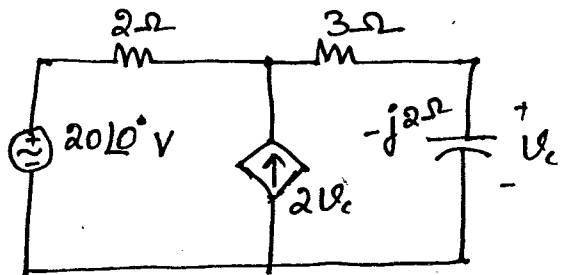


Figure Q.13b

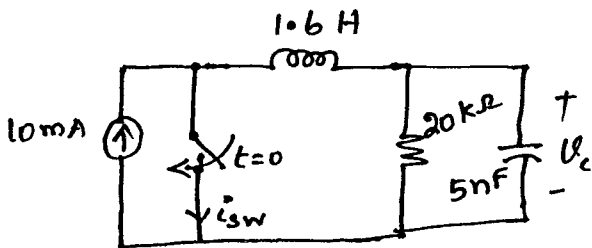


Figure Q.14a

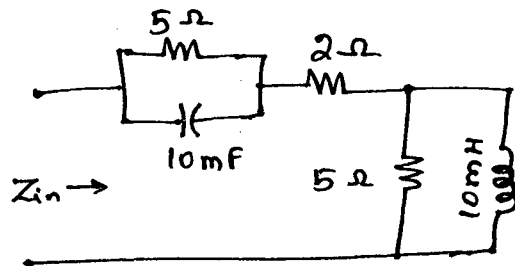


Figure Q.14b

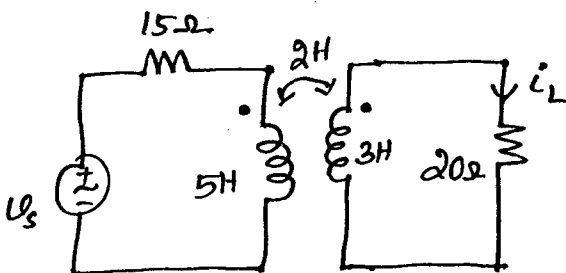


Figure Q.15a

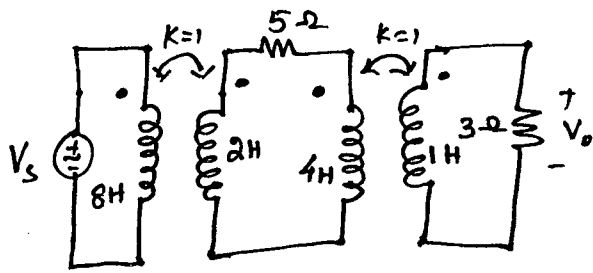


Figure Q.15b