

N.B. : (1) Question No. 1 is compulsory.

(2) Attempt any four questions from Question Nos. 2 to 7.

(3) Assume suitable data wherever necessary with proper justification.

(4) Figures to the right indicate full marks.

1. Attempt any four of the following :-

20

(a) Differentiate between direct coupled amplifier and R-C coupled amplifier.

(b) Differentiate between small signal amplifier and power amplifier.

(c) Explain why constant current source is used in differential amplifier.

(d) Give criterion of sustained sinewave oscillations and explain how oscillation starts and stabilizes in oscillator circuit.

(e) Give important features of CASCADE amplifier.

2. Design a two stage RC coupled amplifier for following specifications :-

20

$$A_v \approx 1000, \quad S_{i_{CO}} < 10, \quad R_i > 10 \text{ k} \Omega$$

$$V_{CC} = 12 \text{ V.d.c.}, \quad f_L < 20 \text{ Hz.}$$

Select transistor from the table given at the end of question paper.

3. (a) Explain how high frequency response of one stage RC coupled JFET CS type of amplifier can be determined. 10


(b) For the differential amplifier shown in figure, determine :-

(i) Q-points of transistors

5

(ii) differential voltage gain (A_d).

5

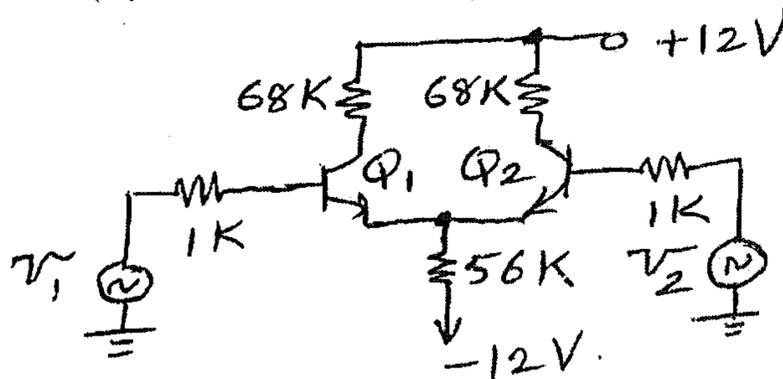

For transistors Q1 and Q2

$$h_{ie_1} = h_{ie_2} = 2 \text{ k} \Omega$$

$$h_{fe_1} = h_{fe_2} = \beta_1 = \beta_2 = 100$$

(neglect h_{oc} and h_{re})

4. (a) List different types of negative feedbacks, give their stability ratios, effect of feedback on input resistance and on output resistance. 10


[TURN OVER

Con. 6549-GS-7101-13.

2

(b) For the amplifier circuit shown in figure, determine –

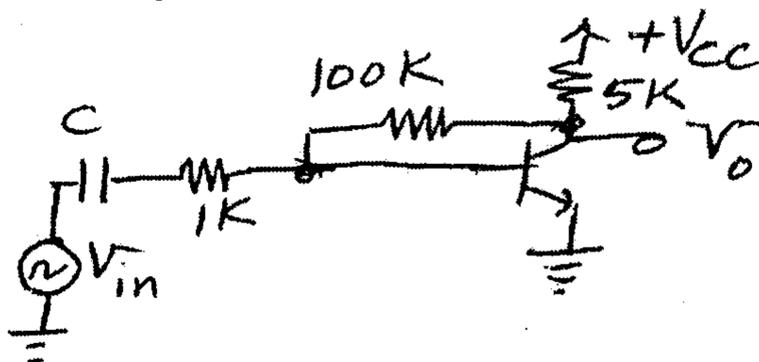- (i) Type of feedback
- (ii) Stability ratio
- (iii) A_{v_f} – voltage gain with feedback.



For transistor

$$h_{ie} = 1 \text{ k}\Omega$$

$$h_{fe} = 100$$

(Neglect h_{oe} and h_{re})

5. (a) Design a class A transformer coupled power amplifier to obtain 10 W average power to a load resistance of 10 ohm. $V_{cc} = 12$ V.d.c.
- (b) Draw the circuit diagram of Wien Bridge oscillator and explain its operation.
6. (a) Discuss problems encountered in multistage direct coupled amplifiers. Suggest methods to take care of these problems.
- (b) For power dissipation of 25 Watts design a heat sink if–

$$\theta_{j-c} = 1^\circ \text{C/W}, \theta_{c-HS} = 0.5^\circ \text{C/W},$$

$$T_{jmax} = 125^\circ \text{C} \text{ and } T_{ambient} = 30^\circ \text{C}.$$

7. Write short notes on any **three** of the following :–

- (a) Crossover distortion in class B amplifier and how to minimize the effect.
- (b) Class C amplifier and its application
- (c) Nyquist stability criterion
- (d) Hartley oscillator.

DATA SHEET

Transistor type	P _{dmax} @ 25°C Watts	I _{cmax} @ 25°C Amps	V _{CE} volts	V _{CE(sat)} volts	V _{BE} volts	T _{jmax} °C	D.C. current		Signal typ.	h _{FE} max.	V _{BE} max.	θ _{jc} °C/W	Derate above 25°C W/°C				
											min	typ.					
2N 3055	115.5	15.0	1.1	100	60	70	90	7	200	20	50	15	50	120	1.8	1.5	0.7
ECN 055	50.0	5.0	1.0	60	50	55	60	5	200	25	50	25	75	125	1.5	3.5	0.4
ECN 149	30.0	4.0	1.0	50	40	—	—	8	150	30	50	33	60	115	1.2	4.0	0.3
ECN 100	5.0	0.7	0.6	70	60	65	—	6	200	50	90	50	90	280	0.9	35	0.05
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	180	125	220	260	0.9	—	—
2N 525(PNP)	0.225	0.5	0.25	85	30	—	—	—	100	35	—	—	45	—	—	—	—
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	290	240	330	500	0.9	—	—

Transistor type	h _{ie}	h _{oe}	h _{re}	θ _{ja}
BC 147A	2.7 K Ω	18 μ Ω	1.5 × 10 ⁻⁴	0.4°C/mW
2N 525 (PNP)	1.4 K Ω	25 μ Ω	3.2 × 10 ⁻⁴	—
BC 147B	4.5 K Ω	30 μ Ω	2 × 10 ⁻⁴	0.4°C/mW
ECN 100	50 Ω	—	—	—
ECN 149	15 Ω	—	—	—
ECN 055	12 Ω	—	—	—
2N 3055	6 Ω	—	—	—

BFW 11—JFET MUTUAL CHARACTERISTICS

	-V _{GS} volts		I _{DS} max. mA		I _{DS} typ. mA		I _{DS} min. mA	
	0.0	10	7.0	4.0	4.0	3.0	2.2	1.6
g _{ms}	0.4	8.3	5.4	2.2	1.6	0.6	0.4	0.2
r _d	1.0	6.1	3.3	0.5	0.8	0.6	0.4	0.2
Derate above 25°C	1.2	4.2	2.7	0.0	1.7	0.6	0.4	0.2
	1.6	3.1	1.7	0.0	1.7	0.6	0.4	0.2
	2.0	2.2	0.8	0.0	0.8	0.6	0.4	0.2
	2.4	2.0	0.2	0.0	0.2	0.6	0.4	0.2
	2.5	2.0	0.0	0.0	0.0	0.6	0.4	0.2
	3.0	1.1	0.0	0.0	0.0	0.6	0.4	0.2
	3.5	0.5	0.0	0.0	0.0	0.6	0.4	0.2
	4.0	0.0	0.0	0.0	0.0	0.6	0.4	0.2

N-Channel JFET

Type	V _{DS} max. Volts	V _{GS} max. Volts	P _d max. @25°C	I _{DSS}	g _{ms} (typical)	r _d	Derate above 25°C	θ _{ja}
2N3822	50	50	300 mW	2 mA	3000 μ S	50 KΩ	2 mW/°C	0.59°C/mW
BFW 11 (typical)	30	30	300 mW	7 mA	5600 μ S	50 KΩ	—	0.59°C/mW