

- N.B. :** (1) Question No. 1 is **compulsory**.
(2) Attempt any **four** questions from remaining **six** questions.
(3) **Figures** to the **right** indicate **full** marks.
(4) Assume suitable **data**, if any.

1. Attempt the following :— 20
 - (a) With the help of block diagram, explain the operation of Online UPS system.
 - (b) Explain Dynamic braking for D. C. motor.
 - (c) What is time ratio control in D. C. choppers ? Explain the use of TRC for controlling the output voltage in choppers.
 - (d) State the need of reduction of harmonics in inverter output.

2. (a) With the help of neat circuit diagram and waveforms, explain the operation of isolated forward converter. 10
(b) Explain the effect of source inductance on the performance of a single phase fully controlled converter with neat diagrams and waveforms, indicating clearly the conduction of various thyristors during one cycle. 10

3. (a) Explain single pulse width modulation as used in PWM inverters. 10
(b) With the help of circuit diagram and associated waveforms, explain the principle of working of two quadrant (class C) chopper. 10

4. (a) State the various methods of speed control of Induction motor. Discuss the stator voltage control method. 10
(b) Describe the working of a single phase full converter fed D. C. separately excited motor with circuit diagram, relevant waveforms and expressions. 10

5. (a) Explain the slip power recovery control of three phase Induction motor. 10
(b) A load commutated chopper, fed from a 230 V d. c. source has a constant load current of 50 A. For a duty cycle of 0.4 and a chopping frequency of 2 kHz, calculate :— 10
- (i) the value of commutating capacitance.
 - (ii) average output voltage.
 - (iii) circuit turn-off time for one SCR pair.
 - (iv) total commutation interval.
6. (a) Explain with diagram, the operation of series inverter. State its limitations. How these limitations are overcome? 10
(b) The speed of a separately excited D. C. motor is controlled by a semiconverter. The field current which is also controlled by a semiconverter is set to the maximum possible value. The A. C. input voltage is single phase, 208 V, 50 Hz. The armature resistance $R_a = 0.25 \Omega$, $R_f = 147 \Omega$ and the motor voltage constant $K_v = 0.7032 \text{ V/A} - \text{rad/sec}$. The load torque is $T_L = 45 \text{ Nm}$ at 1000 rpm. Assume armature current to be continuous and ripple free, calculate :— (i) the field current I_f (ii) the delay angle of converter in armature circuit (α_a) 10
7. Write short notes on the following :— 20
- (a) Parallel Inverter
 - (b) Dual Converter
 - (c) V/f control for Induction Motor.
-