



Name :
Roll No. :
Invigilator's Signature :

CS/B.TECH/ECE(OLD)/SEM-4/EC-402/2013

2013

DIGITAL ELECTRONIC CIRCUITS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following :

10 × 1 = 10

- i) Gray code is called
 - a) reflected code
 - b) non-weighted code
 - c) unit distance code
 - d) all of these.

- ii) The number of select lines in a 16 : 1 multiplexer is
 - a) 4
 - b) 3
 - c) 2
 - d) 1.



iii) $(1AF)_{16} =$

- a) $(567)_8$ b) $(576)_8$
c) $(657)_8$ d) $(557)_8$.

iv) The complement of exclusive OR function is

- a) $AB + A'B$ b) $AB + A'B'$
c) $A'B + A$ d) $AB + AB'$.

v) $A + B'C =$

- a) $\sum m(0,2,3)$ b) $\Pi M(1,4,5,6,7)$
c) $\sum m(1,4,5,6,7)$ d) $\Pi M(1,2,5,6,7)$.

vi) A 4 bit ripple counter uses flip-flop with propagation delay of 50 ns each. The maximum clock frequency which can be used is

- a) 5 MHz b) 10 MHz
c) 20 MHz d) 25 MHz.



vii) In a sequential circuit the output at any instant depends on

- a) present inputs only
- b) past inputs only
- c) past outputs only
- d) present input and past output.

viii) A 10 bit D/A converter gives a maximum output of 10.23 V. The resolution is

- a) 10 mV
- b) 20 mV
- c) 15 mV
- d) 25 mV.

ix) TTL stands for

- a) Transistor Transistor Logic
- b) Transistor Transformer Logic
- c) Transistor Transfer Logic
- d) none of these.



x) For the gate given below the output will be



- a) 0
 - b) 1
 - c) A
 - d) A'.
- xi) In JK flip-flop, the input $J = K = 1$ pulse is as out
- a) set
 - b) reset
 - c) no change
 - d) toggle.
- xii) Which one of the following can be used as parallel to series converter ?
- a) Decoder
 - b) Digital counter
 - c) Multiplexer
 - d) Demultiplexer.

GROUP - B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

2. Design a full adder circuit using two half adder circuits (with truth table).
3. Design a 16 : 1 MUX using 4 : 1 MUX.
4. Design a two-bit comparator circuit by using minimum number of gates.



5. Draw and explain successive approximation type A/D converter.
6. What is race around condition ? How can you eliminate this problem ? Explain with proper diagram. 1 + 4

GROUP – C


(Long Answer Type Questions)

Answer any *three* of the following. 3 × 15 = 45

7. a) Design the following circuits using universal gates (NAND and NOR) :
- i) AND
 - ii) OR
 - iii) X-OR.
- b) Simplify the following using *K*-map :
- i) $F(A, B, C, D) = \sum m(1, 3, 5, 8, 9, 11, 15) + d(2, 13)$
 - ii) $F(A, B, C, D) = \prod M(1, 2, 3, 8, 9, 10, 11, 14) . d(7, 15)$
- c) Distinguish between the combinational circuit and sequential circuits. 3 + 10 + 2

 8. a) Design the following using suitable MUX :

$$F(A, B, C, D) = \sum m(1, 3, 4, 11, 12, 13, 14, 15)$$



- b) Minimize the following function by using Quine McCluskey method :

$$F(A,B,C,D) = \sum m(1,3,7,11,15) + d(0,2,5)$$

- c) Design a full adder circuit using decoder and necessary gates. 4 + 8 + 3

9. a) Make the FF conversions :

i) JK to T

ii) D to SR .

- b) Design a MOD-6 up counter using JK flip-flops.


$$(2 \times 3) + 9$$

10. a) Implement the following two Boolean functions with a PLA :

$$F_1 = \sum m(0,1,2,4)$$

$$F_2 = \sum m(0,5,6,7)$$

 - b) Design the sequence generator using T flip-flops.





11. a) Define the following terms :

- i) Propagation delay
- ii) Threshold voltage
- iii) Fan in
- iv) Fan out
- v) Speed of response.

b) Design and explain the operation of totem-pole output.

c) Design the universal gates using CMOS only. 5 + 5 + 5

12. Write short notes on any *three* of the following : 3 × 5

- a) Priority Encoder
- b) Successive Approximation type ADC
- c) Parity generator and checker
- d) Universal Shift Register
- e) BCD to 7-segment display.

=====