

--	--	--	--	--	--	--	--

## ***B.Tech. Degree V Semester Special Supplementary Examination August 2015***

### **EE 1505 LINEAR INTEGRATED CIRCUITS (2012 Scheme)**

Time : 3 Hours

Maximum Marks : 100

#### **PART A (Answer *ALL* questions)**

(8 × 5 = 40)

- I. (a) Explain the concept of virtual ground.
- (b) Compare open loop inverting and non-inverting amplifier.
- (c) Draw and explain the operation of voltage to current converter.
- (d) Define (i) CMRR (ii) Slew Rate
- (e) Draw and explain op-amp integrator circuit.
- (f) Draw and explain the working of a triangular wave generator.
- (g) Explain PLL.
- (h) Compare active and passive filters.

#### **PART B**

(4 × 15 = 60)

- II. Derive the expression for voltage gain, input impedance and output impedance of a dual input balanced output differential amplifier. (15)
- OR**
- III. Draw the block diagram representation of an op-amp and explain the function of each block. (15)
- IV. (a) Draw and explain the operation of an ac voltage follower. (5)
- (b) Derive the expression for voltage gain and input impedance of an inverting feedback amplifier with a neat circuit diagram. (10)
- OR**
- V. Draw the circuit diagram of an instrumentation amplifier with three op-amps. Derive expression for its voltage gain. (15)
- VI. (a) Explain the working of precision full wave rectifier with a neat circuit diagram. (10)
- (b) Explain sample and hold circuit. (5)
- OR**
- VII. (a) Draw and explain the working of an op-amp astable multivibrator. (6)
- (b) Draw and explain the circuit of Wien bridge oscillator. Derive expression for the frequency of oscillations. (9)
- VIII. (a) Draw and explain the working of successive approximation type ADC. (8)
- (b) Draw and explain the functional block diagram of 555 timer. (7)
- OR**
- IX. (a) Draw and explain the working of all pass filter. (7)
- (b) Explain the working of DAC with R-2R resistors and compare with binary weighted type resistor DAC. (8)