

EX-8402(NGS)
B.E. VIII Semester Examination, June 2014
Digital Electronics and Logic Design - II (Elective-IV)
Time : Three Hours

Maximum Marks : 70

Note: Attempt any two part in each unit. Each unit contains equal marks.

UNIT-I

1. a) Determine the number of flip-flop required to design a sequence generator to generate 1101110.
- b) Construct a mealy state diagram that will detect a serial input sequence of 10110.
- c) Explain mealy and moore machines with the help of example.

UNIT-II

2. a) Design an iterative array which gives output 1 when ci '0' after 3 consecutive 1's is received.
- b) Describe three types of modeling in VHDL.
- c) Write the VHDL code for the following function $f(x, y, z, w) = w + z(x'y + xy') + z'xw$.

UNIT-III

3. a) Boolean expression for the circuit is given by following equation

$$y_1 = x_1x_2 + x_1y_2' + x_2'y_1$$

$$y_2 = x_2 + x_1y_1'y_2 + x_1y_1'$$

$$z = x_2 + y_1$$

Where y_1, y_2 are internal states and z is output find flow table for circuit.

- b) What do you mean by hazards? Explain method of removal of hazards in sequential circuit design.
- c) Differentiate between synchronous and asynchronous sequential machines.

UNIT-IV

4. a) What is ASM chart compare ASM chart with state diagram? Explain with suitable example.
- b) Design a vending machine controller, machine accept the coin of Rs. 1,2,5,10 and gives a milk bottle of 10Rs. and return the extra money in the form of 1Rs. coin.
- c) Derive ASM chart for '0101' sequence detector.

UNIT-V

5. a) Implement the following functions by PROM
 - i) $f_1 = \sum m(1, 4, 6)$
 - ii) $f_2 = \sum m(2, 3, 4, 6)$
 - iii) $f_3 = \sum m(0, 3, 7)$
- b) Implement BCD to excess - 3 code converter by using PAL.
- c) Explain the following
 - i) Xilinx.
 - ii) Hard array logic.
 - iii) FPGA.
