

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 07

BCA (2011 & Onward) (Sem.-3)
DIGITAL CIRCUITS AND LOGIC DESIGN
Subject Code : BSBC-303
Paper ID : [B0230]

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTION TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains SIX questions carrying TEN marks each and a student has to attempt any FOUR questions.

SECTION - A

1) Write briefly :

- a) What is Race condition?
- b) Why universal Gate is called so?
- c) What is Sequential circuit?
- d) What is the use of complements?
- e) What are Registers?
- f) What is meant by Parity Bit?
- g) What is XNOR gate?
- h) Define Binary logic.
- i) What are Decoders?
- j) How to Convert Octal number to binary number? Give example.

SECTION - B

- 2) What are Logic gates? Explain its types with diagram and applications.
- 3) What are K-Maps? Explain how an expression can be solved using K-Maps with suitable example.
- 4) Explain Multiplexer and De-Multiplexer with diagram.
- 5) What are uses of Asynchronous counters? Explain the working of asynchronous counter by giving any counter of your choice.
- 6) Explain the following :
 - a) SOP form
 - b) Binary Adder
- 7) What is Boolean Algebra? Write basic identities of Boolean Algebra. Explain the role of DeMorgan's theorem in Boolean Algebra.