

--	--	--	--	--	--	--	--

B. Tech. Degree V Semester Examination November 2014

EE 1505 LINEAR INTEGRATED CIRCUITS

(2012 Scheme)

Time: 3 Hours

Maximum Marks: 100

PART A (Answer ALL questions)

(8 x 5 = 40)

- I. (a) What are the characteristics of an ideal op-amp?
 (b) Determine the output voltage of a DA for the input voltages of $300\mu V$ and $240\mu V$. The gain of the amplifier is 5000 and the value of the CMRR is (i) 100 and (ii) 10^5 .
 (c) Define slew rate. For an op-amp with slew rate of $0.5V/\mu s$, what is the maximum frequency to get an undistorted sine wave output of 10V peak?
 (d) Draw and explain a current mirror circuit.
 (e) Sketch the circuit diagram of a precision full wave rectifier and compare it with normal rectifier and applications of precision rectifiers.
 (f) Compare comparator and Schmitt trigger.
 (g) Explain the application of PLL as a frequency multiplier.
 (h) Compare active and passive filters.

PART B

(4 x 15 = 60)

- II. Derive the expression for voltage gain, input impedance and output impedance of dual input balanced output differential amplifier with neat diagrams. (15)

OR

- III. (a) Explain in detail, the internal block schematic of op-amp. (10)
 (b) Explain frequency response compensation in op-amp. (5)

- IV. Draw the circuit and derive the expression for overall gain of an instrumentation amplifier with three op-amps. What are its applications? (15)

OR

- V. (a) Derive the expression for voltage gain of a non inverting feedback amplifier, along with a neat circuit diagram. (10)
 (b) Draw and explain an I/V converter. What are its applications? (5)

- VI. (a) Sketch the circuit diagram of an astable multivibrator using op-amp and explain its operation. Derive the expression for frequency of oscillation. (10)
 (b) Explain the internal block diagram of IC 723 with a neat diagram. (5)

OR

- VII. Explain the working of a Wien bridge oscillator using op-amp. Derive the expression for frequency of oscillation. (15)

- VIII. (a) Draw and explain the functional block diagram of 555 timer. (7)
 (b) Draw and explain binary weighted resistor type DAC. (8)

OR

- IX. (a) Design second order Butterworth low pass filter at a high cut-off frequency of 1KHz. (10)
 (b) Explain all pass filter. (5)

