

Roll No

EE-504**B.E. V Semester**

Examination, June 2016

Digital Electronics and Logic Design**Time : Three Hours****Maximum Marks : 70**

Note: i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.

ii) All parts of each questions are to be attempted at one place.

iii) All questions carry equal marks, out of which part A and B (Max.50 words) carry 2 marks, part C (Max.100 words) carry 3 marks, part D (Max.400 words) carry 7 marks.

iv) Except numericals, Derivation, Design and Drawing etc.

1. a) Convert FFF in Hex to binary octal and decimal numbers.
- b) Determine the decimal representation of a negative integer whose 8-bit two's complement code is 10010110.
- c) Where do we use ASCII, Excess-3 and Grey codes?
- d) Perform the following operations:
 - i) Subtract using 9's and 10's complement 34-14
 - ii) Decimal number 102.5 to BCD and binary form.

OR

Hamming codes are a family of (n, k) block error-correcting code. Compute the hamming code for the given data bits 01101001.

2. a) Prove that $AB + A'C + BC = AB + A'C$
- b) Mention the important characteristics of digital IC's?
- c) Draw the logic circuit for the expression $F = x'y'z + x'yz + xy'$.

[2]

- d) Implement the expression $Y(A, B, C) = \Pi M(0, 2, 4, 5, 6)$ using only NOR-NOR logic.

OR

Draw and discuss the circuit of open collector TTT Not gate.

3. a) What is programmable logic array? How it differs from ROM?
- b) Convert the given expression in canonical SOP form $Y = AC + AB + BC$.
- c) Differentiate between the roles of MUX and DEMUX.
- d) Design an 8421 to gray code converter.

OR

Simplify the following Boolean functions by using K'Map in SOP and F (w, x, y, z) = m (1, 3, 4, 6, 9, 11, 12, 14)

4. a) Define race around condition.
- b) The t_{pd} for each flip-flop is 50ns. Determine the maximum operating frequency for MOD - 32 ripple counter.
- c) What is universal shift register?
- d) Realize D and T flip flops using Jk flip flops.

OR

Design a counter with the following repeated binary sequence : 0, 1, 2, 3, 4, 5, 6. use JK Flip-flop.

5. a) Define address and word.
- b) List the various types of A/D converters.
- c) What is meant by memory expansion? Mention its limit.
- d) Draw the circuit of a static MOS RAM cell and explain its operations of Read and Write.

OR

Draw the circuit of R-2R, 4 Bit D/A converter and discuss its conversion process.