

d) Obtain the Fourier expansion of the given waveform.

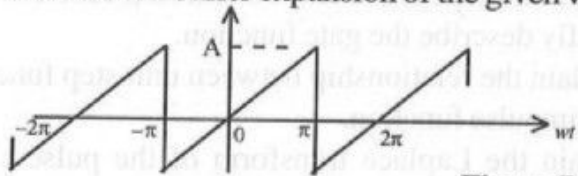


Figure 7

OR

Find the line spectrum of the following waveform using Fourier analysis.

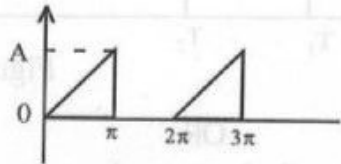


Figure 8

5. a) Write short note on network functions.
- b) How to determine the Y-parameters from two ports network.
- c) What's the relationship between Z and Y parameters. Convert the Z parameter to Y parameter.
- d) The h parameters of a certain two part network are $h_{11} = 1\Omega$, $h_{12} = 2$, $h_{21} = -2$, $h_{22} = 1\Omega$. Find
 - i) Z- parameters
 - ii) Y- Parameters
 - iii) ABCD parameters

OR

Obtain Z parameter for following figure 9.

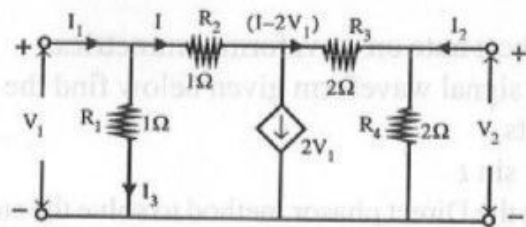


Figure 9

Roll No

EE/EI/EX - 305

B.E. III Semester

Examination, December 2015

Network Analysis

Time : Three Hours

Maximum Marks : 70

- Note:**
- i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.
 - ii) All parts of each question are to be attempted at one place.
 - iii) All questions carry equal marks, out of which part A and B (Max. 50 words) carry 2 marks, part C (Max. 100 words) carry 3 marks, part D (Max. 400 words) carry 7 marks.
 - iv) Except numericals, Derivation, Design and Drawing etc.

1. a) Enlist the properties of RLC parallel resonance network.
- b) Write down the various properties of complete incidence matrix.
- c) Explain voltage source to current source transformation.
- d) Using mesh analysis, obtain the current through the 10V battery for the circuit shown in figure 1 below.

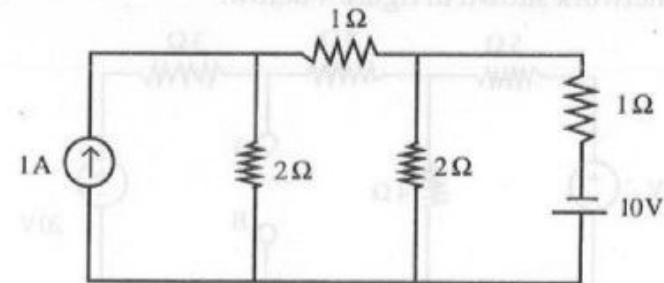


Figure 1

OR

For the resistive network shown in figure below draw the graph and tree of the network. Also develop the fundamental cut set matrix.

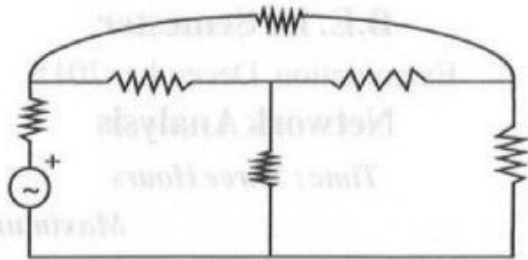


Figure 2

2. a) Why are use network theorems.
- b) State the maximum power transfer theorem.
- c) State and explain substitution theorem.
- d) Verify substitution theorem for the 2Ω resistor in the network shown in figure 3 below.

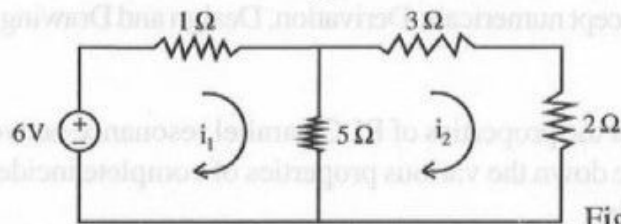


Figure 3

OR

Obtain Norton's equivalent circuit at terminal AB of the network shown in figure 4 below.

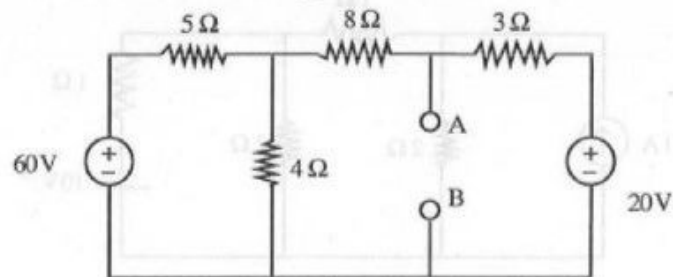


Figure 4

3. a) Write the response to shifted unit step function.
- b) Briefly describe the gate function.
- c) Explain the relationship between unit step function and unit impulse function.
- d) Obtain the Laplace transform of the pulse shown in figure 5 below.

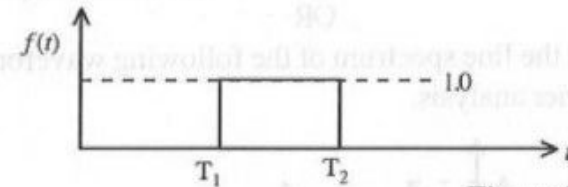


Figure 5

OR

In figure 6 below the battery voltage is applied for a steady state period. Obtain the complete expression for the current after closing the switch K. Assume $R_1 = 1\Omega$, $R_2 = 2\Omega$, $L = 1H$, $E = 10V$.

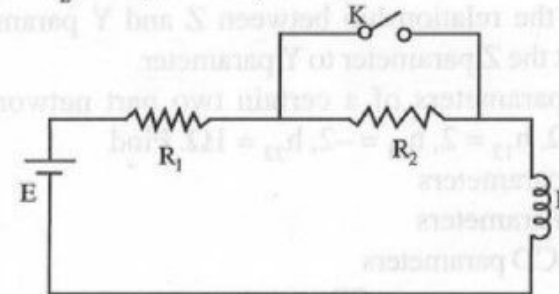


Figure 6

4. a) Write short note on waveform symmetries.
- b) For the signal waveform given below find the even and odd parts
 $f_2(t) = t \sin t$
- c) Explain the Direct phasor method to solve the steady state response to a given periodic signal input.