



# Alternating currents (A.C)

145


145

An alternating current can be defined as a current that changes its magnitude and polarity at regular intervals of time.


a

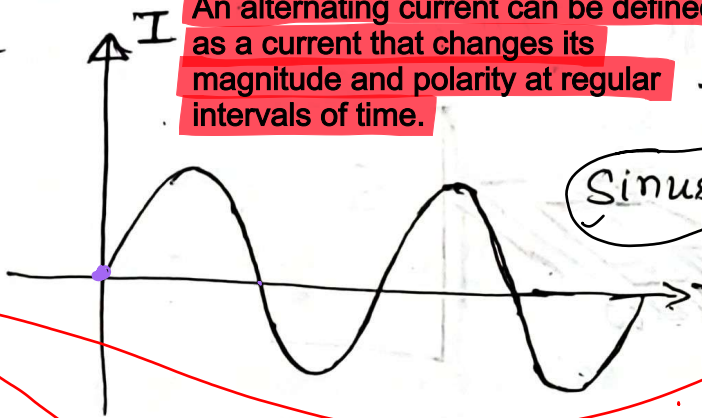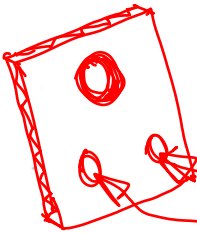


Step Ac

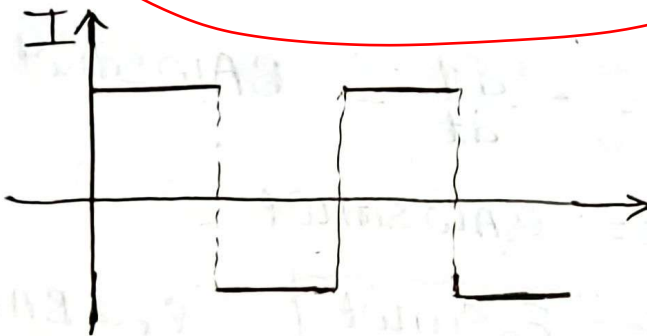

Triangular Ac

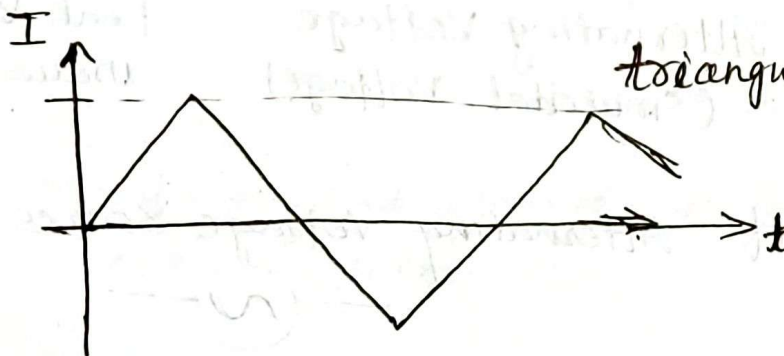


Saw tooth Ac

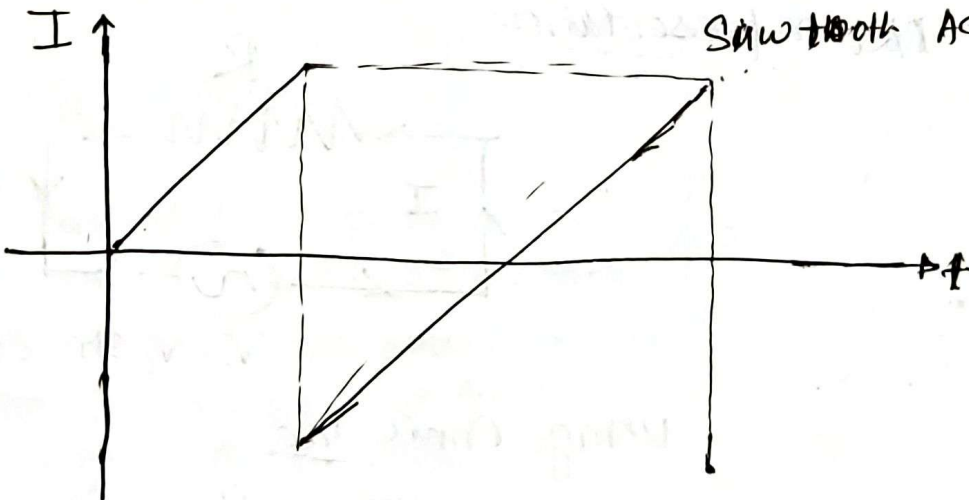

Current which continuously (periodically) changes its magnitude and direction called AC

Ac generator

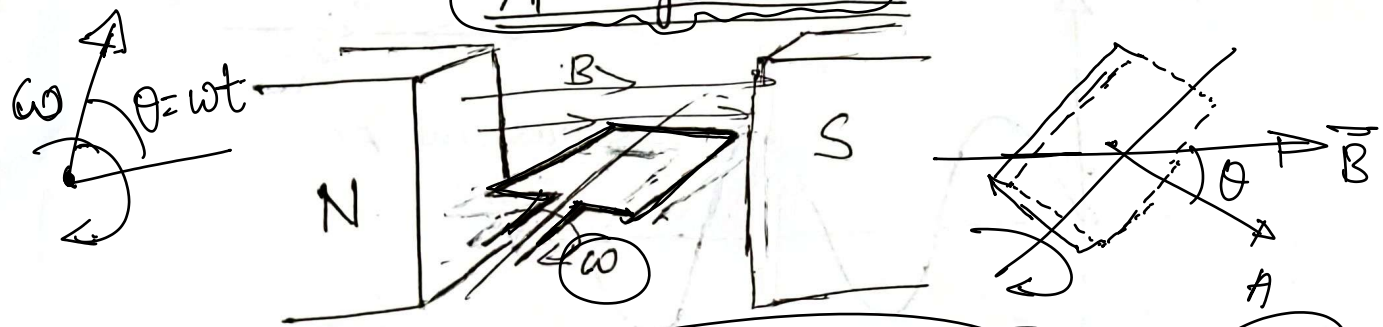

$\theta = \omega t$

constant angular velocity

$\phi = NB \cdot A \cos(\omega t)$   $BA \cos \theta$

$\mathcal{E} = -\frac{d\phi}{dt} = NBA\omega \sin \omega t$

$\mathcal{E} = NBA\omega \sin \omega t$

or,  $\mathcal{E} = \mathcal{E}_0 \sin \omega t$


Alternating Voltage  
(Sinusoidal voltage)

$\mathcal{E}_0 = NBA\omega$

Peak value of induced emf

Symbol of Alternating voltage source

In CRT representation

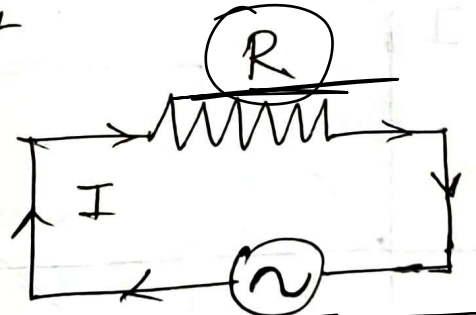

$V = V_0 \sin \omega t$

Using Ohm's law

$I = \frac{V}{R} = \frac{V_0}{R} \sin \omega t$

$I = I_0 \sin \omega t$

$I_0 = \frac{V_0}{R}$

$V_0 \rightarrow$  Peak voltage Max<sup>m</sup>  
 $I_0 \rightarrow$  Peak current Max<sup>m</sup>

$I_0 \rightarrow$  Peak current or Maximum current  
 $V_0 \rightarrow$  Peak Voltage or Maximum Voltage

$\omega \rightarrow$  Angular frequency

$$\omega = \frac{2\pi f}{T} = \frac{2\pi}{T}$$

$\omega t \rightarrow$  Phase angle or phase of AC

In general eqn of Alternating voltage

$$V = V_0 \sin(\omega t + \phi)$$

$\phi$  is Initial phase (at  $t=0$ )

Ques  $V = 10 \sin(3t + \frac{\pi}{4})$  volt

$R = 0.1 \Omega$

$I = ?$

$I_0 = ?$

$\omega = ?$

$\phi = ?$

eqn of Alternating current

$$I = I_0 \sin(\omega t + \phi)$$

Note  $\checkmark$  voltage and current in this case changes but  $\omega$  doesn't change


$\checkmark$  In house hold supply -  $f = 50 \text{ Hz}$  so  $\omega = 2\pi f = 100\pi$

220V

Average Value

$$I_{\text{Avg}} = \frac{\text{Total charge}}{\text{Total time}}$$

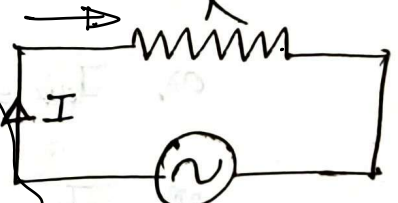$\rightarrow I_{\text{av}}$   
 \* Avg. current for a given time interval is defined as "the ratio of the total charge passed through the ckt during that time interval to the time taken"




$$V = V_0 \sin \omega t$$

$$I = I_0 \sin \omega t$$

$$I_0 = \frac{V_0}{R}$$

$$I_{\text{av}} = \frac{q}{t}$$

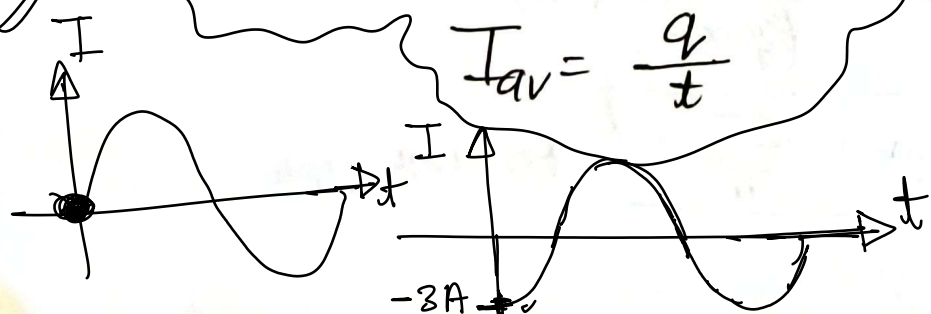

$$I = I_0 \sin(\omega t + \phi)$$

$$I = I_0 \sin \phi \quad (\text{at } t=0)$$

$\phi = \omega \times 0 = 0$

$$I = \frac{dq}{dt} \Rightarrow dq = I dt \quad I_0 = 3A$$


$$\phi = -\pi/2 \quad (I = -3A)$$

$$Q = \int I dt$$

Mathematically

$$I_{av} = \frac{\int_a^t I dt}{t}$$

Total charge between 0 to t time

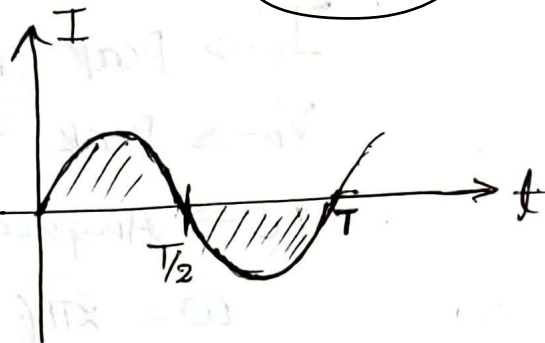

over a full cycle  $t = T$

$$I_{av} = \frac{\int_0^T I_0 \sin \omega t dt}{T}$$

$$= \frac{I_0}{T\omega} [\cos \omega t - \cos 0]$$

$$\Rightarrow \frac{I_0}{T\omega} [\cos \frac{2\pi}{T} \times T - \cos 0]$$

$$I_{av} = \frac{I_0}{T} \left[ \frac{-\cos \omega t}{\omega} \right]_0^T = 0$$

0

→ So, we calculate  $I_{av}$  over a half cycle i.e. for  $t = T/2$

V.V.I

$$I_{av} = \frac{\int_0^{T/2} I_0 \sin \omega t dt}{T/2}$$


$$\text{or, } I_{av} = \frac{2I_0}{T} \int_0^{T/2} \sin \omega t dt$$

$$\text{or, } I_{av} = \frac{2I_0}{T} \left[ \frac{-\cos \omega t}{\omega} \right]_0^{T/2}$$

$$\text{or, } I_{av} = \frac{-2I_0}{\omega T} \left[ \cos \frac{2\pi}{T} \times \frac{T}{2} - \cos \frac{2\pi}{T} \times 0 \right] \quad \text{as, } \omega = \frac{2\pi}{T}$$

$$\text{or, } I_{av} = \frac{-2I_0}{\left(\frac{2\pi}{T}\right) \times T} \times (-2)$$
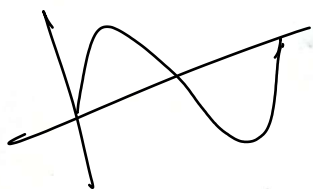
$$\text{or, } \boxed{I_{av} = \frac{2I_0}{\pi}} \quad \text{for half cycle}$$



Similarly

$$V_{av} = \frac{2V_0}{\pi} \quad \text{For half cycle}$$

$$\& V_{av} = 0 \quad \text{For full cycle}$$

→ The  $I_{av}$  &  $V_{av}$  can't be used to calculate power calculation in ckt

RMS current and RMS Voltage

RMS  
(Root mean square)


RMS → Root mean square

as  $P = I^2 R$

or  $P = (I_0^2 R \sin^2 \omega t)$  ( $I_{eff}^2 R$ )

or  $P = P_0 \sin^2 \omega t$

$$P_0 = I_0^2 R$$

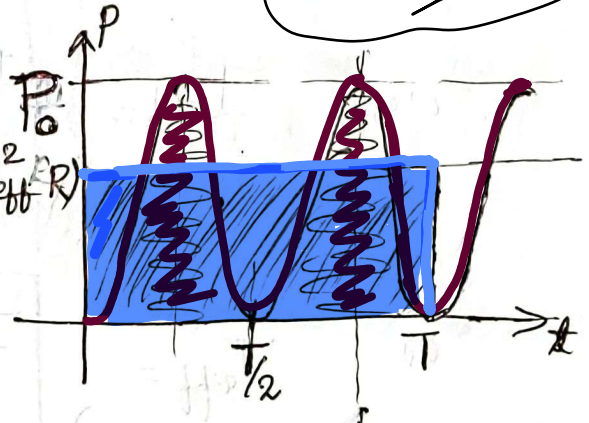

Effective or RMS current is a steady (DC) current which gives us same amount of heat in one cycle (time period T) as that given by

AC

∴ RMS current =  $I_{RMS}$  or  $I_{eff}$

then mathematically

$$I_{eff}^2 R T = \int_0^T I^2 R dt$$

Heat generated in T time by  $I_{eff}$

$$\text{Energy} = \int P dt$$

Power

$$\int_0^T I^2 R dt$$

Heat generated in T time by AC

Using this result

$$I_{\text{eff}}^2 R T = \int_0^T I^2 R dt$$

$$I_{\text{eff}}^2 T = \int_0^T I_0^2 \sin^2 \omega t dt$$

or,  $I_{\text{eff}} = \sqrt{\frac{\int_0^T I^2 dt}{T}}$  RMS

$I_{\text{eff}} = \sqrt{\frac{\int_0^T I_0^2 \sin^2 \omega t dt}{T}}$  (mean) avg of square of I

or,  $I_{\text{eff}} = \sqrt{\frac{I_0^2 \int_0^T (1 - \cos 2\omega t) dt}{2T}}$

or,  $I_{\text{eff}} = \sqrt{\frac{I_0^2 \left[ \frac{1}{2} \int_0^T dt - \int_0^T \frac{\cos 2\omega t}{2} dt \right]}{T}}$

or,  $I_{\text{eff}} = \sqrt{\frac{I_0^2 \times T/2}{T}}$

or,  $I_{\text{eff}} = \frac{I_0}{\sqrt{2}}$

$I_0 = I_{\text{max}}$

$I_{\text{RMS}} = \frac{I_0}{\sqrt{2}}$

Similarly

$V_{\text{eff}} = \frac{V_0}{\sqrt{2}}$   $V_0 = V_{\text{max}}$

All AC appliances are rated with RMS values of voltage and current (alternating)

Ex

A 60 W, 220 V. bulb

→ RMS Voltage

↳ Resistance

to find (i) Peak voltage

(ii) RMS current

(iii) Resistance

(151)

(151)

P, V, R.

$$\frac{V^2}{R} = P$$

Soln

Note

$$V_{rms} = 220V$$

$P = \frac{V_{rms}^2}{R}$
$P = I_{rms}^2 R$
$P = V_{rms} \cdot I_{rms}$

→ Formulae valid only if only resistances are in ckt (i.e. no capacitor, no inductor)

So (i)  $V_0 = \text{Peak voltage} = V$

$$V_{rms} = \frac{V_0}{\sqrt{2}} \Rightarrow V_0 = \sqrt{2} V_{rms}$$

$$\text{or, } V_0 = \sqrt{2} \times 220 \text{ V}$$

(ii) RMS current

$$I_{rms} = \frac{P}{V_{rms}} = \frac{60}{220}$$

$$I_{rms} = \frac{3}{11} \text{ A}$$

$$I_0 = \sqrt{2} I_{rms} = \frac{3\sqrt{2}}{11} \text{ A}$$




(iii) Resistance

$$R = \frac{V_{rms}^2}{P}$$

$$= \frac{220 \times 220}{60}$$

$$R = \frac{2420}{3} \Omega$$

# AC Circuits

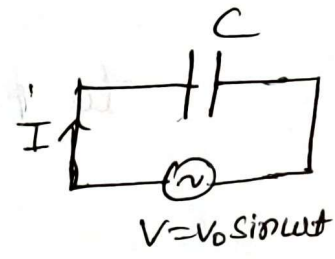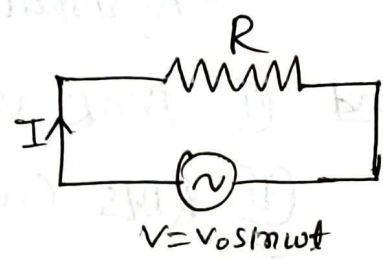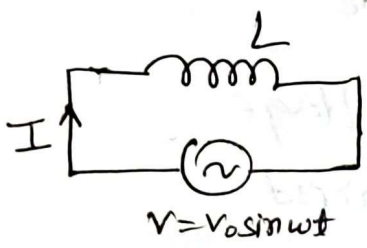

two SHM oscillation can be added

by using phasor diagram

$$y = A \sin(\omega t + \theta)$$


$$V = V_0 \sin(\omega t + \phi)$$

as  $y = y_1 + y_2$

$$y = A_1 \sin \omega t + A_2 \sin(\omega t + \delta)$$

$$A = \sqrt{A_1^2 + A_2^2 + 2A_1A_2 \cos \delta}$$

Phasor diagram method.

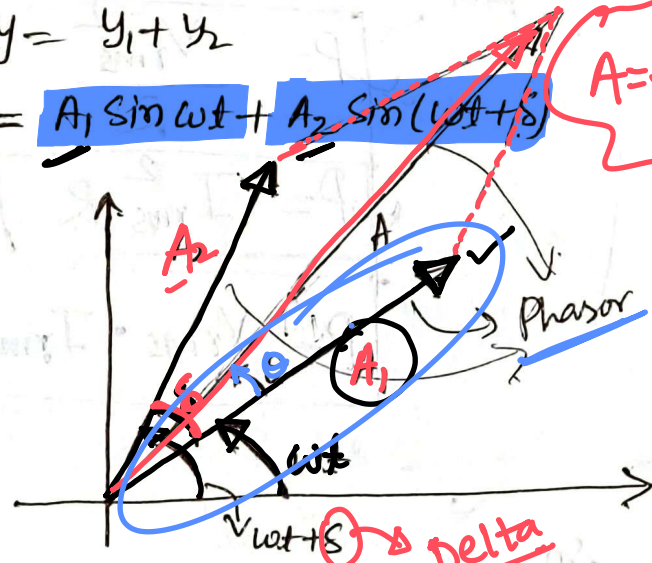

$$\tan \theta = \frac{A_2 \sin \delta}{A_1 + A_2 \cos \delta}$$

$$y = A \sin(\omega t + \theta)$$


$$A = \sqrt{A_1^2 + A_2^2 + 2A_1A_2 \cos \delta}$$

Q  $3 \sin \omega t + 4 \sin(\omega t + 60^\circ)$   
 $\sqrt{37} \sin(\omega t + 14.8^\circ)$



Since here voltages and currents are sinusoidal, these can't be added simply. We have to use a convenient method which using which we can add two Alternating (sinusoidal) quantities taking the effect of their phase and magnitude at the same time.

Phasor representation

$$V = V_0 \sin \omega t$$

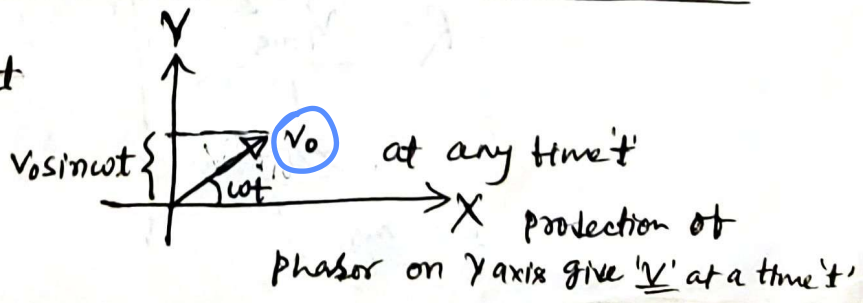



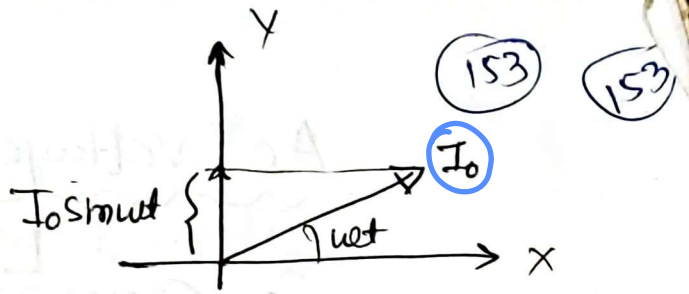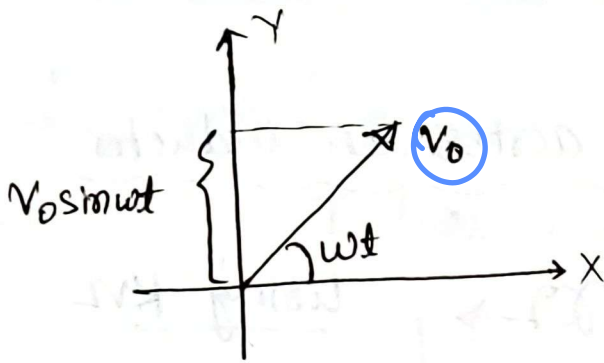

Note Voltage and current are not vectors but only this method we add these quantities as vectors

AC voltage across a resistance


Pure Resistive Circuit

$I = \frac{V}{R}$

or,  $I = \frac{V_0 \sin \omega t}{R}$

or,  $I = I_0 \sin \omega t$

$\frac{V_0}{R}$


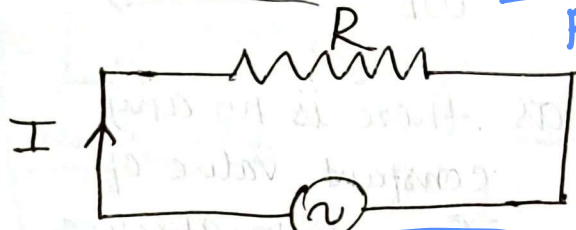


$V = V_0 \sin \omega t$

Here (a) V & I are in phase

(b)  $I_0 = \frac{V_0}{R}$

Phasor diagram

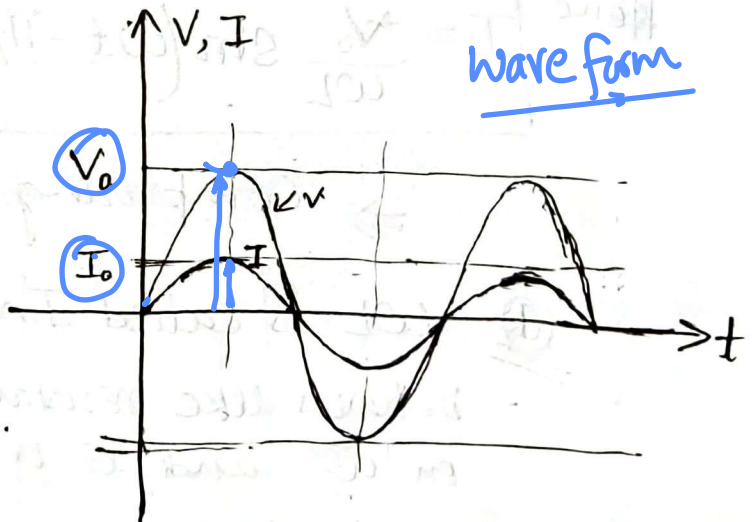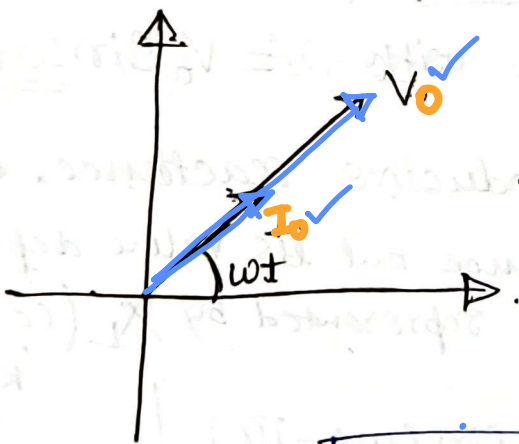


$V_0 = I_0 R$

$V = IR$

For AC resistive (purely) Ckt

# AC voltage across an inductor

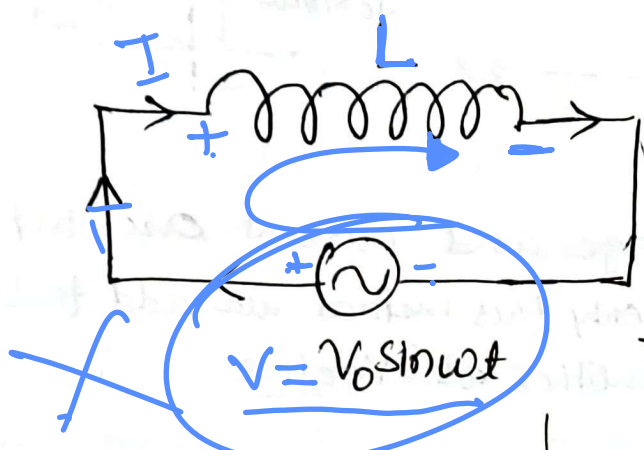

Using KVL

$$-L \frac{dI}{dt} + V_0 \sin \omega t = 0$$

$$\Rightarrow L \frac{dI}{dt} = V_0 \sin \omega t$$

$$\Rightarrow dI = \frac{V_0}{L} \sin \omega t dt$$

$$\Rightarrow I = \int \frac{V_0}{L} \sin \omega t dt$$

$$\Rightarrow I = +\frac{V_0}{L} \left( \frac{-\cos \omega t}{\omega} \right) + c$$

$$\Rightarrow I = -\frac{V_0}{\omega L} \cos \omega t + c$$

or,  $I = \frac{V_0}{\omega L} \sin(\omega t - \pi/2) + c$

as there is no any constant value of current in absence of voltage. so

I will also oscillate about (up & down)

'0' value, so  $c=0$

Hence:  $I = \frac{V_0}{\omega L} \sin(\omega t - \pi/2)$

$-\cos \theta$   
 $\sin(\theta - \pi/2)$   
 $\sin(\pi/2 - \theta) = \cos \theta$

Comparing with  $V = V_0 \sin \omega t$

(1)  $\omega L$  is called Inductive reactance, it behaves like resistance but its value depends on ' $\omega$ ' and it is represented by  $X_L$  (called 'Reff' also)

So  $I = \frac{V_0}{X_L} \sin(\omega t - \pi/2)$

SI unit =  $\Omega$

$V_0 = I_0 X_L$   
 $V_{rms} = I_{rms} X_L$

Purely Inductive AC ckt

$X_L = \omega L$       $I = I_0 \sin(\omega t - \pi/2)$

$\omega = 2\pi f = \frac{2\pi}{T}$       $I_0 = V_0 / X_L$

$$X_L = 2\pi fL = \frac{2\pi}{T}L$$

(2)

Comparing with  $V = V_0 \sin \omega t$

155  
155

For DC

$$f = 0$$

$$\omega = 0$$

$$X_L = 0$$

For DC Inductor acts as short circuit


If  $V = V_0 \sin \omega t = 0$

$I$  lags behind  $V$  by  $\pi/2$

$$I = I_0 \sin(\omega t - 90^\circ)$$

$$I = -I_0 \sin \omega t$$

$$I = -I_0$$

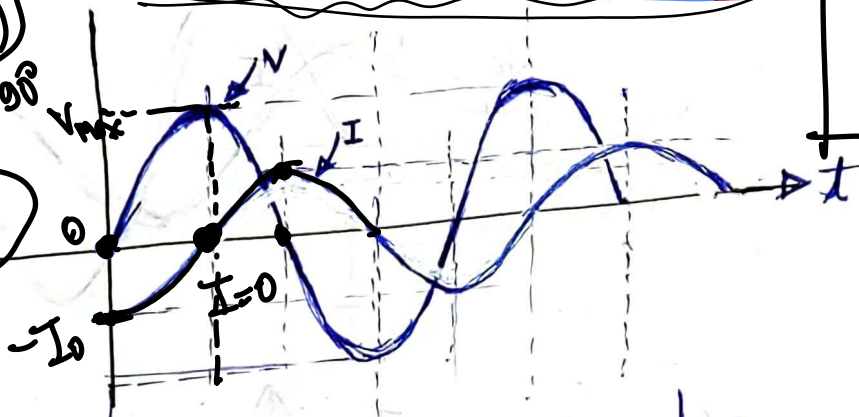

For dc  $\omega = 0$  so  $X_L = \omega L = 0$

For dc No  $X_L$  exist


$$V = 10 \sin(3t + 60^\circ)$$

$$L = 10 \text{ mH}$$

$$X_L = \omega L$$

$$V_0 = 10$$

$$I_0 = ?$$

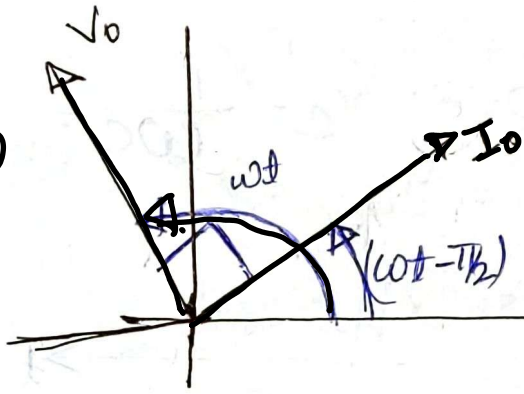


$$I = \frac{1000}{3} \sin(3t - 30^\circ)$$

$$\frac{10}{10 \times 10^{-3} \times 3}$$

AC Voltage across capacitor
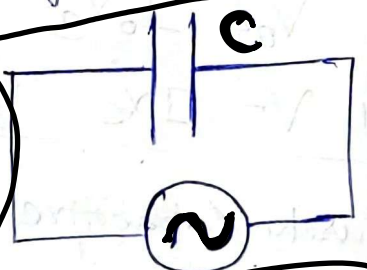
$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC}$$




$$q = CV = CV_0 \sin \omega t$$

$$\frac{dq}{dt} = CV_0 \omega \cos \omega t$$

$$I = \frac{V_0}{\left(\frac{1}{\omega C}\right)} \sin(\omega t + \pi/2)$$

$X_C$

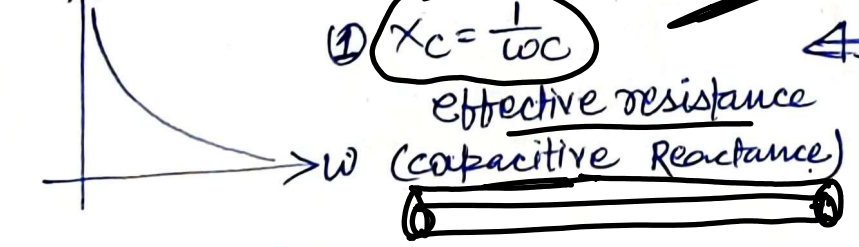

$$X_C = \frac{1}{\omega C}$$


$$I = \frac{V_0}{X_C} \sin(\omega t + \pi/2)$$

$$X_C = \frac{1}{\omega C}$$


2  $V$  lags behind  $I$  by  $\pi/2$

$$V = V_0 \sin \omega t = 0$$
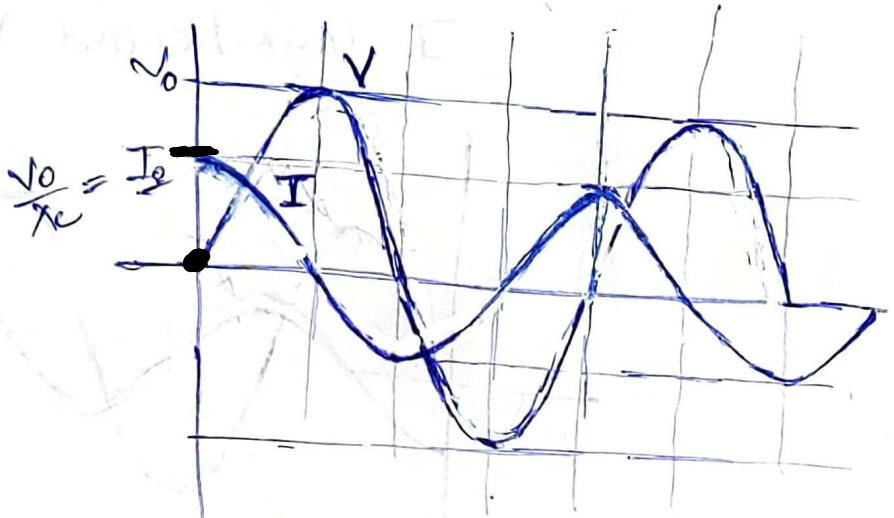
$$I = I_0 \sin(\omega t - \pi/2) = -I_0 \cos \omega t$$



3 Phasor diagram

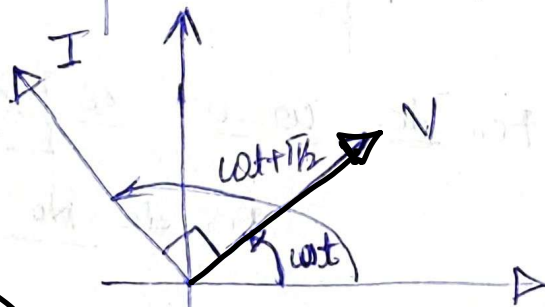


④ For DC  $f=0$   
 $\omega=0$

$$X_c = \frac{1}{\omega C} \rightarrow \infty \rightarrow \text{open circuit}$$


For DC ✓

$$X_c = \infty$$

Open ckt.

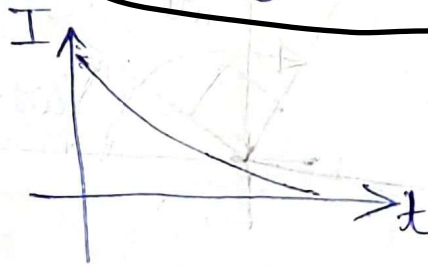

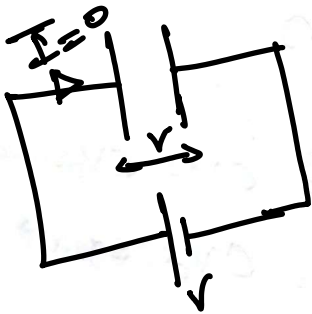For DC circuit  
Capacitor acts  
as open circuit




$$V_0 = I_0 X_c$$

$$V_{RMS} = I_{RMS} X_c$$

Purely capacitive AC ckt  $10^{-6}$

Ques  
 $V_{RMS} = \frac{V_0}{\sqrt{2}}$

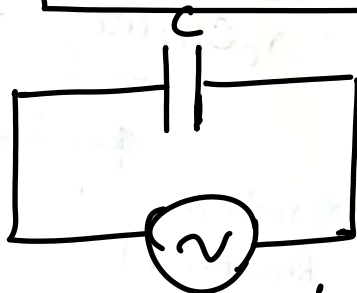

$$C = 3 \mu F$$

$$\omega = 100$$

$$X_c = \frac{1}{100 \times 3 \times 10^{-6}}$$


$$I_0 =$$

$$I = I_0$$



$$V = 15 \sin(\omega t - 30^\circ)$$

Series combination

① L-R CKT

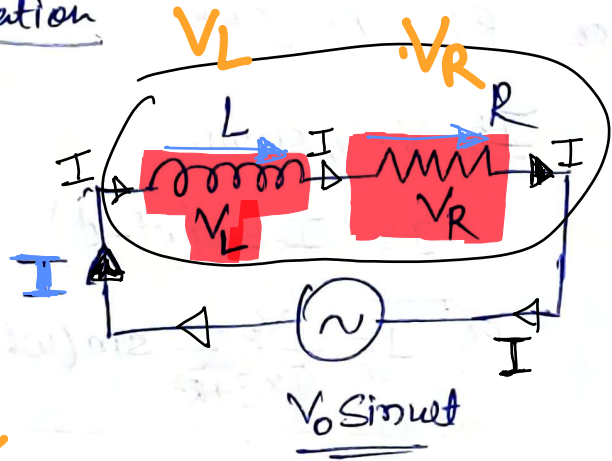

in series

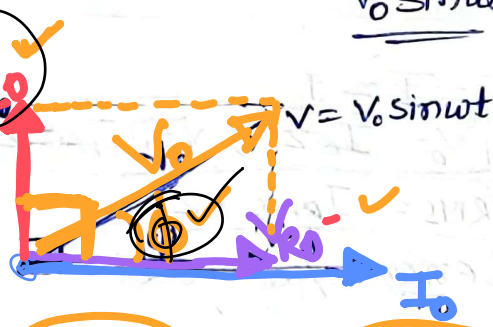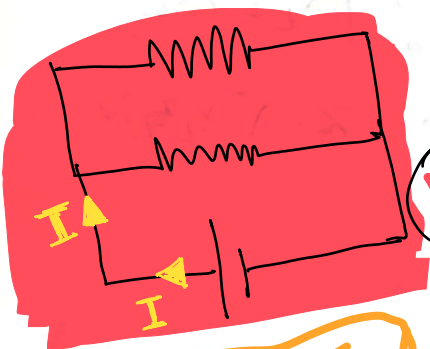

$V_L = \text{Max}^m \text{ voltage across inductor}$   
 $V_R = \text{max}^m \text{ voltage across resistor}$   
 $V_0 = \text{Max}^m \text{ supplied voltage}$

$\sqrt{A_1^2 + A_2^2 + 2A_1A_2 \cos \theta}$   
 $\sqrt{V_L^2 + V_R^2 + 2V_L V_R \cos 90^\circ}$   
also  
 $\sqrt{V_L^2 + V_R^2}$

$V_L = I_0 X_L$  ;  $V_R = I_0 R$

$V_0 = \sqrt{V_L^2 + V_R^2}$


$V_0 = \sqrt{I_0^2 X_L^2 + I_0^2 R^2}$

$V_0 = I_0 \sqrt{X_L^2 + R^2}$

or,  $V_0 = I_0 Z$

$Z \rightarrow \text{Impedance of CKT}$   
 $Z = \sqrt{X_L^2 + R^2}$

SI unit -  $\Omega$

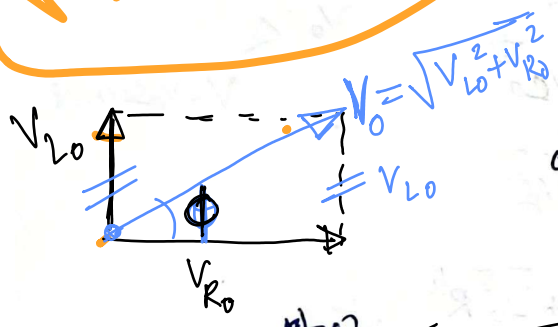

$\tan \phi = \frac{V_L}{V_R} = \frac{I_0 X_L}{I_0 R}$

$\phi = \tan^{-1} \left( \frac{X_L}{R} \right)$

also  $\cos \phi = \frac{V_R}{V_0} = \frac{I_0 R}{I_0 Z}$

$\phi = \cos^{-1} (R/Z)$

Power factor

I can be written as  
 $I = I_0 \sin(\omega t - \phi)$

because I is lagging behind V by angle phi

$I_0 = \frac{V_0}{Z} = \frac{V_0}{\sqrt{X_L^2 + R^2}}$

So For RL AC ckt

$V = V_0 \sin \omega t$

$I = I_0 \sin(\omega t - \phi)$

or,  $I = \frac{V_0}{\sqrt{X_L^2 + R^2}} \sin(\omega t - \phi)$

$\tan \phi = \frac{X_L}{R} = \frac{\omega L}{R}$

$X_L = \omega L$

$Z = \sqrt{X_L^2 + R^2}$

$I_{RMS} = \frac{V_{RMS}}{Z}$


$X_L = \omega L = 2\pi f L$

$V_0 = I_0 Z ; \sqrt{X_L^2 + R^2} = Z$

$V_{RMS} = I_{RMS} \times Z$

R-c Series AC ckt



Ques  $R=4\Omega$   $L=3mH$

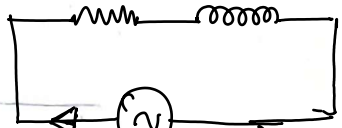

$V = 20 \sin(1000t)$

$X_L = ?$   $Z = ?$

$\phi = ?$   $I_0 = ?$

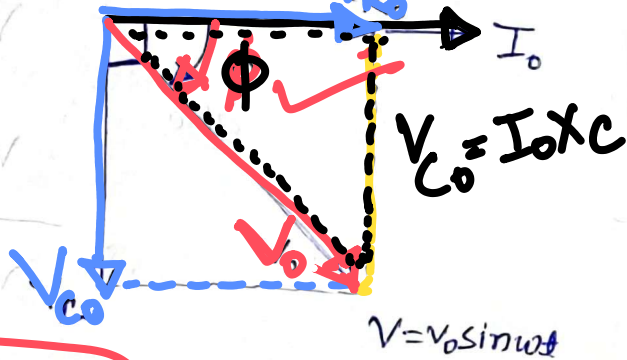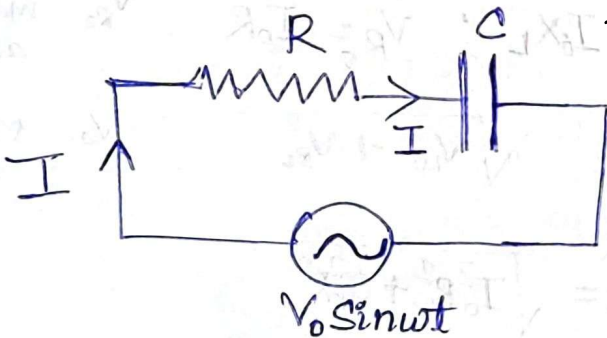

$V_{C0} = I_0 X_C$  ✓

$V_{R0} = I_0 R$

$V_0 = \sqrt{V_{C0}^2 + V_{R0}^2}$

$V_0 = \sqrt{I_0^2 X_C^2 + I_0^2 R^2}$

$V_0 = I_0 \sqrt{X_C^2 + R^2}$

or,  $V_0 = I_0 Z ; Z = \sqrt{X_C^2 + R^2}$

Impedance

$V_{R0} \rightarrow V_{max}$  across 'R'

$V_{C0} \rightarrow V_{max}$  across 'C'

$V_0 \rightarrow$  'Max<sup>m</sup> Supplied Voltage'

$\tan \phi = \frac{V_{C0}}{V_R} = \frac{I_0 X_C}{I_0 R} = \frac{X_C}{R} = \frac{1}{\omega RC}$  ✓

$\tan \phi = \frac{1}{\omega RC}$

$\cos \phi = \frac{V_R}{V} = \frac{R}{Z}$

So For RC AC CKL

If  $V = V_0 \sin \omega t$  supplied voltage

$I = I_0 \sin(\omega t + \phi)$

(Forward)

$I_0 = \frac{V_0}{Z} = \frac{V_0}{\sqrt{X_C^2 + R^2}}$  Since I is leading by an angle  $\phi$  from supplied voltage

Also

$V_0 = I_0 Z$

$Z = \sqrt{X_C^2 + R^2}$


$V_{RMS} = I_{RMS} \times Z$

$X_C = \frac{1}{\omega C}$ ;  $\tan \phi = \frac{V_{C0}}{V_{R0}} = \frac{1}{\omega RC}$

$\cos \phi = \frac{R}{Z}$



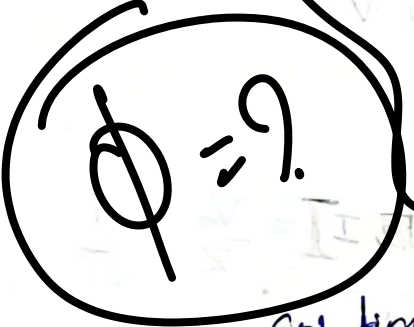~~$\frac{V_{L0}}{V_{R0}} = \frac{X_L I_0}{I_0 R}$~~   
 ~~$\frac{V_{L0}}{V_{R0}} = \frac{X_L}{R}$~~



So given 100 V dc  $\rightarrow$  1 A current

So given 100 V, 50 Hz AC  $\rightarrow$  0.5 A current

- find a) Impedance of coil
- b) Reactance, Resistance  $\rightarrow R = ?$
- c) Instantaneous current in AC

If  $V = V_0 \sin \omega t$  Supply voltage

$I = ?$

In dc,  $X_L = 0$   
only R

So  $100 = R \times I$

or,  $R = \frac{100}{1} = 100 \Omega$

In AC  $X_L = \omega L$  & effective resistance

$Z = \sqrt{X_L^2 + R^2}$

Given for AC  
 $V_{RMS} = 100V$   
 $I_{RMS} = 0.5A$

$I_{RMS} = \frac{V_{RMS}}{Z} \Rightarrow 0.5 = \frac{100}{Z} \Rightarrow Z = 200 \Omega$

~~$V = IZ$~~

Solution

Now

$$Z = \sqrt{X_L^2 + R^2} = \sqrt{(50L)^2 + 100^2}$$

$$V_0 = ?$$

$$I_0 = \frac{V_0}{Z}$$

$$\Rightarrow 200 = \sqrt{(50 \times 2\pi \times L)^2 + 100^2}$$

$$\Rightarrow 200^2 = \underbrace{(100\pi L)^2}_{X_L} + 100^2 \Rightarrow X_L = \sqrt{200^2 - 100^2}$$

$$\Rightarrow 200^2 - 100^2 = X_L$$

$$\Rightarrow 100\sqrt{3} = X_L$$

$$\Rightarrow X_L = \omega L = 2 \times \pi \times 50 \times L = 100\sqrt{3}$$

$$L = \frac{\sqrt{3}}{\pi} \text{ H}$$

$$X_L = \omega L$$

$$X_L = 2\pi f L$$

$$\phi = ?$$
  
$$I_0 = ?$$

Now

Instantaneous current

$$V_{RMS} = 100V = \frac{V_0}{\sqrt{2}}$$

$$V_0 = 100\sqrt{2} \text{ V}$$

$$I_{RMS} = 0.5 = \frac{I_0}{\sqrt{2}}$$

$$I_0 = \sqrt{2} I_{RMS} \dots \text{or } I_0 = \frac{V_0}{Z} = \frac{1}{\sqrt{2}} \checkmark$$

$$\frac{V_0}{\sqrt{2}} = V_{RMS} \Rightarrow V_0 = 100\sqrt{2}$$

Now using

$$I_0 = \frac{V_0}{Z} \text{ or } I = I_0 \sin(\omega t - \phi)$$

$$\tan \phi = \frac{V_L}{V_R} = \frac{\omega L}{R}$$

$$\tan \phi = \frac{X_L}{R} = \frac{100\sqrt{3}}{100}$$

$$\phi = \pi/3$$

as  $Z = 100\Omega$   
 $V_0 = 100\sqrt{2} \text{ V}$

$$I = \frac{1}{\sqrt{2}} \sin\left(\frac{100\pi t}{\omega} - \pi/3\right)$$

$$\omega = 2\pi f$$




# Example

161

21  
161

Find  $V_{RMS}$

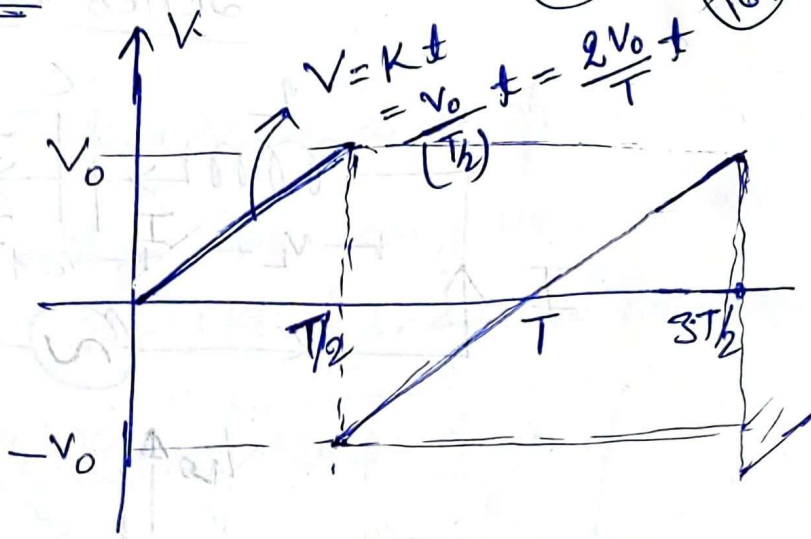

$$V_{RMS} = \sqrt{\frac{\int_0^{T/2} V_0^2 dt}{T/2}}$$

$$V_{RMS} = \sqrt{\frac{\int_0^{T/2} \left(\frac{2V_0}{T}\right)^2 t^2 dt}{T/2}}$$

$$V_{RMS} = \sqrt{\frac{4V_0^2 \int_0^{T/2} t^2 dt}{T/2}}$$



$$\Rightarrow V_{RMS} = \sqrt{\frac{8V_0^2}{T^3} \int_0^{T/2} t^2 dt}$$

$$\Rightarrow V_{RMS} = \sqrt{\frac{8V_0^2}{T^3} \left[ \frac{t^3}{3} \right]_0^{T/2}}$$

$$V_{RMS} = \sqrt{\frac{8V_0^2}{T^3} \times \frac{T^3}{8} \times \frac{1}{3}}$$

$$V_{RMS} = \frac{V_0}{\sqrt{3}}$$

# Series LCR CKT

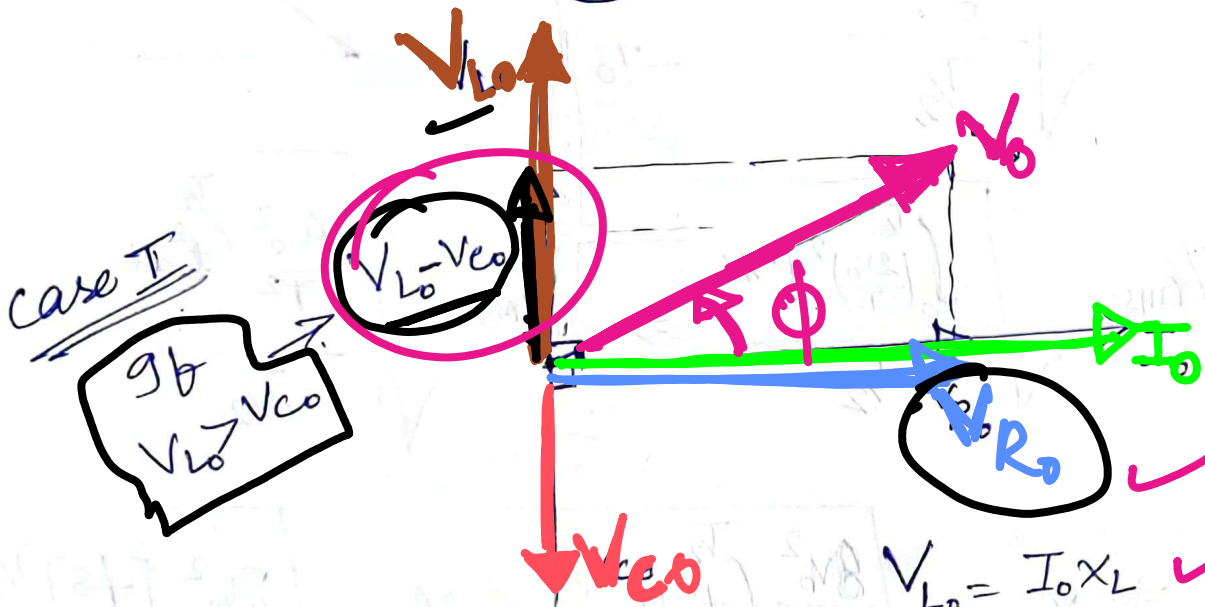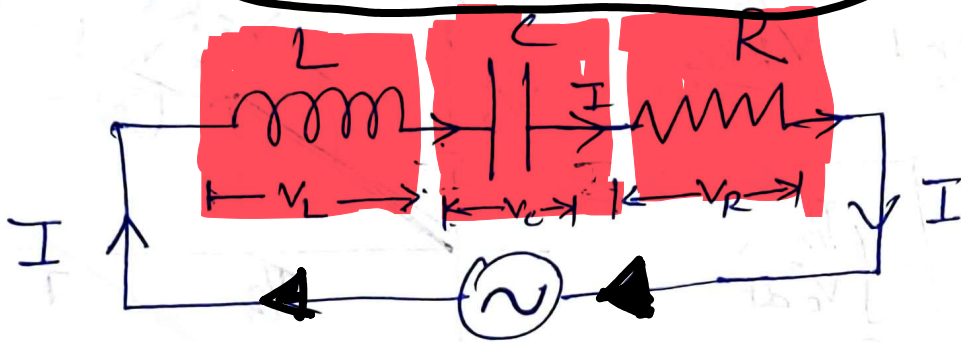

$V_L = I_0 X_L$  ✓  
 $V_R = I_0 R$  ✓  
 $V_C = I_0 X_C$  ✓

$$V_0 = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\text{or, } V_0 = \sqrt{I_0^2 R^2 + (I_0 X_L - I_0 X_C)^2}$$

$$\text{or, } V_0 = I_0 \sqrt{R^2 + (X_L - X_C)^2}$$


$$V_0 = I_0 Z$$

$$\text{or, } I_0 Z = V_0$$

where,  $Z = \sqrt{R^2 + (X_L - X_C)^2}$   
 Impedance ✓

also  
 $I_{RMS} = \frac{V_{RMS}}{Z}$

$I = I_0 \sin(\omega t - \phi)$

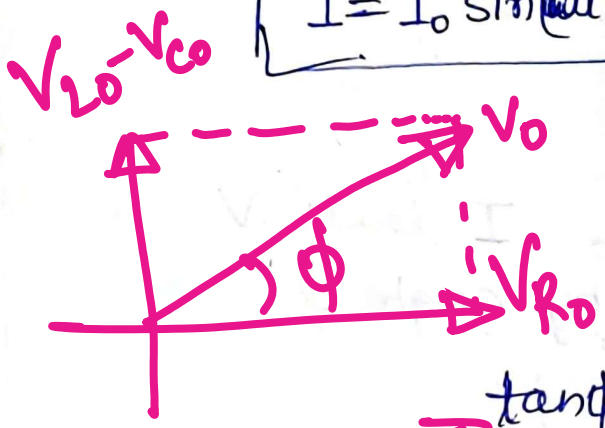

I lags V by angle phi

ckt is ~~more~~ acting like RL-ckt (Inductive behaviour)

$\tan \phi = \frac{V_{L0} - V_{C0}}{V_{R0}} \Rightarrow \tan \phi = \frac{X_L - X_C}{R}$

So

$I_0 = \frac{V_0}{Z}$  ;  $Z = \sqrt{R^2 + (X_L - X_C)^2}$


also  $I_{RMS} = \frac{V_{RMS}}{Z}$

$V = V_0 \sin \omega t$

$I = \frac{V_0}{Z} \sin(\omega t - \phi)$

$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$

Case II  
 $V_C > V_L$

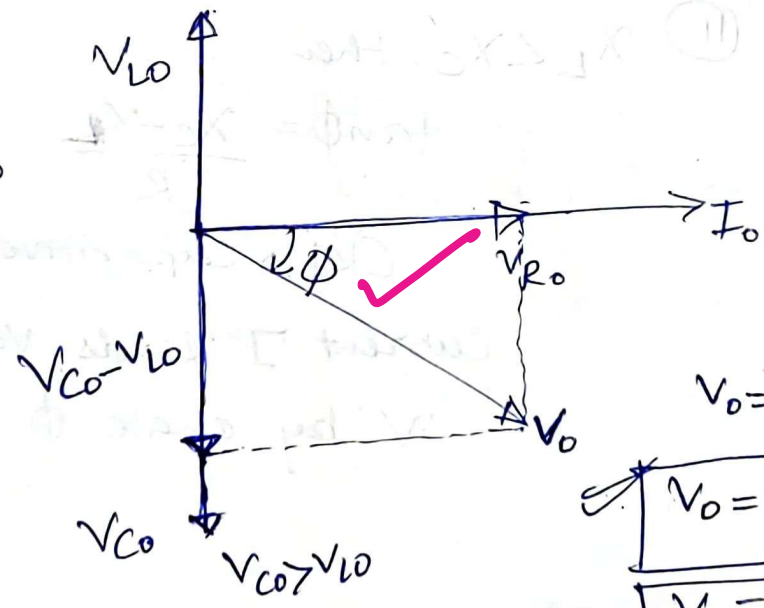

$V_0 = \sqrt{V_{R0}^2 + (V_{C0} - V_{L0})^2}$

$V_0 = I_0 \sqrt{R^2 + (X_C - X_L)^2}$

or,  $V_0 = I_0 Z$

$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$I = \frac{V_0}{Z} \sin(\omega t + \phi)$$

because I leads V  
by angle  $\phi$

$$\tan \phi = \frac{X_C - X_L}{R}$$

→ overall behaviour of CKT is capacitive

So

if

(i)  $X_L > X_C$  then

$$\tan \phi = \frac{X_L - X_C}{R}$$

CKT → Inductive


current I lags by  $\phi$   
w.r.t voltage 'V' (supplied)

(ii)  $X_L < X_C$ , then

$$\tan \phi = \frac{X_C - X_L}{R}$$



CKT → Capacitive

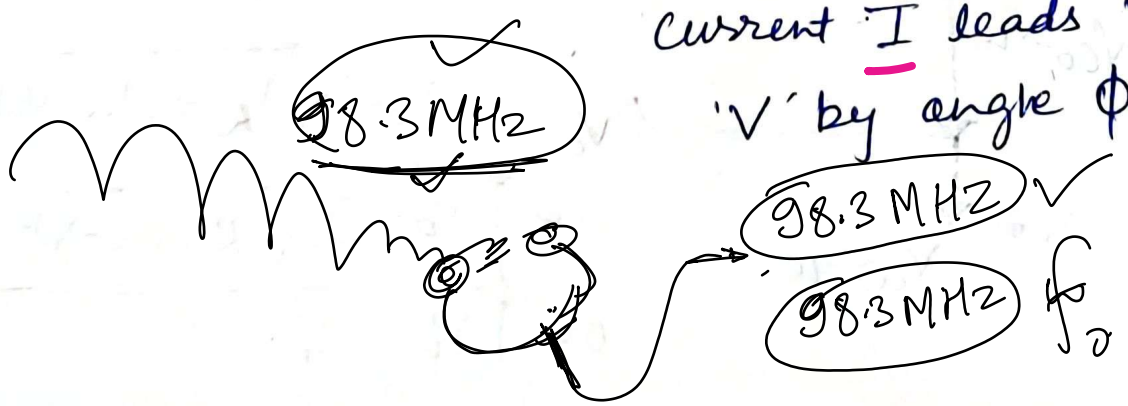current I leads voltage (supply)  
'V' by angle  $\phi$



Case-3

Resonance in L-C-R Series AC CKT

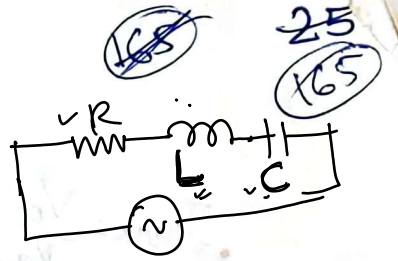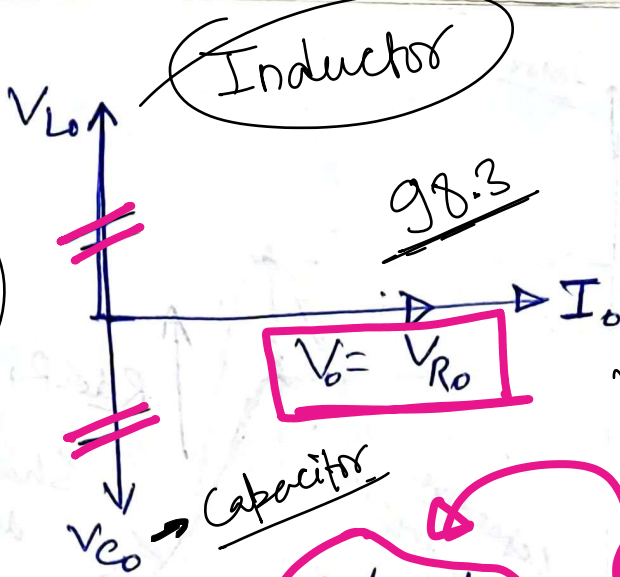

$$V_0 = \sqrt{I_0 R^2 + (I_0 X_L - I_0 X_C)^2}$$

$$V_0 = I_0 R$$

$$V_0 = \sqrt{V_R^2 + (V_L - V_C)^2}$$

When

→ (V) Voltage and current (I) in series L-C-R AC CKT are in same phase, this situation is called resonance

When  $V_{L0} = V_{C0}$  then

$$V_{R0} = V_0$$

$$(V_R)_{rms} = V_{rms}$$

$$I_0 X_L = I_0 X_C$$

$$X_L = X_C$$

$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0^2 L = \frac{1}{C}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = 2\pi f$$

Resonant Angular Frequency

Resonant Frequency

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

At \* CKT behaviour → Purely resistive

$f_{circuit} = f_{current}$


Current at resonance

$$I_0 = \frac{V_0}{Z} = \frac{V_0}{R}$$

$$I_{RMS} = \frac{V_{RMS}}{R}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = R$$

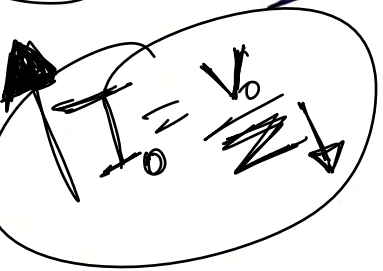

\* In phase current


$$I = \frac{V_0}{R} \sin \omega t$$

$$\therefore \tan \phi = \frac{X_L - X_C}{R} = 0$$


$$\Rightarrow \phi = 0$$

In resonance condition

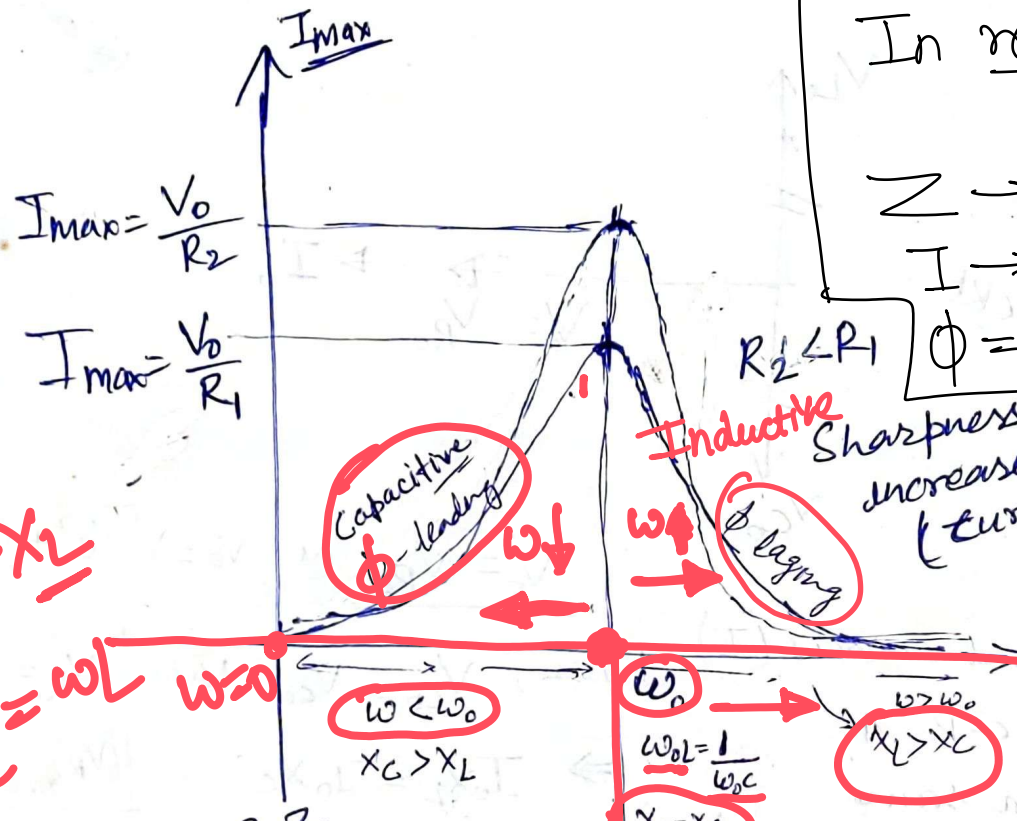$Z \rightarrow \text{min}^m = R$   
 $I \rightarrow \text{Max}^m = \frac{V}{R}$   
 $\phi = 0^\circ \quad \cos\phi = 1$




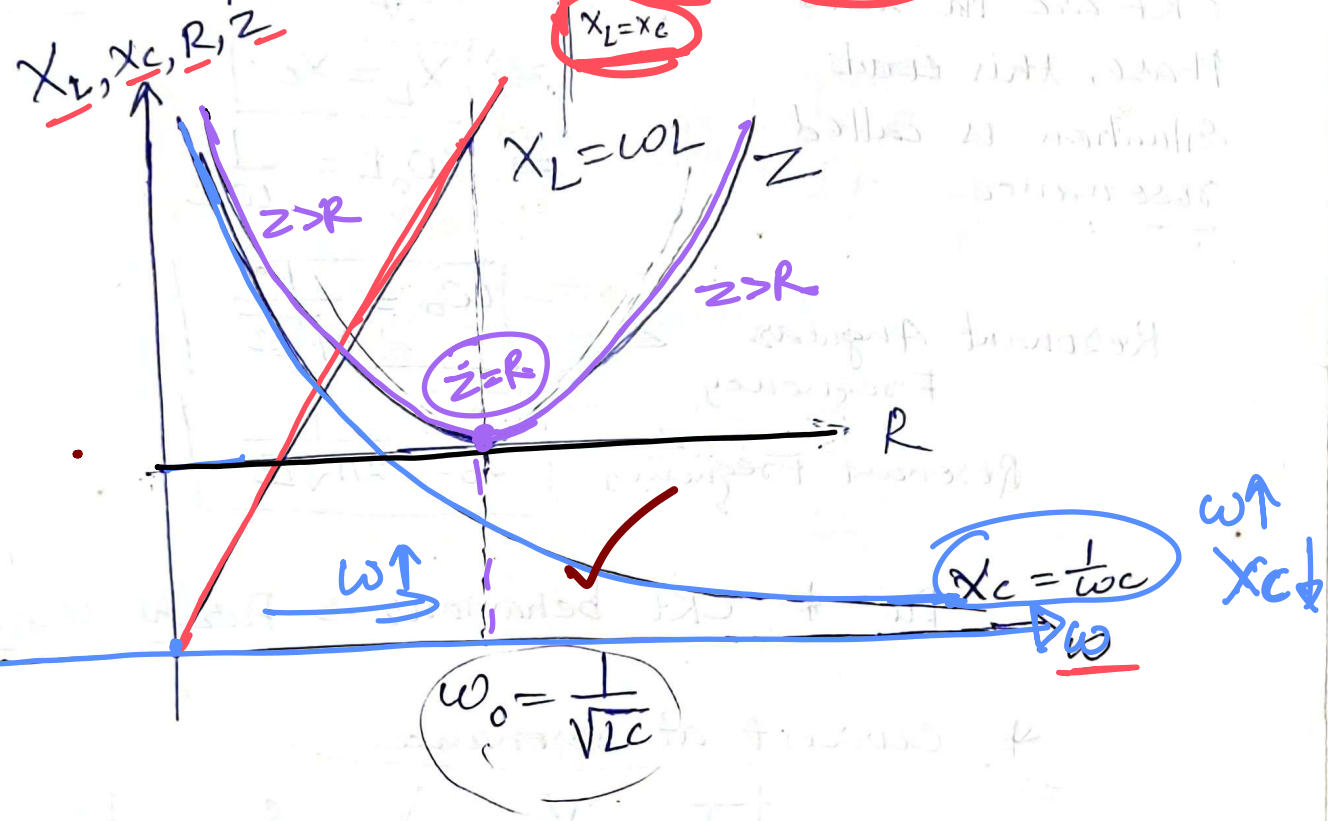$X_C > X_L$   
 $\frac{1}{\omega C} = \omega L$


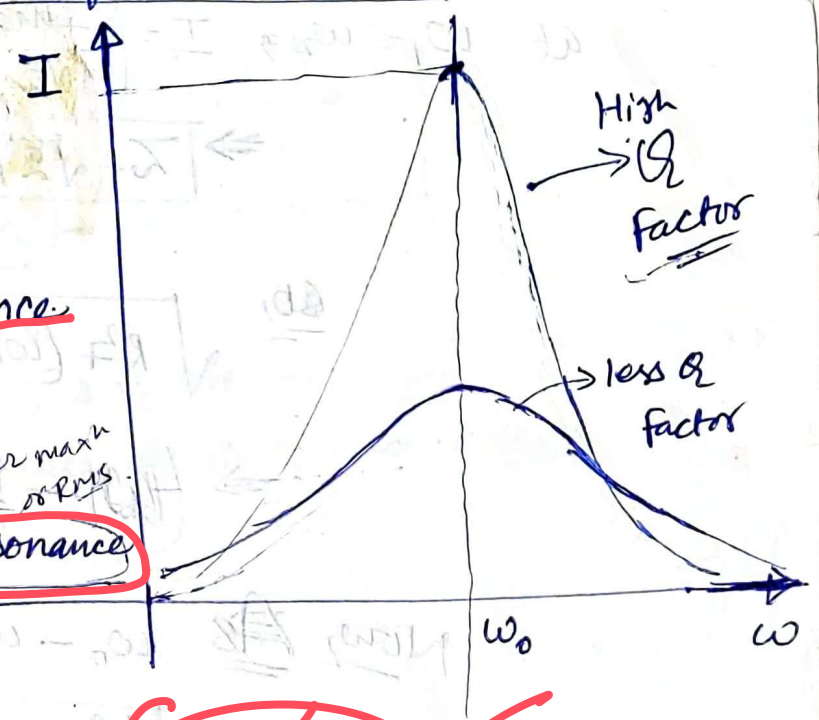
# Sharpness of Resonance

✓ Q-Factor defines Sharpness of Resonance



Mathematically

$Q = \frac{V_C \text{ or } V_L \text{ at resonance}}{V_R}$

$Q = \frac{IX_C}{IR}$


$Q = \frac{IX_L}{IR}$

$Q = \frac{X_C}{R} = \frac{1}{\omega RC}$

also  $Q = \frac{\omega L}{R} = \frac{X_L}{R}$
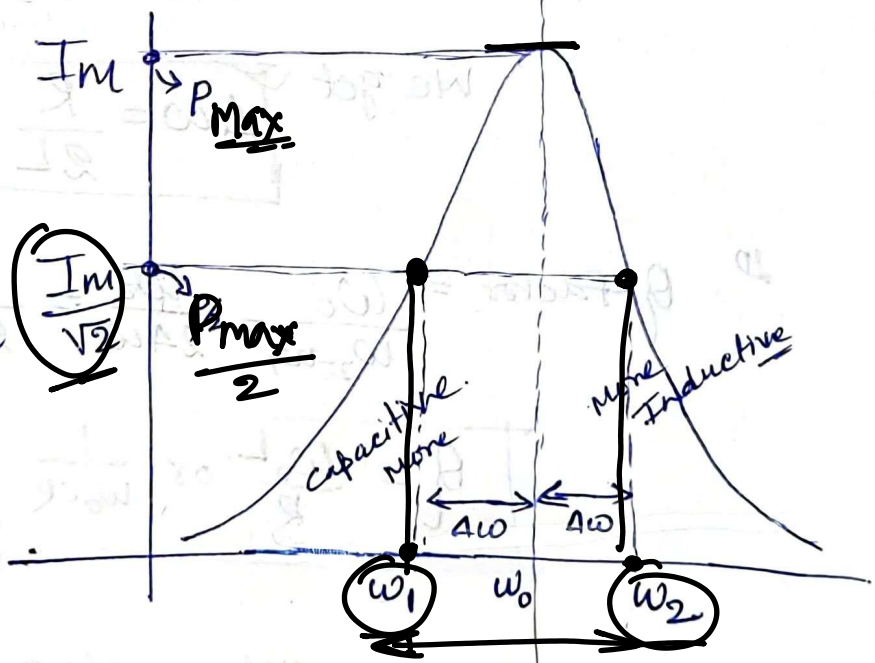
## Half Power Frequencies

Frequencies ( $f_1$  &  $f_2$ ) or  $\omega_1$  &  $\omega_2$  at which L-R-C ckt dissipates half power of the power in the resonance cond<sup>n</sup>



$\omega_1, \omega_2 =$  half power frequency

$Q = \frac{\omega_0}{2\Delta\omega}$

or  $Q = \frac{\omega_0}{\omega_2 - \omega_1}$

$\omega_2 - \omega_1 \rightarrow$  Band width

25

at  $\omega_1$  &  $\omega_2 \Rightarrow I_0 = \left( \frac{I_{\max}}{\sqrt{2}} \right) \rightarrow \frac{V_0}{R}$  Resonant current

$\Rightarrow \boxed{Z_0 = \sqrt{2} R}$  at  $\omega_1 = \omega_2$

So,  $\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} = \sqrt{2} R$

$\Rightarrow (\omega L - \frac{1}{\omega C}) = R^2 \quad \text{--- (1)}$

Now, As  $\omega_0 - \omega_1 = \omega_2 - \omega_0 = \Delta\omega$

$\Rightarrow \boxed{\omega_2 = \omega_0 + \Delta\omega}$  also  $\boxed{\omega_1 = \omega_0 - \Delta\omega}$

So eq<sup>n</sup> (1) will be satisfied at  $\omega = \omega_2$  &  $\omega_1$  also

then putting  $\omega = \omega_0 + \Delta\omega = \omega_2$

or  $\omega = \omega_0 - \Delta\omega = \omega_1$


We get  $\boxed{\Delta\omega = \frac{R}{2L}}$  &  $\omega_2 - \omega_1 = 2\Delta\omega$

Q-factor =  $\frac{\omega_0}{\omega_2 - \omega_1} = \frac{\omega_0}{2\Delta\omega} = \frac{\omega_0}{\cancel{2} \frac{R}{\cancel{2} L}}$

$\boxed{Q = \frac{\omega_0 L}{R} \text{ or } \frac{1}{\omega_0 C R}}$  } as  $\omega_0 L = \frac{1}{\omega_0 C}$   
} at resonance

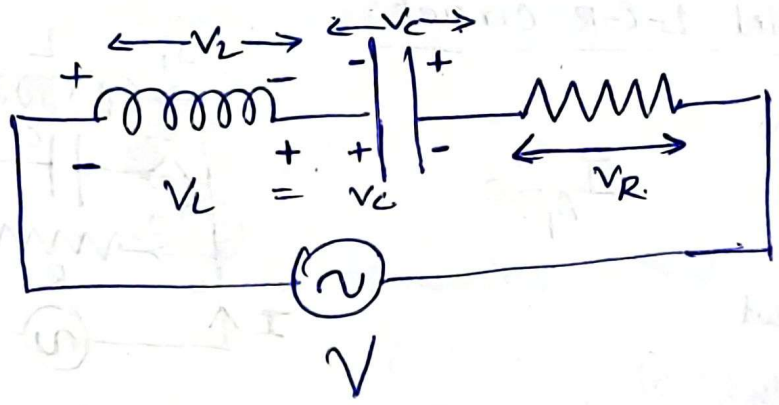$\checkmark$  L-C-R series resonance ckt is also called frequency selector ckt





at resonance  $V_L$  &  $V_C$  are not zero  
 only compensate effects of each other

~~Parallel LCR cu~~

Power developed in AC circuit

$P = VI$

in AC

Alternating voltage

$V = V_0 \sin \omega t$   
 $I = I_0 \sin(\omega t + \phi)$  ;  $I_0 = \frac{V_0}{Z}$

$P = VI = V_0 I_0 \sin \omega t \cdot \sin(\omega t + \phi)$

Avg. power  $\Rightarrow P_{av} = \frac{\int_0^T P dt}{T} = \frac{V_0 I_0}{2T} \int_0^T 2 \sin \omega t \cdot \sin(\omega t + \phi) dt$

or,  $P_{av} = \frac{V_0 I_0}{2T} \int_0^T \cos[\omega t - (\omega t + \phi)] dt$

$$\frac{2 \sin A \cdot \sin B}{2} = \frac{\cos(A-B) - \cos(A+B)}{2}$$

or,  $P_{av} = \frac{V_0 I_0}{2T} \int_0^T \cos \phi - \cos(2\omega t + \phi) dt$

or,  $P_{av} = \frac{V_0 I_0}{2T} \left[ \int_0^T \cos \phi dt - \int_0^T \cos(2\omega t + \phi) dt \right]$

→ Zero

or,  $P_{av} = \frac{V_0 I_0 \cos \phi}{2T} \int_0^T dt - \int_0^T \cos(2\omega t + \phi) dt$

or,  $P_{av} = \frac{V_0 I_0 \cos \phi}{2T} \cdot T = \frac{V_0 I_0 \cos \phi}{2}$

or,  $P_{AV} = \frac{V_0 I_0}{2} \cos \phi$

Also we can write

$P_{av} = \left(\frac{V_0}{\sqrt{2}}\right) \left(\frac{I_0}{\sqrt{2}}\right) \cos \phi$

$P_{av} = V_{rms} \cdot I_{rms} \cos \phi$

Phase diff between V & I

In case of pure resistance


$\phi = 0; P_{av} = V_{rms} I_{rms} \cos 0$

$\Rightarrow P_{av} = V_{rms} I_{rms}$

or  $P_{av} = I_{rms}^2 R$

or  $P_{av} = \frac{V_{rms}^2}{R}$

General case

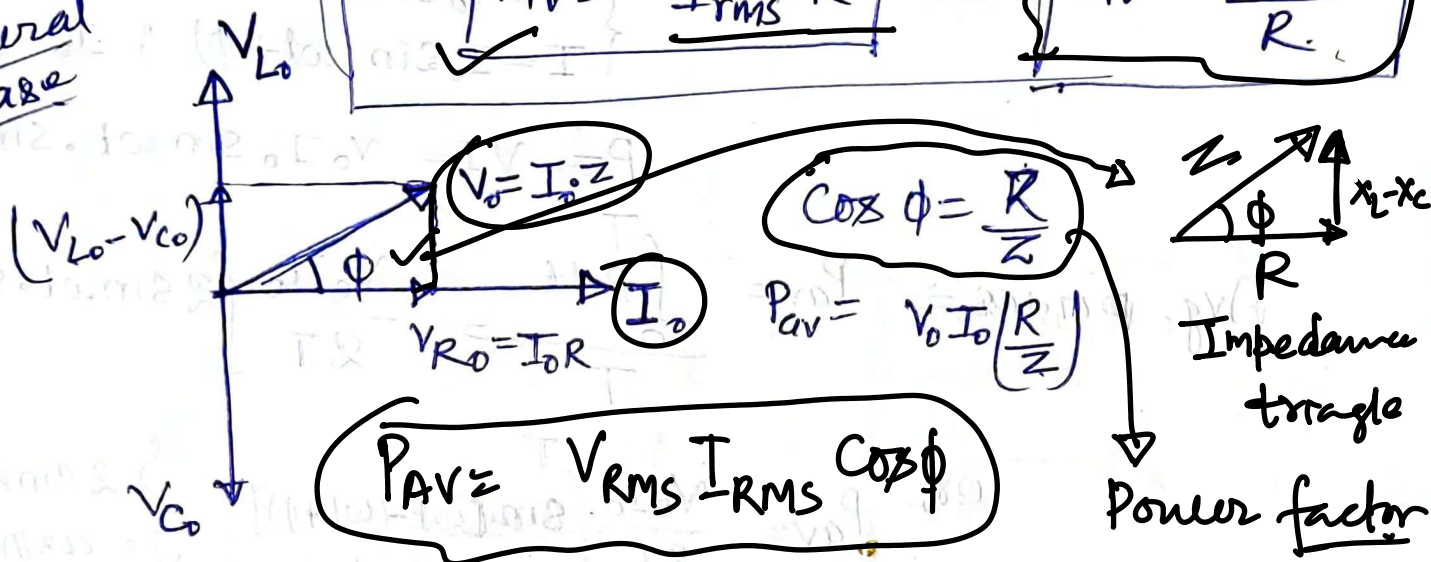


\* For Pure Inductor & Pure Capacitors

$\phi = 90^\circ \cos \phi = 0$

$P_{av} = 0$


Hence no power is consumed by Inductor & capacitor in a complete cycle.

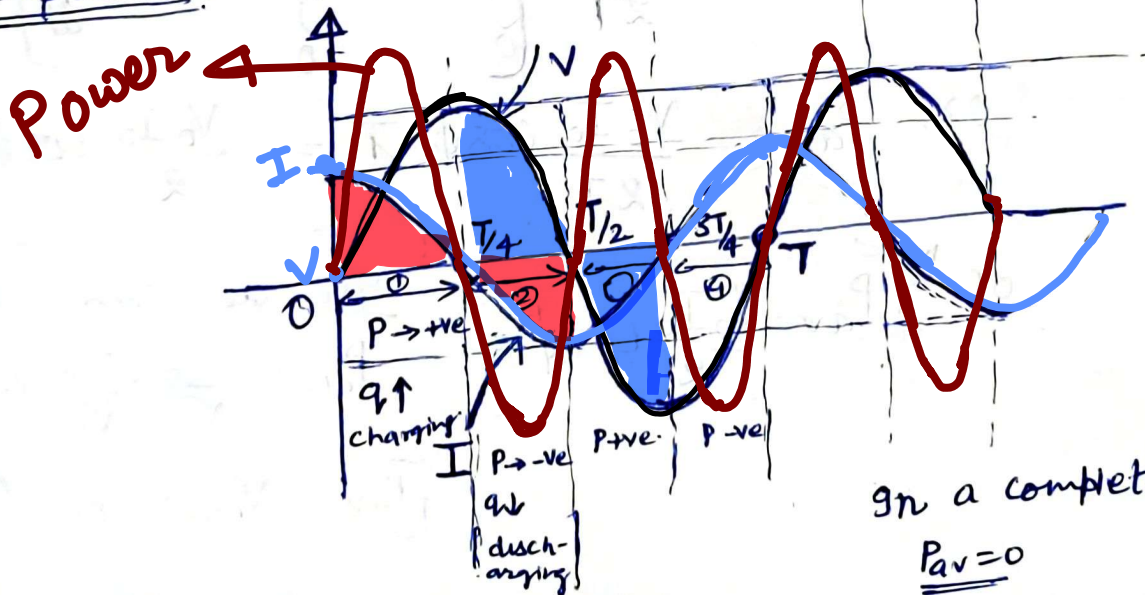\* Capacitor  $\rightarrow$  power consumed in AC ckt



Inductor Power consumed in AC ckt

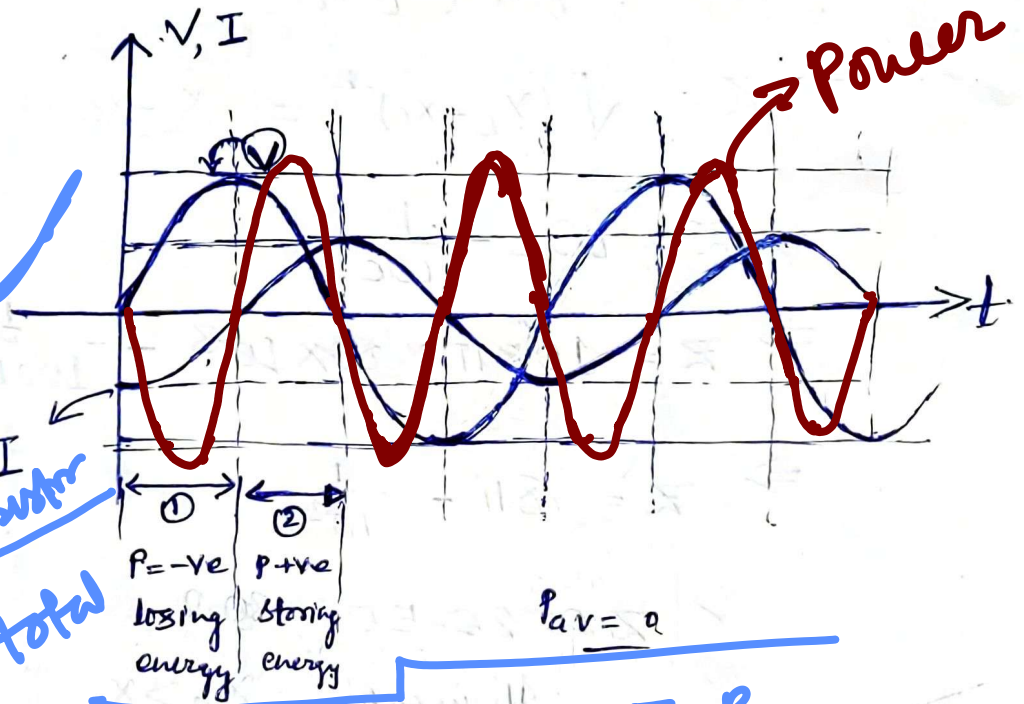Power Factor  
 $\cos \phi = \frac{R}{Z}$   
 $\cos \phi = \frac{P_{\text{resistor}}}{P_{\text{total}}}$



In resonance  $Z=R$

$\cos \phi = \frac{R}{R} = 1$

General situation

Power in LCR ckt


Power loss in resistor

$P_{\text{av}} = V_{\text{rms}} I_{\text{rms}} \cos \phi$

$\cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$

$P_{\text{av}} = \frac{I_{\text{rms}} \cdot V_{\text{rms}} R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$

Ex

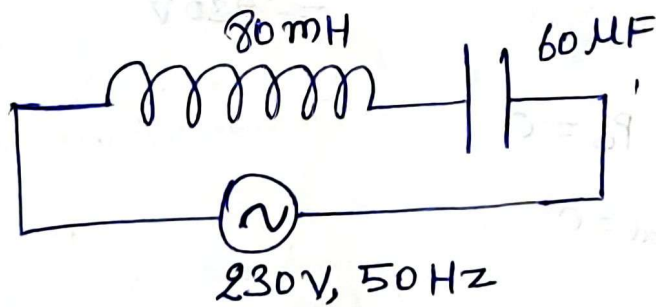

- (1)  $I_{\text{rms}}$ . (2)  $P_L, P_C$  (3)  $P_{\text{total}}$  (4)  $V_L \& V_C$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\Rightarrow Z = \sqrt{(X_L - X_C)^2} = \underline{X_L - X_C}$$

$$\Rightarrow Z = \omega L - \frac{1}{\omega C}$$

$$\Rightarrow Z = 100\pi \times 80 \times 10^{-3} - \frac{1}{100\pi \times 6 \times 10^{-6} \times 10^{-3}}$$

$$\Rightarrow Z = 8\pi - \frac{1}{10^3 \pi}$$

$$\Rightarrow Z \approx 25 - 55 = -30 \Omega$$

It means  $X_C > X_L$

Now For finding current. We take the  $Z$

$$I_{rms} = \frac{V_{rms}}{Z} = \frac{230}{30}$$

$$I_{rms} = 7.6 A$$

$$V_L = I \cdot X_L \approx 207 V$$


$$V_C = I \cdot X_C \approx 437 V$$

$$V_{net} = 437 - 207 \\ = 230 V$$

$$\star P_L = P_C = 0$$

$$\star P_{total} = 0$$

# TRANSFORMER

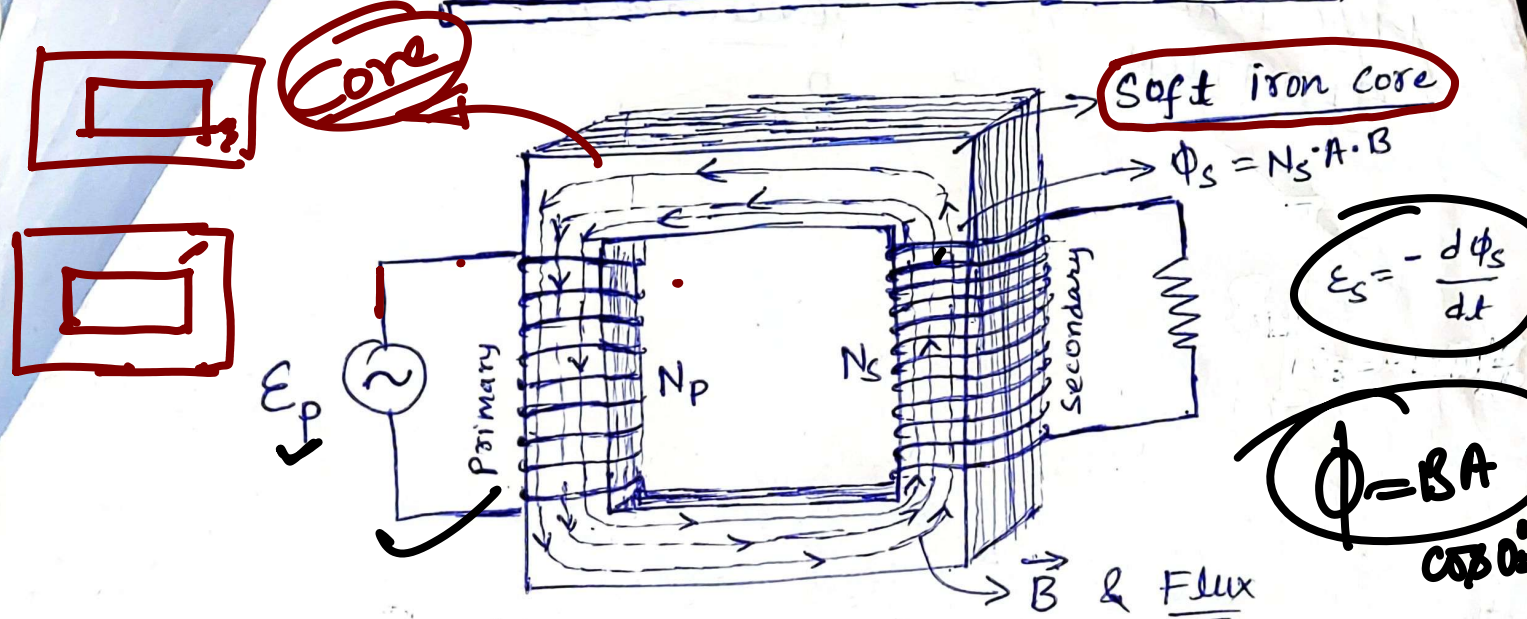

Transformer is a device which transfers voltage (or current) from one circuit to another circuit without any actual contact between the circuits and without changing the supplied power and frequency

$$E_p = - \frac{d\phi_p}{dt} = -N_p \cdot A \frac{dB}{dt}$$

$$E_p = -N_p \cdot A \frac{dB}{dt}$$

$$\frac{E_s}{E_p} = \frac{N_s A \frac{dB}{dt}}{N_p A \frac{dB}{dt}}$$

$$\Rightarrow \frac{E_s}{E_p} = \frac{N_s}{N_p}$$

$$\frac{N_s}{N_p} \Rightarrow \text{Turn ratio} = K$$

\*  $K > 1 \Rightarrow E_s > E_p$   
Step up TF

\*  $K < 1 \Rightarrow E_s < E_p$   
Step down TF

In an ideal transformer  
Power at primary coil  
= Power at secondary coil

$$\Rightarrow E_s I_s = E_p I_p$$

$$\Rightarrow \frac{I_s}{I_p} = \frac{E_p}{E_s} = \frac{N_p}{N_s} \quad \frac{I_p}{I_s} = \frac{N_s}{N_p}$$

# Efficiency of Transformer ( $\eta$ )

PRACTICAL SITUATION

$$\eta = \frac{P_{\text{secondary}}}{P_{\text{primary}}}$$



$$E_p = -N_p \frac{d\phi}{dt} = -N_p \cdot A \frac{dB}{dt}$$

$$E_s = -N_s \frac{d\phi}{dt} = -N_s \cdot A \frac{dB}{dt}$$

$$\frac{E_s}{E_p} = \frac{N_s \cdot A \frac{dB}{dt}}{N_p \cdot A \frac{dB}{dt}} = \frac{N_s}{N_p}$$

Transformer is a device which transfers voltage (and current) from one circuit to another circuit without any actual physical transfer of electrons and the results are without changing the applied power and frequency.

The ideal transformer has no losses.

