



**M 27059**

**Reg. No. : .....**

**Name : .....**

**IV Semester B.Tech. Degree (Reg./Sup./Imp. – Including – Part Time)**

**Examination, May 2015**

**(2007 Admn. Onwards)**

**PT2K6/2K6 EC 406 : DIGITAL ELECTRONICS**

**Time : 3 Hours**

**Max. Marks : 100**

1. Convert  $(3287.5100098)_{10}$  to octal.
2. Define a demultiplexer. Explain how to convert a decoder into a demultiplexer.
3. Give the truth-table for each flip-flop type :
  - a) RS
  - b) D
  - c) T
4. What is a ripple counter ?
5. Compare Mealy and Moore machines.
6. What are the two models of sequential circuits ? Explain.
7. Explain the characteristics of IIL logic family.
8. Mention the advantages of CMOS gate. **(8×5=40)**
9. a) Implement the following Boolean function using 8 : 1 MUX  
$$F(A, B, C, D) = \sum m(0, 2, 6, 10, 11, 12, 13) + d(3, 8, 14).$$
**15**

OR

  - b) What are the various type of ROM's ? Discuss their relative advantages and disadvantages. **15**

**P.T.O.**



10. a) Design MOD 5 synchronous counter using JK flip flops and implement it. **15**

OR

b) Explain the classification of shift registers. **15**

11. a) Explain counter design with state equation and state diagrams. **15**

OR

b) Design a synchronous decade counter to count in the following sequence :  
1, 0, 2, 3, 4, 8, 7, 6, 5. **15**

12. a) Draw the circuit of TTL NAND gate and explain its operation. Compare the  
TTL and ECL logic families. **15**

OR

b) Discuss the characteristics of RTL families. **15**

---