

## UNIT-I DC Circuits

**Voltage:**— The difference in potential energy of the charges called the potential difference. potential difference in electrical terminology is known as voltage. It is denoted by 'V'. Its units are volts.

$$V = \frac{W}{Q} \quad \text{or} \quad V = \frac{dW}{dQ}$$

Where,  $dW$  is the small change of energy  
 $dQ$  is the small change in charge.

Where,

energy ( $W$ ), is expressed in Joules (J).  
charge ( $Q$ ), is expressed in Coulombs (C).  
Voltage ( $V$ ), is expressed in Volts (V).

1) If 70J of energy is available for every 30C of charge, what is the voltage.

$$V = \frac{W}{Q} = \frac{70}{30} = 2.33V$$

**Current:**— It is defined as the rate of flow of electrons in a conductive or semiconductive material.

$$I = \frac{Q}{t} \quad \text{or} \quad i = \frac{dQ}{dt}$$

Where,  $I$  is the current  
 $Q$  is the charge of electrons &  
 $t$  is the time.

Where,  $dQ$  is the small change in current  
 $dt$  is the small change in time.

$$1 \text{ Coulomb} = 6.25 \times 10^{18} \text{ electrons.}$$

\*) Five Coulombs of charge flow past in a given point in a wire 2secs, How many amperes of current is flowing?

$$I = \frac{Q}{T} = \frac{5}{2} = 2.5A$$

**Power:-** It is the rate of change of energy & it is denoted p, Its units watts.

$$P = \frac{W}{T} \quad \text{or} \quad P = \frac{dW}{dt}$$

$$P = \frac{\text{energy}}{\text{Time}}$$

$$P = \frac{dW}{dt} = \frac{dW}{dq} \times \frac{dq}{dt}$$

$$P = Vi \quad \text{watts.}$$

Where,  $V = \frac{dW}{dq}$

$$i = \frac{dq}{dt}$$

**Energy:-** Energy is the capacity for doing work (or), energy is nothing but stored work.

\* Energy is measured in Joules (J).


1) What is the power in watts if energy equal to 50J is used in 2.5sec?

$$P = \frac{W}{T} = \frac{50}{2.5} = 20W$$

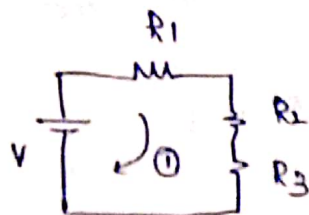**Electrical Networks:-**

\* Interconnection of two or more simple circuit elements (Voltage source, current, resistor, Inductor & capacitor) is called an electrical network.

\* In a network contains at least one closed path, it is called an electric circuit



∴ Here closed paths = 1

\* Broadly, network elements may be classified into 4 groups. They are

- 1) Active or passive
- 2) Unilateral or Bilateral
- 3) Linear or Non-linear
- 4) Lumped or Distributed

### 1) Active elements:-

\* Energy sources are active elements, capable of delivering power to some external devices.

Ex:- Ideal sources, voltage sources & current sources.

### passive Elements:-

\* The passive elements are, which are capable of receiving the power.

Ex:- Resistor (R), Inductor (L), & capacitor (C).

### 2) Bilateral :-

\* In the bilateral element, the voltage-current relation is same for current flowing in either direction.

Ex:- High conductivity materials.

### unilateral:-

\* A unilateral element has different relations b/w voltage & current for the two passive directions of current.

Ex:- Vacuum diodes, silicon diodes.

### 3) Linear Element:-

\* An element is said to be linear, if its voltage-current char is at all times a straight line through origin

(or)

\* Which satisfies the principle of superposition & principle of homogeneity is called linear element.

### Non-linear Element:-

\* An element which doesn't satisfy the superposition & homogeneity principle.

#### 4) Lumped Elements:-

\* The elements which are physically separable

Ex:- Resistor, inductor, capacitor, Transformer.

#### Distributed Elements:-

\* The elements which are not electrically separable.

Ex:- A transmission line which has distributed R, L & C along its length.

Ohm's law:- At constant temperature V is directly proportional to I

$$V \propto I$$

$$V = IR \quad ; \quad I = \frac{V}{R}$$

#### Electrical circuit Elements (R, L & C):-

##### R-parameter:-

\* The property of a material to restrict the flow of electrons is called resistance, It is denoted by R

          R            
          |||          

\* The unit of resistor is ohm's ( $\Omega$ ).

$$\boxed{V = IR} \quad ; \quad I = \frac{V}{R} \Rightarrow R = \frac{V}{I} \quad ; \quad \frac{1}{R} = G$$

Where G = conductance its units mho ( $\mathcal{M}$ ).

\* The power absorbed by the resistor is

$$P = VI$$

$$V = IR$$

$$P = I^2 R$$

(Or)

$$P = VI$$

$$I = \frac{V}{R}$$

$$P = \frac{V^2}{R}$$

\* Energy lost in a resistor is

$$W = \int_0^t p dt = Pt = I^2 R t$$

$$\boxed{W = I^2 R t \quad \text{or} \quad \frac{V^2}{R} t}$$

1) A 10Ω resistor is connected across a 10V battery. How much current flows through the resistor?

$$V = IR$$

$$I = \frac{V}{R} = \frac{10}{10} = 1.0A$$

Inductance parameters:-

\* Inductor stores the energy by associated form a current. It is denoted by "L". The unit of inductance is "Henry".



\* The wire of a certain length, when twisted in to a coil becomes a basic conductor. If current is made to pass through an inductor an electromagnetic field is formed

\* The current-voltage relation is given by

$$V = L \frac{di}{dt}$$

\* The power absorbed by inductor is

$$W_L = \int_0^t P dt = \int_0^t L i \frac{di}{dt} dt$$

$$W_L = \int_0^t L i di$$

$$W_L = \frac{1}{2} L i^2 \text{ Joules.}$$

1) The current in a 2H inductor varies at a rate of 2A/sec. Find the voltage across the inductor and energy stored in the magnetic field at 2A.

Given data,

$$L = 2H$$

$$\frac{di}{dt} = 2 A/sec$$

$$i = 2A$$

$$V = L \frac{di}{dt}$$

$$V = 2 \times 2 = 4 \text{ Volts}$$


$$W_L = \frac{1}{2} L i^2$$

$$W_L = \frac{1}{2} \times 2 \times 4$$

$$W_L = 4J$$
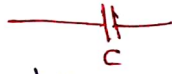
## Capacitance parameter:-

- \* Capacitor stores energy by associated form of voltage. It is denoted by "C", the unit of capacitor is Farad.



- \* Any two conducting surfaces separated by an insulating medium exhibit the property of a capacitor. The conducting surfaces are called electrodes. & insulating medium is called dielectric.

$$C = \frac{Q}{V} \quad \text{or} \quad C = \frac{dq}{dV}$$

$$i = \frac{dq}{dt}$$

$$dq = i dt \quad \text{--- (1)}$$

from above eq

$$Q = CV$$

$$dq = C dV \quad \text{--- (2)}$$

Sub (1) in (2)

$$i dt = C dV$$

$$i = C \frac{dV}{dt}$$

$$\Rightarrow V = \frac{1}{C} \int i dt$$

- \* The power absorbed by the capacitor is given by

$$P = vi$$

$$P = V C \frac{dV}{dt}$$

- \* The energy stored by the capacitor is

$$W_C = \int_0^t p dt$$

$$W_C = \int_0^t V C \frac{dV}{dt} \times dt$$

$$W_C = \int_0^t V C dV$$

$$W_C = \frac{1}{2} C V^2 \text{ Joules}$$

1) A capacitor having a capacitance  $2\mu\text{F}$  is charged to a voltage of  $1000\text{V}$ , calculate the stored energy in Joules? ④

$$W_c = \frac{1}{2} CV^2$$

$$W_c = \frac{1}{2} \times 2 \times 10^{-6} \times (1000)^2$$


$$W_c = 1\text{J}$$

Kirchhoff's laws:-

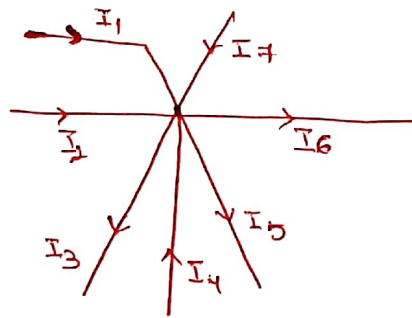- 1) Kirchhoff's current law (KCL)
- 2) Kirchhoff's Voltage law (KVL)

Kirchhoff's current law (KCL):-

\* It states that the sum of the current entering in to any point is equal to the sum of the current leaving that point.




From this diagram

entering currents = leaving currents

$$I_1 + I_2 + I_4 + I_7 = I_3 + I_5 + I_6$$

$$I_1 + I_2 - I_3 - I_4 - I_5 - I_6 + I_7 = 0$$

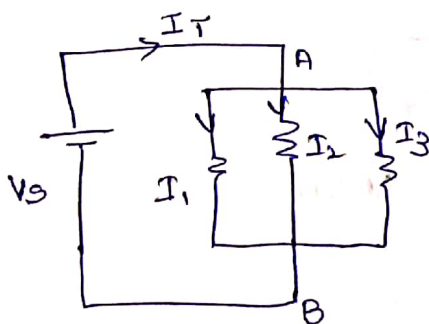
\* This means the algebraic sum of all the currents meeting at a junction is equal to "zero!"



∴ Entering current = leaving current

$$I_T = I_1 + I_2 + I_3$$

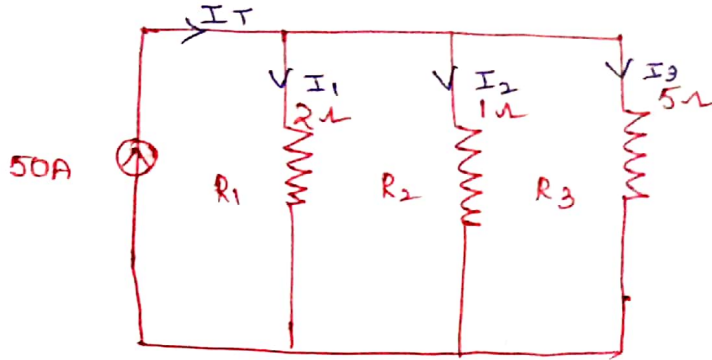1) Determine the currents in all resistors in the circuit shown in fig.



Sol:- \* In KCL voltages are same current is dividing

$$I_T = I_1 + I_2 + I_3$$

$$50 = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$50 = V \left[ \frac{1}{2} + \frac{1}{1} + \frac{1}{5} \right]$$

$$V = 29.41V$$

$$I_1 = \frac{V}{R_1} = \frac{29.41}{2} = 14.705A$$


$$I_2 = \frac{V}{R_2} = \frac{29.41}{1} = 29.41A$$

$$I_3 = \frac{V}{R_3} = \frac{29.41}{5} = 5.882A$$

$$I_T = I_1 + I_2 + I_3$$

$$50A \approx 49.95A$$

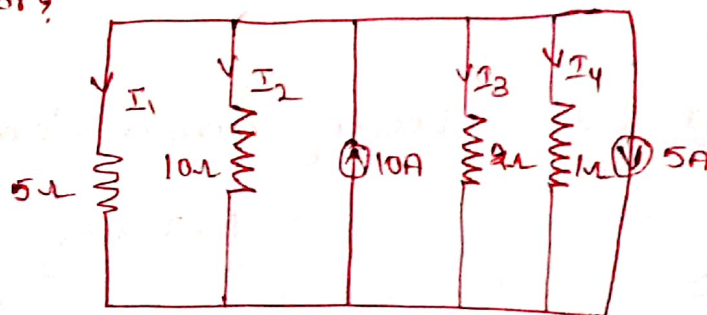2) For the circuit shown in fig. Find the current flows through 10Ω resistor?





$$I_T = I_1 + I_2 + I_3 + I_4$$


$$10 - 5 = \frac{V}{5} + \frac{V}{10} + \frac{V}{2} + \frac{V}{1}$$

$$V = 2.78V$$

$$I = \frac{V}{10} = \frac{2.78}{10}$$

$$I = 0.278A$$

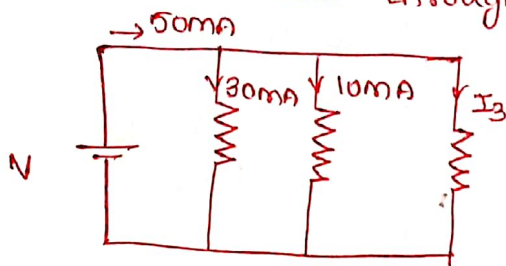3) Determine the current through resistance  $R_3$  in the circuit.




$$I_T = I_1 + I_2 + I_3$$

$$50 = 30 + 10 + I_3$$

$$I_3 = 10mA$$

Current Division Rule:—

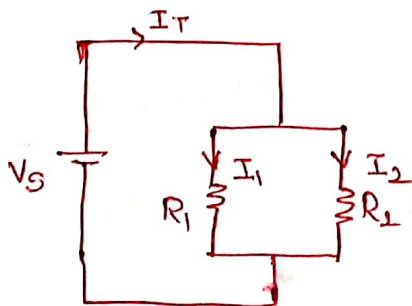- \* The parallel circuit act as a current divider.
- \* The total current entering in to the parallel branches is divided in to the branches current according to the resistance values.



Here, In KVL Voltage  $V_s$  same

$$I_1 = \frac{V_s}{R_1} \Rightarrow V_s = I_1 R_1 \quad \text{--- (1)}$$

$$I_2 = \frac{V_S}{R_2} \Rightarrow V_S = I_2 R_2 \quad \text{--- (2)}$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_T \text{ (or) } R_{\text{equ}} = \frac{R_1 R_2}{R_1 + R_2} \quad \text{--- (3)}$$

$$I_T = \frac{V_S}{R_T} = \frac{V_S (R_1 + R_2)}{R_1 R_2} \quad \text{--- (4)}$$

Sub (1) in (4)

$$I_T = \frac{I_1 R_1 (R_1 + R_2)}{R_1 R_2}$$


$$I_1 = I_T \cdot \frac{R_2}{R_1 + R_2} \quad \text{--- (5)}$$

Sub (2) in (4)

$$I_T = \frac{I_2 R_2 (R_1 + R_2)}{R_1 R_2}$$

$$I_2 = I_T \cdot \frac{R_1}{R_1 + R_2} \quad \text{--- (6)}$$

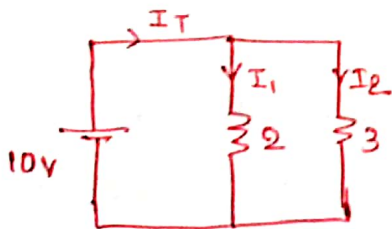1) Determine the current through each resistor in the ckt shown in fig:



$$I_T = \frac{V}{R_{\text{equ}}}$$

$$R_{\text{equ}} = (2 \parallel 3) = \frac{2 \times 3}{2 + 3} = \frac{6}{5} = 1.2$$

$$I_T = \frac{V}{R_{\text{equ}}} = \frac{10}{1.2} = 8.33 \text{ A}$$

$$I_1 = I_T \times \frac{3}{2 + 3}$$

$$I_1 = 8.33 \times \frac{3}{5} = 4.998$$


$$I_2 = I_T \times \frac{2}{2 + 3}$$

$$I_2 = 8.33 \times \frac{2}{5} = 3.332$$

$$I_T = I_1 + I_2$$

$$8.33 = 4.99 + 3.33 \Rightarrow 8.33 \approx 8.322$$

2)

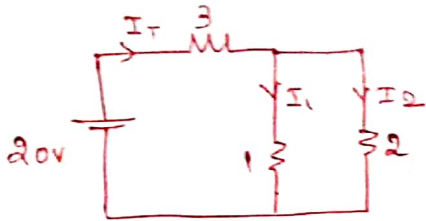


$$I_T = \frac{V}{R_{eq}}$$

$$R_{eq} = (1 \parallel 2) + 3 = \frac{1 \times 2}{1+2} + 3$$

$$R_{eq} = 3.66 \Omega$$

$$I_T = \frac{20}{3.66} = 5.46 A$$

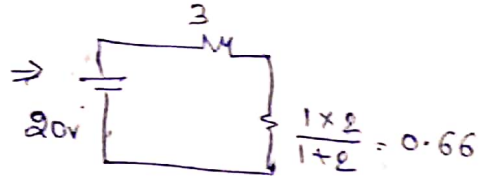

$$I_1 = I_T \times \frac{2}{2+1} = 5.46 \times \frac{2}{3} = 3.64 A$$


$$I_2 = I_T \times \frac{1}{1+2} = 5.46 \times \frac{1}{3} = 1.82 A$$

$$I_T = I_1 + I_2$$

$$5.46 \approx 3.64 + 1.82$$

$$5.46 \approx 5.46$$

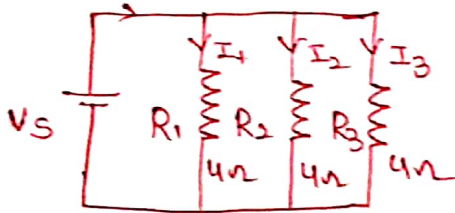3) Determine the current through each resistor in the ckt shown in fig 9. 12A



$$I_1 = I_T \times \frac{(R_2 \parallel R_3)}{R_1 + R_2 + R_3} \Rightarrow 12 \times \frac{(4 \times 4)}{4+4} = 4 A$$

$$I_2 = I_T \times \frac{(R_1 \parallel R_3)}{R_2 + (R_1 \parallel R_3)} = 12 \times \frac{(4 \times 4)}{4+4} = 4 A$$


$$I_3 = I_T \times \frac{(R_1 \parallel R_2)}{R_3 + (R_1 \parallel R_2)} = 12 \times \frac{(4 \times 4)}{4+4} = 4 A$$

$$I_T = I_1 + I_2 + I_3$$

$$12 A \approx 12 A$$
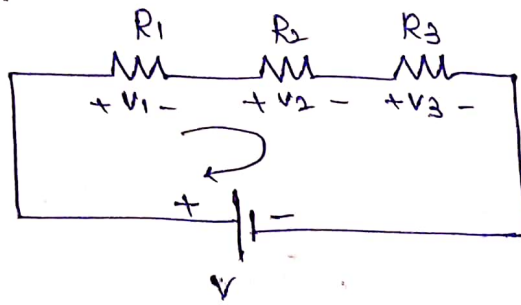
## Kirchhoff's Voltage Law:-

- \* Kirchhoff's Voltage Law states that the algebraic sum of the voltages around any closed path in a circuit is always zero.



Apply the KVL

$$V = V_1 + V_2 + V_3$$


$$V = IR_1 + IR_2 + IR_3$$

$$V = I[R_1 + R_2 + R_3]$$

$$I = \frac{V}{R_1 + R_2 + R_3}$$

- \* In KVL voltage is divided, current is same.
- \* In any element, the current always flows from higher potential to lower potential.

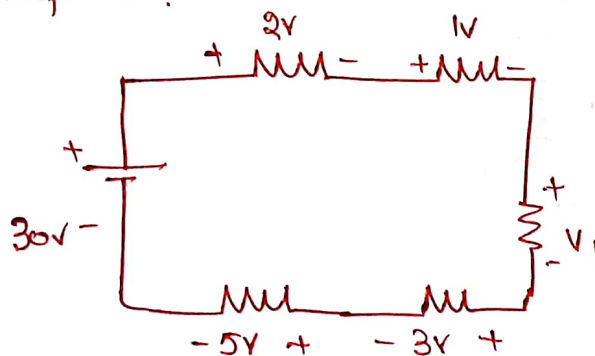
1) For the circuit shown in figure, determine the unknown voltage drop  $V_1$ ?



$$30 = 2 + 1 + V_1 + 3 + 5$$

$$V_1 = 19V$$

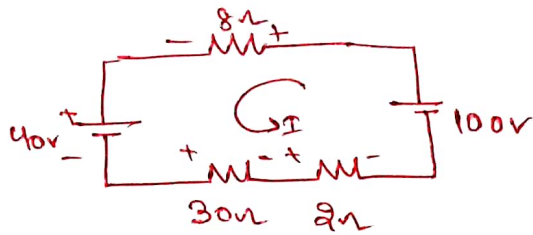2) In the circuit shown in fig. find the voltage at 30V?  $\oplus$



Apply KVL

$$100 = 8I + 40 + 30I + 2I$$


$$I = 1.5A$$

$$V_{30\Omega} = 30 \times 1.5$$

$$V = 45V$$


Voltage division rule:-

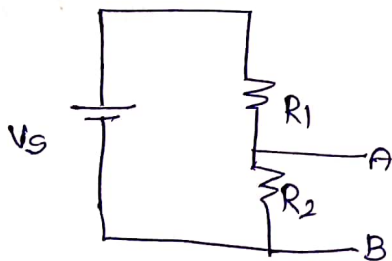- \* The series circuit act as a voltage divider
- \* Using this principle, different voltages can be obtained from a single source called voltage divider.



$$V_{AB} = V_s \times \frac{R_2}{R_1 + R_2}$$


1) What is the voltage across 10Ω?

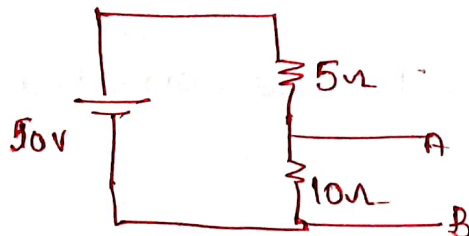

$$V_{AB} = 50 \times \frac{10}{10+5}$$


$$V_{AB} = \frac{100}{3} = 33.3V$$

2)

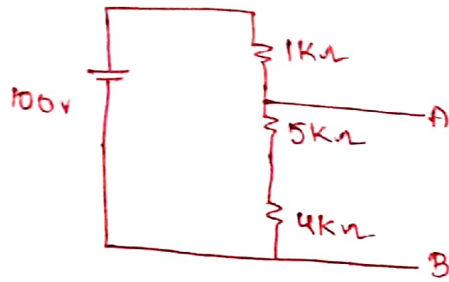

Voltage drop AB is  $V_{AB} = 100 \times \frac{5+4}{1+5+4} = 90\text{V}$


3)

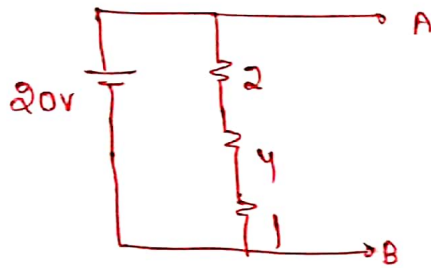

Voltage drop AB is  $V_{AB} = 20 \times \frac{2+4+1}{2+4+1} = 20 \times \frac{7}{7} = 20\text{V}$

Network Reduction Techniques (R, L & C Series and Parallel connection):-

1) Resistor in Series:-

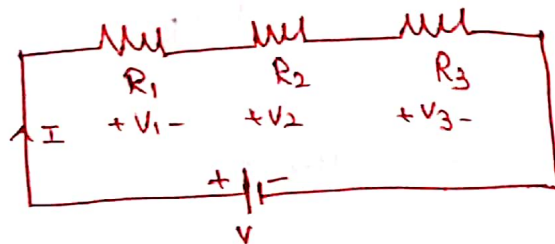

The Resistances  $R_1, R_2$  &  $R_3$  are connected in series

Apply the KVL

$$V = V_1 + V_2 + V_3$$


$$V = IR_1 + IR_2 + IR_3$$

$$V = I[R_1 + R_2 + R_3]$$

$$R_1 + R_2 + R_3 = R \text{ (or) } R_{eq}$$

$$R = R_1 + R_2 + R_3 + \dots + R_n$$

2) Resistors in parallel:-

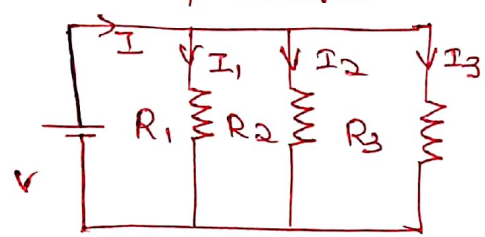

$$I = I_1 + I_2 + I_3$$


$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$I = V \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$\frac{1}{R_{equ}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$I = \frac{V}{R_{equ}}$$

3) Inductors in series:-

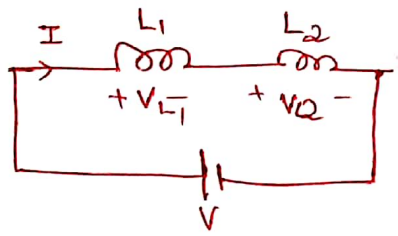

$$V = V_{L1} + V_{L2}$$

$$V = L \frac{di}{dt}$$

$$V = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$$


$$L \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$$

$$L \frac{di}{dt} = \frac{di}{dt} [L_1 + L_2]$$

$$L = L_1 + L_2$$

$$L_{equ} = L_1 + L_2 + \dots + L_n$$

4) Inductors in parallel:-

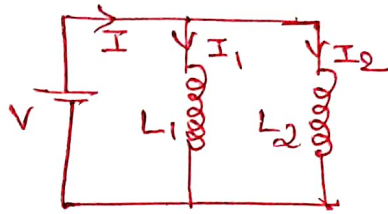

$$I = I_1 + I_2$$


$$V = L \frac{di}{dt} \Rightarrow I = \frac{1}{L} \int V dt$$

$$\frac{1}{L} \int V dt = \frac{1}{L_1} \int V dt + \frac{1}{L_2} \int V dt$$

$$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$L = \frac{L_1 L_2}{L_1 + L_2}$$

5) Capacitors in series:-

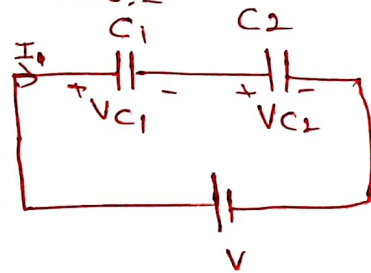

$$V = V_{c1} + V_{c2}$$

$$V = \frac{1}{C} \int i dt$$

$$\frac{1}{C} \int i dt = \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt$$


$$\frac{1}{C} \int i dt = \int i dt \left[ \frac{1}{C_1} + \frac{1}{C_2} \right]$$

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C = \frac{C_1 C_2}{C_1 + C_2}$$



6) capacitor in parallel:-

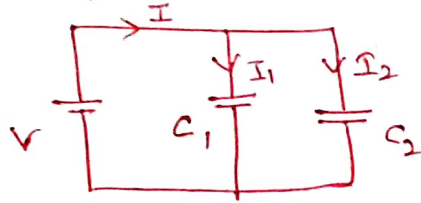

$$I = I_1 + I_2$$


$$i = c \frac{dv}{dt}$$

$$c \frac{dv}{dt} = c_1 \frac{dv}{dt} + c_2 \frac{dv}{dt}$$

$$c \frac{dv}{dt} = \frac{dv}{dt} [c_1 + c_2]$$

$$c = c_1 + c_2$$

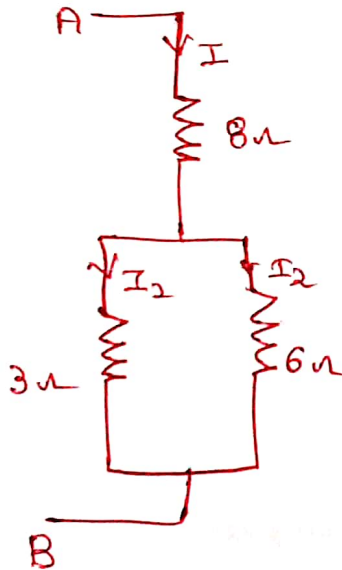1) What is the equivalent resistance b/w A & B of the circuit given below?




3 & 6 are in parallel  $\Rightarrow (3 \parallel 6) = \frac{3 \times 6}{3 + 6} = 2 \Omega$





$$\Rightarrow 8 + 2 = 10 \Omega$$


2)

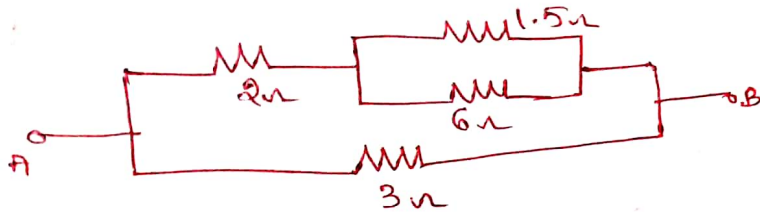


Here,  $(1.5 || 6) = \frac{1.5 \times 6}{1.5 + 6} = 1.2$

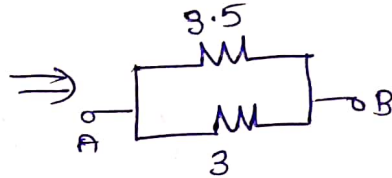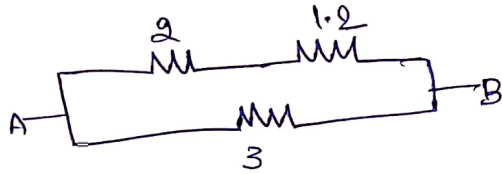


$(3.5 || 3) = \frac{3.5 \times 3}{3.5 + 3} = 1.5$

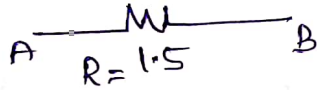

3)

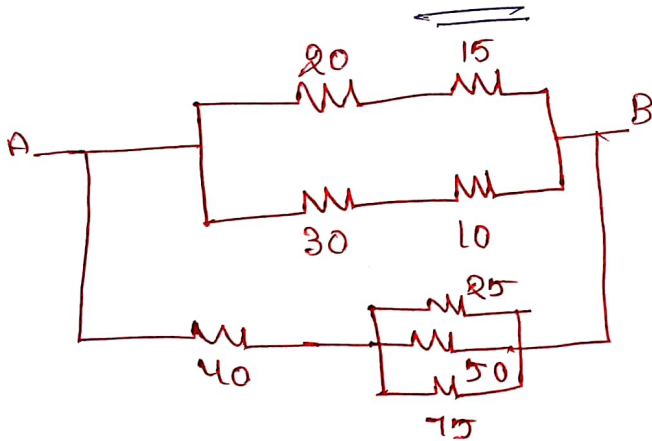

4) In fig, find R across x-y terminals?

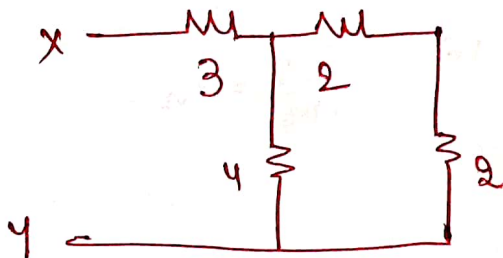

$((2+2) || 4) + 3 \Rightarrow (4 || 4) = \frac{4 \times 4}{4+4} + 3 = 5$