



Code No. : 5332/S

**FACULTY OF ENGINEERING**  
**B.E. 2/4 (ECE) I Semester (Suppl.) Examination, July 2012**  
**ELECTRONIC DEVICES**

Time : 3 Hours]

[Max. Marks : 75

**Note : Answer all questions from Part A.**

**Answer any five questions from Part B.**

**PART – A**

**(25 Marks)**

1. Explain the formation of depletion region in a PN junction. 2
2. Determine the forward bias voltage applied to a silicon diode to cause a forward current of 20 mA and reverse saturation current,  $I_0 = 20 \times 10^{-6}$  A at room temperature. 3
3. Compare LED and LCD. What are the advantages of LCD over LED ? 3
4. A diode with  $V_f = 0.7$  V is connected as a half wave rectifier. The load resistance is  $1 \text{ k}\Omega$  and the (rms) ac input is 22 V. Determine the peak out put voltage, the peak load current and diode PIV. 3
5. Draw the input output characteristics of CB configuration. 2
6. Write the equations for calculating  $R_B$  and  $R_C$  for a base bias circuit. 3
7. Draw the equivalent h-parameter model for common emitter configuration. 2
8. Compare V-I characteristics of SCR and TRIAC. 3
9. What are the advantages of FET over BJT ? 2
10. Define the pinch-off voltage, sketch the depletion region before and after pinch off. 2

**PART – B**

**(50 Marks)**

11. a) The diode current is 0.6 mA when the applied voltage is 400 mV, and 20 mA when the applied voltage is 500 mV. Determine  $\eta$ . Assume  $\frac{kT}{q} = 25$  mV. 5
- b) Explain zener voltage regulator also give its limitations. 5

12. a) Draw and explain the operation of full wave rectifier with capacitive filter. 5  
 b) Draw V-I characteristics of tunnel and varactor diode. 5
13. a) Explain the pnp transistor current components. 5  
 b) What is stability factor ? Derive the stability factor of a self bias circuit. 5
14. A voltage source of internal resistance  $R_s = 900 \Omega$  drives a CE amplifier using  $R_L = 2k\Omega$ . The CE h-parameters are  $h_{ie} = 1200\Omega$ ,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{fe} = 60$  and  $h_{oe} = 25 \mu A/V$ . Compute  $A_v$ ,  $R_i$ ,  $A_v$  and  $R_o$  using approximate analysis and exact analysis. 10
15. a) Draw and explain the V-I characteristics of UJT. 5  
 b) Write a short notes on CCD, bias stabilisation and compensation techniques. 5
16. a) A FET has a driven current of 4 mA. If  $I_{DSS} = 8 \text{ mA}$  and  $V_G s(\text{off}) = -6 \text{ V}$ . Find the values of  $V_{GS}$  and  $V_p$ . 5  
 b) Show that in a FET trans conductance  $g_m = \frac{2\sqrt{I_{DS} I_{DSS}}}{V_p}$ . 5
17. Write a short notes on : 10  
 a) Bridge rectifier  
 b) Thermal run way  
 c) CRO.