

Reg. No. :

Name :

VIII Semester B.Tech. Degree (Supplementary – Including Part Time)**Examination, October 2014****(2007 Admn. Onwards)****PT 2K6/2K6 EE 802 : INDUSTRIAL ELECTRIC DRIVES**

Time: 3 Hours

Max. Marks : 100

Instruction : Answer all questions.

1. a) Draw the block diagram of an electric drive.
 - b) What are the advantages of electric drives ?
 - c) A fully controlled converter is feeding a separately excited d. c. motor. In which quadrant of torque-speed plane can the motor be operated ? What are the requirements of such an operation ?
 - d) Explain current limit control.
 - e) What are the features of a PWM inverter fed induction motor drive ?
 - f) How induction motor speed control is achieved by using VSI ?
 - g) Draw and explain the block diagram of a CSI fed synchronous motor drive.
 - h) Explain the principle of variable frequency control of synchronous motor drive. (8×5=40)
- II. a) With the help of torque-speed coordinate explain the multiquadrant operation. 8
 - b) Brief the factors on which the choice of an electric drive depends. 7
- OR
- c) Explain the different classifications of load torque with examples.. 8
 - d) Describe the phase locked loop control. 7
- III. a) Draw and explain chopper control of a separately excited DC motor. Also derive the equation for armature current. 15
- OR
- b) Explain the closed loop armature control with field weakening for a DC motor. 15

P.T.O.



IV. a) Explain with neat sketch the working of CSI controlled induction motor drive. What are its features ? 15

OR

b) Explain the slip power recovery scheme of speed control scheme for a 3 phase induction motor. Draw the block schematics of the scheme and bring out the characteristics of the converter used. 15

V. a) Draw and explain the block diagram of a self controlled synchronous motor fed from a three phase inverter. 15

OR

b) With block diagram and flow chart explain the microprocessor based speed control of a synchronous motor. 15

(8x2=16)

II. a) With the help of torque-speed coordinate explain the multiphase operation. 8
b) Brief the factors on which the choice of an electric drive depends. 7

OR

c) Explain the different classifications of load torque with examples. 8
d) Describe the phase locked loop control. 7

III. a) Draw and explain chopper control of a separately excited DC motor. Also derive the equation for armature current. 15

OR

b) Explain the closed loop armature control with field weakening for a DC motor. 15

P.T.O.