

**EX-403****B.E. IV Semester**

Examination, December 2015

**Digital Electronics Logic Design - I****Time : Three Hours****Maximum Marks : 70**

- Note:** i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.  
 ii) All parts of each question are to be attempted at one place.  
 iii) All questions carry equal marks, out of which part A and B (Max. 50 words) carry 2 marks, part C (Max. 100 words) carry 3 marks, part D (Max. 400 words) carry 7 marks,  
 iv) Except numericals, Derivation, Design and Drawing etc.

1. a) i) Convert  $(2F.C4)_{16} = ( \quad )_8$   
 ii) Convert  $(762.013)_8 = ( \quad )_{16}$   
 b) The 7's complement of a certain octal number is 5264. Determine the binary and hexadecimal equivalents of that octal number.  
 c) Draw logic implementation of a EX-OR using NOR only.  
 d) Minimize the Boolean function  
 $f(A, B, C) = \sum_m (0, 1, 3, 5) + \sum_d (2, 7)$   
 using the mapping method is minimized SOP form.

OR

- c) A 4-bit ring counter and a 4-bit Johnson counter are in turn clocked by a 10 MHz clock signal. Determine the frequency and duty cycle of the output flip-flop in the two cases.  
 d) Design a 3-bit binary counter using TFF that has a repeated sequence of 6 states.  
 000-001-010-011-100-101-110. Give the state table, state diagram and logic diagram.

OR

Design a synchronous Mod-6 counter using JKFF.

5. a) Draw the static and dynamic RAM cells.  
 b) What is access time and cycle time of a memory.  
 c) Implement the function  
 $F_1 = \sum (0, 1, 2, 5, 7)$  and  
 $F_2 = \sum (1, 2, 4, 6)$   
 using PROM.  
 d) Describe with the help of a schematic diagram, the operation of a tracking-type A/D converter. Explain how it over comes the inherent disadvantage of a longer conversion time of the conventional counter-type A/D converter.

OR

Draw a PLA circuit to implement the function.

$$F_1 = \overline{AB} + \overline{AC}$$

$$F_2 = \overline{(AC + AB + BC)}$$

\*\*\*\*\*

Simplify the expression

$$\overline{AB + ABC + A(B + \overline{AB})}$$

and implement the simplified function using gates.

2. a) Design Half-adder using only NAND gates.
- b) Implement full adder using multiplexer.
- c) Design a three bit even parity generator.
- d) Draw and explain the BCD adder circuit.

OR

Implement the 3-variable Boolean function

$$F(A, B, C) = \overline{A}.C + A.\overline{B}.C + A.B.\overline{C}$$

Using i) 8 to 1 multiplexer and


ii) 4 to 1 multiplexer.

3. a) Draw the state diagram and characteristics equation of a D-FF.
- b) What is latch? What is the difference between latch and flip-flop?
- c) Realize T-flip-flop using SR flip-flop.
- d) Reduce the number of states in the following state table, and tabulate the reduced state table.

Present state	Next state		Output	
	X = 0	X = 1	X = 0	X = 1
a	f	b	0	0
b	d	c	0	0
c	f	e	0	0
d	g	a	1	0
e	d	c	0	0
f	f	b	1	1
g	g	h	0	1
h	g	a	1	0

OR

 Analyze the synchronous sequential logic circuit and derive the transition table and state diagram.



4. a) Differentiate Asynchronous and Modulus Counter.
- b) Determine the number of flip-flops required to construct.
  - i) a Mod-10 ring counter and
  - ii) a Mod-10 Johnson counter