SE-SEMII (ETRX) CRW) may 2017 2015/13 D. S.D. - I

133: 1ST HALF-13 (p)-JP

Con. 6453-13.

GS-6306

(3 Hours)

[Total Marks: 100

N.B. (1) Question No. 1 is compulsory.

- (2) Attempt any four, out of remaining six questions.
- 1. (a) Simplify $y = A + B\overline{C} + AB\overline{D} + ABCD$ using Boolean theorems and implement 20 it using only NAND gates.
 - (b) Differentiate between Combinational and Sequential circuits.
 - (c) Explain the term "Metastability", its causes and effects.
 - (d) Draw the circuit diagram of 2 I/P CMOS NAND gate.
- 2. (a) Explain Gray Codes. Design 3-bit binary to gray code convertor using 74151 IC's. 20
 - (b) Obtain Hamming code for "1010" data using odd parity? Why Hamming codes are called error correcting codes? Justify.
- 3. (a) Simplify $F = \sum m(1, 2, 4, 7, 11, 13) + d(9, 15)$ using K-map. Implement the function 20 using only NOR gates.
 - (b) Explain comparator IC 7485. Write its function table and design 12 bit comparator using three 7485 IC'S.
- 4. (a) Using Quine McCluskey Simplification Method: Simplify $F = \sum m (1, 3, 8, 9, 13, 15) + \sum d (10, 11)$.
 - (b) Briefly explain the classification of Logic families. Draw the diagram of 2 I/P TTL NAND gate and explain the advantages of Totem-pole output.
- 5. (a) Explain 4 bit Johnson counter using circuit diagram, state diagram and timing diagram. 20
 - (b) Draw circuit diagram of JKFF using NAND gates. Derive its characteristic equation and excitation table. What is a Race around condition in JKFF and give any two remidies to overcome it.
- 6. (a) Design Mod-11 synchrounous counter using TFF.
 - (b) A lawn sprinkling system is controlled automatically by certain combination of the following variables –

season (S = 1 if summer, 0 otherwise)

Temperature (T = 1 if high; O if low)

Atmospheric humidity (H = 1, if high; O if low)

Moisture content of the soil (M = 1, if high; O if low)

The sprinkler is turned ON under any of the following circumstances:

- (i) The moisture content is low in winter
- (ii) The temperature is high and moisture content is low in summer
- (iii) The temperature is high and humidity is high in summer
- (iv) The temperature is low and moisture content is low in summer
- (v) The temperature is high and humidity is low.
- 7. Write short notes on :—

20

20

20

- (a) Static and Dynamic Hazards
- (c) ECL Circuit for 2 I/P NOR Gate
- (b) Switch Debouncing Logic Circuit (d) Alphanumeric Codes.