


(3 Hours)

[Total Marks : 100]

- N.B. (1) Question No. 1 is compulsory.
 (2) Attempt any four from remaining questions.
 (3) Assume suitable data if necessary.

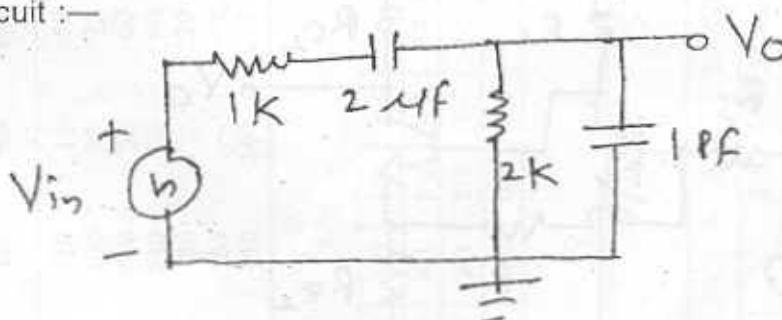1. Attempt any four questions from the following :— 20

- State and prove Barkhausen criterion for sustained oscillations.
- Write short notes on CASCODE amplifier.
- Explain the use of swamping resistor in Differential Amplifier.
- Explain design steps for Heat sinks.
- For the following circuit, determine corner frequencies and bandwidth of the circuit :—




2. Design two stage RC coupled CE amplifier to provide $A_v = 3000$, $V_o = 2.5 \text{ V}$ and $S = 8$. 20
 Determine R_{in} , R_o , V_o of the amplifier you have designed.

3. Design class AB power amplifier for following specifications :— 20

$P_o = 12 \text{ W}$, load resistance = 15 ohms, $V_{cc} = 12 \text{ V}$,
 Calculate circuit efficiency, draw DC load line.

Calculate power dissipation under zero signal conditions.

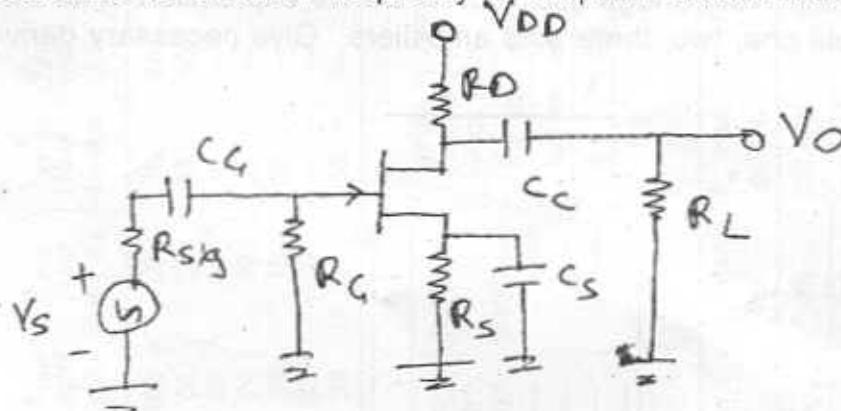4. (a) Determine lower cutoff frequency for amplifier shown in the figure :— 14



$$C_G = 0.01 \mu\text{F}$$

$$R_{sig} = 10 \text{ K}\Omega$$

$$I_{DSS} = 8 \text{ mA}$$

$$C_C = 0.5 \mu\text{F}$$

$$R_G = 1 \text{ M}\Omega$$

$$V_P = -4 \text{ V}$$

$$C_S = 2 \mu\text{F}$$

$$R_D = 4.7 \text{ K}\Omega$$

$$R_S = 1 \text{ K}\Omega$$


$$R_L = 2.2 \text{ K}\Omega$$

$$V_{DD} = 20 \text{ V}$$

$$\gamma_d = \infty$$

[TURN OVER]

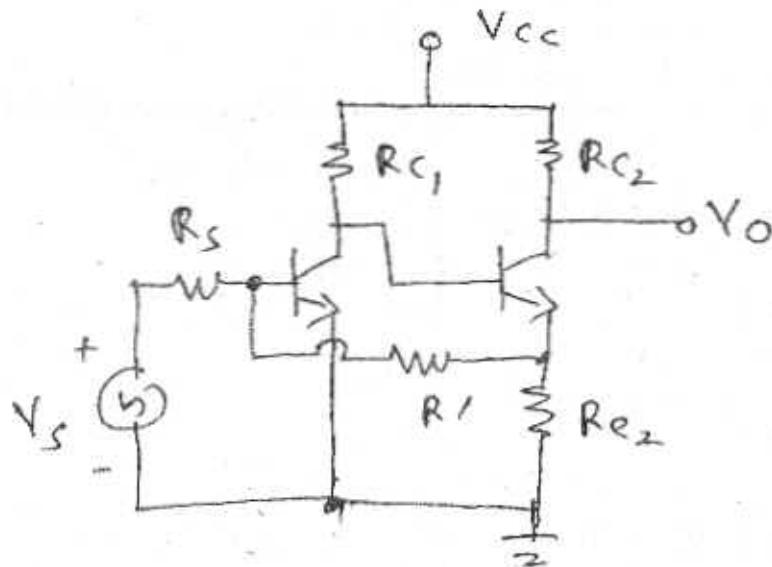- (b) Explain Miller effect in amplifiers. 6
5. For the amplifier shown in the figure determine :— 20
- A Feedback factor β , A_{Vf} , Identify feedback type
 - B R_{in} , R_{out}
 - C R_o , R_{of}
- $RC_1 = 3 \text{ K}$, $RC_2 = 500 \Omega$, $R' = R_s = 1.2 \text{ K}\Omega$
 $RC_2 = 50 \Omega$, $h_{ie} = 1.1 \text{ K}$, $h_{fe} = 50$, $V_{CC} = 15 \text{ V}$.



Draw Equivalent circuit without feedback.

6. (a) Derive the expression of differential gain, common mode gain, CMRR for dual input balanced output differential amplifier. 10
(b) Derive the expression of $f\beta$ and fT . 10
7. (a) State and explain Wein bridge oscillator ? Derive expression of its frequency. 10
(b) Explain in detail one, two, three pole amplifiers. Give necessary derivations. 10

Con. 2946-RK-1854-11.

DBEC DATA SHEET

R type		Pdmax @ 25°C Watts	Icmax @ 25°C Amps	Vce(max) Volts	Vceo d.c. Volts	Vceo (SUS) Volts	Vceo (SUS) Volts d.c.	Vceo Volts	Vceo Volts	Tj max °C	D.C. current	Current typ.	D.C. current max.	Small signal gain	Small signal gain min.	Signal typ.	Signal max.	hfe typ.	hfe max.	Vak max.	Derate above 25°C W/mW
NPN		113.5	15.0	1.1	100	60	70	90	7	200	20	50	70	15	50	120	1.8	1.5	0.7	3.5	0.4
		50.0	5.0	1.0	60	50	55	60	5	200	25	50	100	25	75	125	1.5	1.5	0.7	4.0	0.3
		30.0	4.0	1.0	50	40	—	—	8	150	30	50	110	33	60	115	1.2	4.0	0.5	3.5	0.05
		5.0	0.7	0.6	70	60	65	—	6	200	50	90	280	50	90	280	0.9	3.5	—	—	—
		0.25	0.1	0.25	50	45	50	—	6	125	115	180	220	125	220	260	0.9	—	—	—	—
		0.225	0.5	0.25	55	30	—	—	—	100	35	—	65	—	45	—	—	—	—	—	—
		0.25	0.1	0.25	50	45	50	—	6	125	200	290	450	240	330	500	0.9	—	—	—	—
JFET		Vds max.		Vgs max.		Pd max.		Tj max.		Ids		gms		-Vp Volts		rds		Derate above 25°C		θ_{je}	
(typical)		50	50	50	50	300	mW	175°C	2 mA	3000	μΩ	6	50 kΩ	2 mW/mW	6	50 kΩ	2 mW/mW	—	—	0.59°C/mW	0.59°C/mW
		30	30	30	30	300	mW	200°C	7 mA	5600	μΩ	2.5	50 kΩ	—	—	—	—	—	—	0.59°C/mW	0.59°C/mW