

SE / ETRX / III (REM) 24/5/2012

Con. 3892-12.

Digital System Design GN-5294

(3 Hours)

[Total Marks : 100]

- N.B. :** (1) Question No. 1 is **compulsory** and solve any **four** from remaining **six** questions.
 (2) In **all** attempt **five** questions.
 (3) **Figures** to the **right** indicate **full** marks.
 (4) Assume **data** if **necessary** and **justify** the **same**.

1. Answer the following :—

- | | |
|--|------------------------|
| (a) Construct Hamming code for BCD 0110. Use even parity. | 5 |
| (b) Explain the term 'metastability', its causes and effects. | 5 |
| (c) Define the following terms :— | 5 |
| (i) Fan out | (iv) Propagation delay |
| (ii) Noise margin | (v) Figure of merit. |
| iii) Fan in active pull up | |
| (d) Implement X-NOR operation using only minimum number of NAND gates. | 5 |

2. (a) Implement the following expression using IC 74138, 3:8 active low decoder and additional gates. 10

$$F(A,B,C,D) = \prod M \{ 0, 6, 7, 8, 12, 13, 14, 15 \}$$

- (b) Find reduced SOP form using K-maps, and implement using universal gates :— 10

$$(i) f(A, B, C, D) = \sum m \{ 2, 3, 6, 7, 8, 9, 12, 13 \} + d(4, 10, 14)$$

$$(ii) f(A, B, C, D) = \prod M \{ 0, 6, 7, 8, 12, 13, 14, 15 \}$$

3. (a) Simplify the following using Quine Mc-Clusky method. 10

$$f(A, B, C, D, E) = \sum m \{ 0, 1, 9, 15, 24, 29, 30 \} + d(3, 11, 31)$$

- (b) Implement the following using single IC 74151 and some gates. 10

$$(i) f_1 = \sum m \{ 1, 2, 4, 7, 10, 13, 14 \}$$

$$(ii) f_2 = \sum m \{ 1, 4, 5, 7, 8, 12, 13, 15 \}$$

4. (a) Determine whether any static 0 or static 1 hazards exist in the following Boolean expression. Identify where the hazards are and what must be done to avoid them. 10

$$f(A,B,C,D) = \sum m \{ 5, 7, 8, 9, 10, 11, 13, 15 \}$$

- (b) Explain and draw asynchronous counter for the following :— 10

-4- 5-6-7-8-9-10-11-12-13-14-15-

5. (a) Design and explain one digit BCD adder using IC 7483 and NAND gates. 10

- (b) Write short notes on : 10

(i) ALU (ii) programmable logic unit

6. (a) Construct twisted ring counter using IC 74194 and draw the output wave-form. 10

- (b) Draw and explain a 9 bit even parity checker using IC 74180. 10

7. (a) Implement binary to BCD converter using universal gates. 10

- (b) Explain the following :— 10

(i) Self complementing codes, with example.

(ii) The term 'noise margin' and its value for TTL and CMOS families.