



M 26234

Reg. No. :

Name :

V Semester B.Tech. Degree (Reg./Sup./Imp. – Including Part Time)
Examination, November 2014
(2007 Admn. Onwards)

PT2K6/2K6 EC/AEI 505 : LINEAR INTEGRATED CIRCUITS

Time : 3 Hours

Max. Marks : 100

- I. a) Draw the block level diagram of an op-amp and explain each block. **5**
b) Define unity gain band width. Also explain the significance of unity gain band width. **5**
c) List out typical CMOS op-amp parameters. **5**
d) Design a non inverting amplifier with gain = 11. **5**
e) Explain the advantages of differential amplifier over single input amplifier. **5**
f) Draw and explain the working of voltage to current converter with proper derivation ? **5**
g) What is filter ? Draw the ideal characteristics of LPF, HPF, BPF and BRFF. **5**
h) Explain the difference between active and passive filter. **5**
- II. a) Explain and derive the equation for :
1) Slew rate
2) CMRR
3) PSRR. **15**
- OR
- b) Define input bias current ? Derive the equation for output offset voltage due to input bias current. Also explain how to nullify the effect of input bias current. **15**
- III. a) Explain the operation of cross coupled pair differential amplifier with neat circuit diagram. Also listout the advantages of cross coupled pair differential amplifier. **15**
- OR
- b) Explain the working of wide swing current differential amplifier with neat circuit diagram. **15**

P.T.O.



- IV. a) Define oscillator ? Explain the two conditions required for sustained oscillation ?
Explain wein bridge oscillator with neat circuit diagram and derive the equation
for f_o and R_F/R_I . 15
- OR
- b) Explain the working of Astable multivibrator circuit using op-amp with neat
circuit diagram and derive the equation for frequency, f . 15
- V. a) Draw the circuit diagram of a second order Butterworth sallenkey configuration
high pass filter and derive the equation for transfer function, $H(S)$. 15
- OR
- b) i) Explain the concept of inductance simulation using Antonious gyrator. 8
- ii) Design a 2nd order Butterworth high pass filter with cut-off frequency 2KHz. 7
-