



1. (1) Question No. 1 is compulsory.

(2) From remaining six questions solve any four questions.


(3) Assume suitable additional data if required.

(4) Figures to the right indicate full marks.

  1. (a) Design a circuit to implement the following function using a Type-1 MUX design :— 8  
 $F(A, B, C, D, E) = \sum m(0, 5, 7, 11, 15, 16, 18, 25, 29)$ .
- (b) For the logic diagram shown in the figure below carry out the detailed analysis (including state diagram). X is the input signal and Z is output signal. 12



 2. (a) Explain the path sensitization method of fault detection and location. What are the advantages and disadvantages of the path sensitization method? Use this method for the following circuit :— 10




- (b) Implement the following sets of functions using a decoder and some gates. Design the logic for minimum chip count. 10

$$F_1(A, B, C) = \sum m(0, 1, 2)$$

$$F_2(A, B, C) = \sum m(1, 2, 3, 4, 5, 7)$$

$$F_3(A, B, C) = \sum m(2, 3, 5, 7).$$

 
3. (a) The incoming serial data is to be detected in overlapping mode for the sequence ..... 10110 ..... 12  
 The output Z is asserted high when the sequence is received. Draw the state diagram and realize the logic using D-flip-flops and gates.
- (b) For the circuit given below determine the number of logic hazards. What product terms are necessary to eliminate these logic hazards? Write the logic hazard free function for the circuit. 8




[ TURN OVER



 4. (a) Design a circuit to implement a BCD to 2421 code converter using PAL. The signal list is  $F_3, F_2, F_1, F_0, I_3, I_2, I_1, I_0$  8  
 (b) Minimize the state diagram in **figure** given below and implement the logic using D-flip-flops 12 and gates.





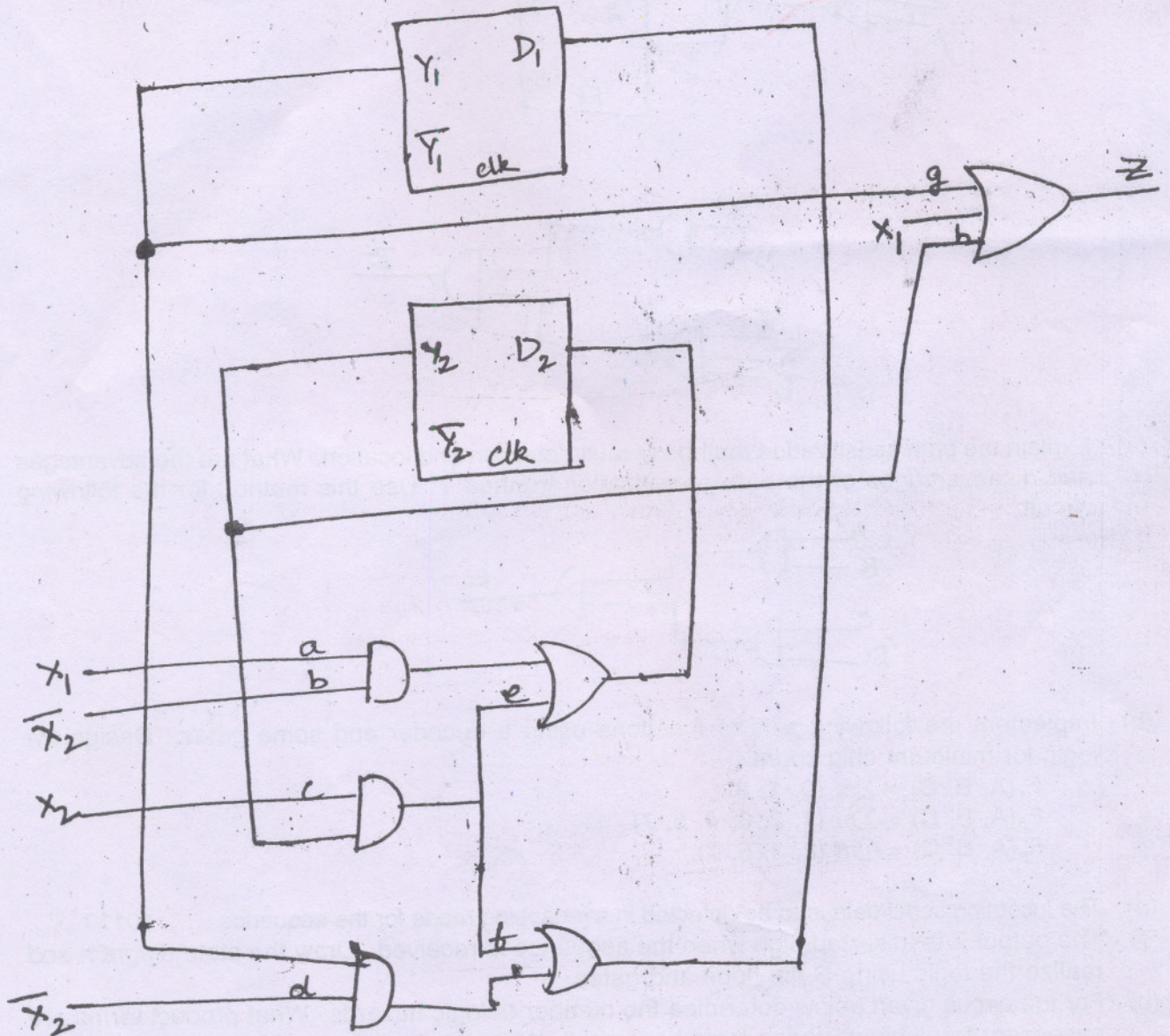5. Consider the following faults of the D F/F circuit of **figure**  $a_0, b_0, c_0, d_0, e_1, f_1, g_1, h_1$  where  $a, b, \dots, h$  denote the location of the faults in the circuit and the subscript 0 and 1 denote s-a-0 and s-a-1 faults respectively — 20  
 (a) Determine the undetectable faults  
 (b) Determine the indistinguishable faults  
 (c) Find the optimum test sequence to detect these faults






  6. State diagram for a sequential network is shown below. Realise the network using IC 745163 and PLA. Use the order  $Q_D, Q_C, Q_B, Q_A$  for the state variables. Operation of 745163 is also shown :-



Clear	Load	PT	$Q_D$	$Q_C$	$Q_B$	$Q_A$	
0	X	X	0	0	0	0	(Clear)
1	0	X	$D_D$	$D_C$	$D_B$	$D_A$	(Load)
1	1	0	$Q_D$	$Q_C$	$Q_B$	$Q_A$	(No change)
1	1	1	Present State +1				(Increment count)

 7. Two four bit numbers are loaded in two shift registers X and Y which are part of a digital system. It is desired to design this system which will work as a four bit serial adder. The input-output signals are shown in the Schematic diagram.



On receiving 'start' it will begin the serial operation of adding the numbers in the registers X and Y. After the operation is over the sum will be stored in the register X, the carry will be available as an output and it will output 'Done'.

Make a functional partition diagram of the system and MDS diagram of its controller. Design the controller.