

USN

--	--	--	--	--	--	--	--	--	--



06CS32

Third Semester B.E. Degree Examination, Dec.09/Jan.10

Electronic Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1
 - a. With a neat diagram and waveforms, explain the working of a positive clamper with respect to the stiff clamper condition. (08 Marks)
 - b. An LED is used in the indicator circuit for the a.c. power line of 230V AC with 50Hz frequency. The circuit consists of a capacitor of 0.68μf. Calculate the capacitive reactance and average LED current. (04 Marks)
 - c. Explain with relevant diagrams, the principle of operation of a varactor diode. (08 Marks)
- 2
 - a. Explain with a neat circuit diagram and a.c. equivalent circuit, the working of base biased amplifier. (08 Marks)
 - b. Sketch the output waveform for the clipper circuit of FigQ2(b) shown below. Assume silicon diode and obtain the peak magnitude of the output waveform.

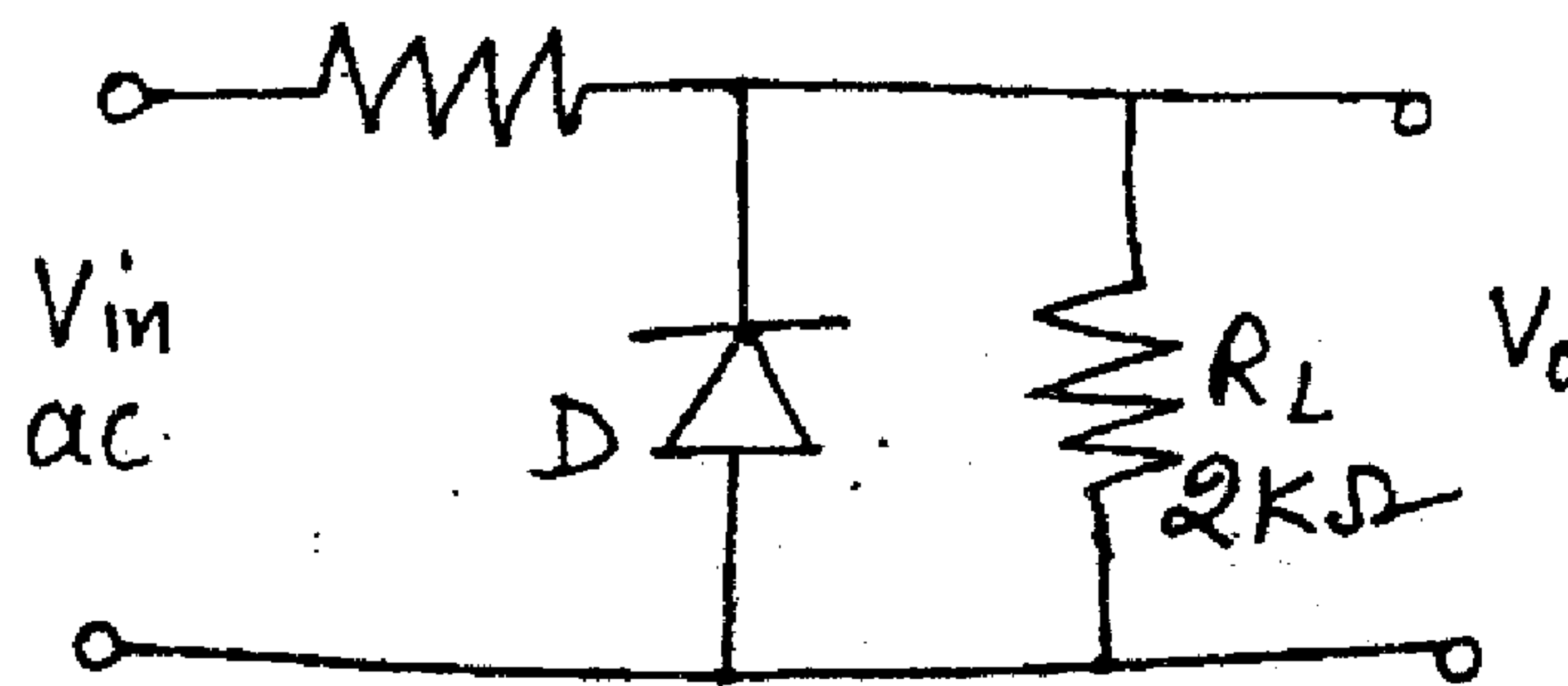
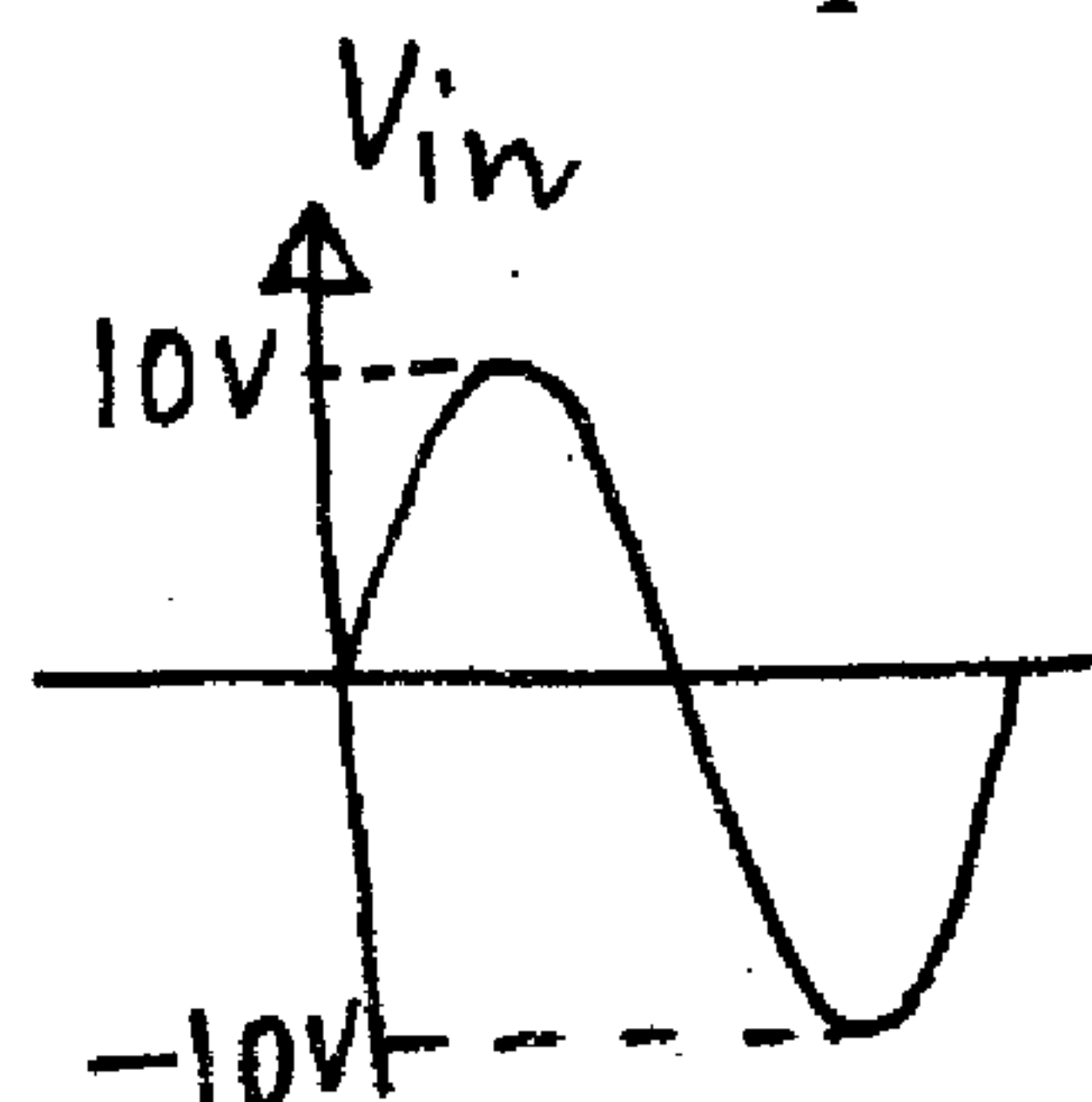


Fig.Q2(b)

(06 Marks)

- c. Find the voltage gain and output voltage across the load resistor for the given circuit of FigQ2(c).

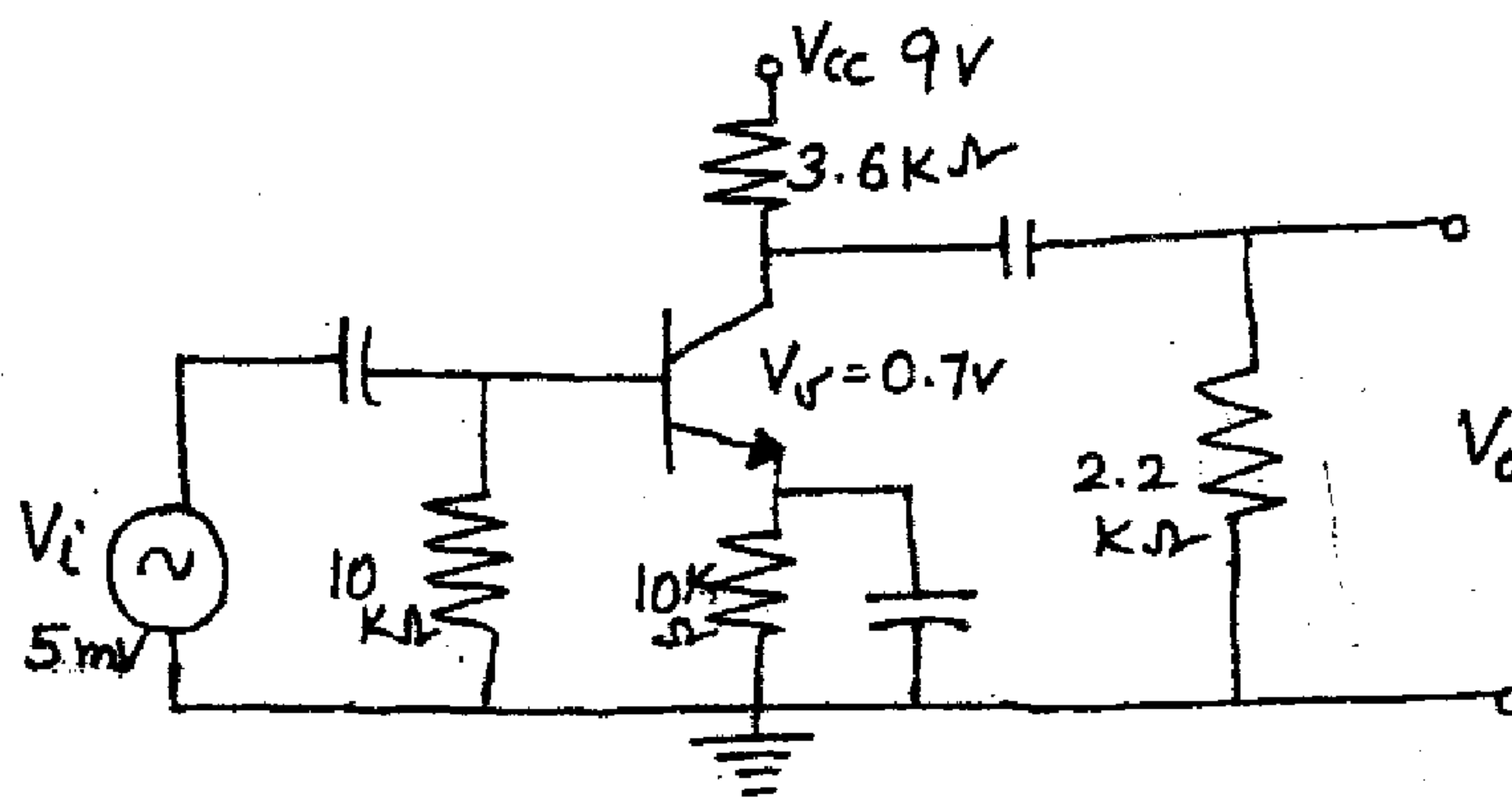


Fig.Q2(c)

(06 Marks)

- 3
 - a. Explain the working of a swamped amplifier with a neat circuit diagram. Derive the expression for voltage gain. (08 Marks)
 - b. Draw the cascaded CE and CC stages of amplifier. Explain. (06 Marks)
 - c. Derive an expression for an output voltage for a series feedback type regulator. (06 Marks)
- 4
 - a. Explain the principal of operation of class B push-pull amplifier with a neat circuit diagram and relevant waveforms. (08 Marks)
 - b. In a class B amplifier, $V_{CE(min)} = 1$ volt, supply voltage $V_{CC} = 18$ volts. Calculate the collector circuit efficiency. (04 Marks)
 - c. What is digital switching? Explain in detail passive load switching and active load switching. (08 Marks)

Important Note: 1. On completing your answer, compulsorily draw diagonal cross lines on remaining blank pages. 2. Any revealing of identification, appeal to evaluator and/or Equations written, eg, 42+8=50, will be treated as malpractice.

PART -B

- 5 a. What is impedance matching? Explain. (04 Marks)
b. Explain briefly decibel power gain and decibel voltage gain. (06 Marks)
c. Explain ideal closed loop voltage gain, gain stability, closed loop input impedance, closed loop output impedance and non linear distortion, with respect to VCVS amplifier. (10 Marks)
- 6 a. With relevant details, explain VCIS amplifier. (06 Marks)
b. Write a note on comparators with nonzero references. (06 Marks)
c. With a neat circuit diagram and waveforms, explain the sine wave to rectangular converter, using OP-AMP. (08 Marks)
- 7 a. Explain the principle of relaxation oscillator to generate rectangular output. Draw a neat circuit diagram and waveform. (08 Marks)
b. Explain with a neat connection diagram and waveforms, how IC555 timer is used as a stable multivibrator. (08 Marks)
c. What do you know about phase locked loops? Explain. (04 Marks)
- 8 Write an explanatory note on :
a. Opto electronic devices
b. Load lines in power amplifiers
c. Voltage controlled oscillator
d. Switching regulators. (20 Marks)
