

**(DEE 321)**

**B.Tech. DEGREE EXAMINATION, MAY - 2015**

**(Examination at the end of Third Year)**

**ELECTRICALS AND ELECTRONICS**

**Paper - I : Linear IC'S & Applications**

**Time : 3 Hours**

**Maximum Marks : 75**

**Answer question No. 1 compulsory**

**(15)**

**Answer one question from each unit**

**(4 × 15 = 60)**

- 1) a) Define slew rate.
- b) Define CMRR.
- c) Explain thermal drift.
- d) Explain PSRR.
- e) Define clamper.
- f) What is Band stop filter?
- g) Define voltage regulator.
- h) What is A/D converter?
- i) Define clipper?
- j) Explain principle of oscillator.
- k) What is negative feed back?
- l) What is wide band filter?
- m) Draw 555 timer IC.
- n) Define peak detector.
- o) Define precision rectifier?

## UNIT – I

- 2) a) Design a differentiator an input signal that varies in frequency from 10Hz to about 1kHz. If a sine wave of 1v peak at 1000Hz is applied to this differentiator. Draw output wave forms.
- b) Explain how op-amp can be used as summing amplifier.

OR

- 3) Explain
- a) Block diagram of operational amplifier.
- b) Current to voltage converter.

## UNIT - II

- 4) a) Draw the square wave generator using op-amp and derive the expression for frequency of oscillations.
- b) Explain Schmit trigger.

OR

- 5) a) Explain triangular wave generator.
- b) List the conditions in all the three types of oscillators namely, RC phase shift, Wien bridge and quadrature oscillators.

## UNIT - III

- 6) a) Describe weighted resistor DAC and what are the draw back of it?
- b) Calculate the no. of bits required to represent a full scale voltage of 10v with resolution of 5mv.

OR

- 7) a) Discuss about R-2R DAC.
- b) Explain about dual slope DAC.

## UNIT - IV

- 8) a) Draw the wide band reject filter circuit and also the frequency response of it.
- b) Draw the schematic diagram of an all pass filter and determine phase shift between the i/p and o/p at  $f = 2\text{kHz}$ .

OR

- 9) a) What are the applications of 565 PLL.
- b) Design second order low pass filter at a high cut off frequency of 1kHz

φφφ