

B.E./B.Tech.(Full Time) DEGREE END SEMESTER EXAMINATION , APRIL/MAY 2011

Electronics and Communication Engineering

Second Semester

EC182 Circuit Analysis

(Regulation - 2004)

Time: Three hours

Maximum ; 100 Marks


Answer all questions

Part- A (10x2=20 marks)

1. A resistive load consumes 20W power while 200V source is connected across its terminals. Then, find the resistance and current flow through the load.
2. State: Kirchoff's current law.
3. If a source has internal impedance $2+j3$ Ohms. Then, find the value of the load which can derive the maximum power from the source.
4. Write the superposition principle.
5. Write the phase relationship between current and voltage while a voltage source is connected to an inductor
6. Relate instantaneous power and average power.
7. Write the formula for resonance frequency and Q-factor of a series RLC circuit.
8. What is time constant of RC circuit? How is it measured?
9. What is branch and node in a tree?
10. What is mutual inductance?


Part-B (5x16=80)

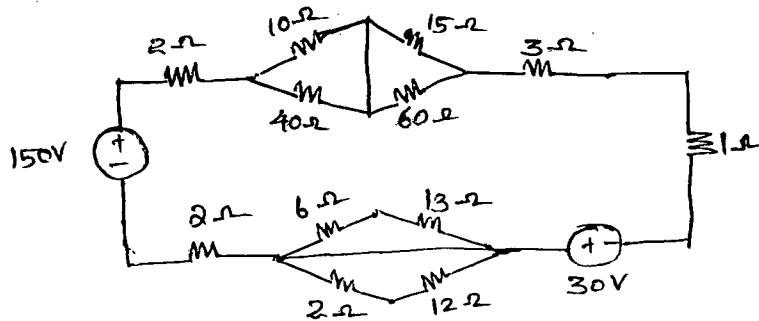11. a) Use both resistance and source combinations, as well as current division in the circuit Q11.a, to find
 - (i) Current through each element in the circuit (5)
 - (ii) Voltage across each element in the circuit (5)
 - (iii) the power absorbed by the 1Ω , 10Ω and 13Ω resistors (6)



Q11.a

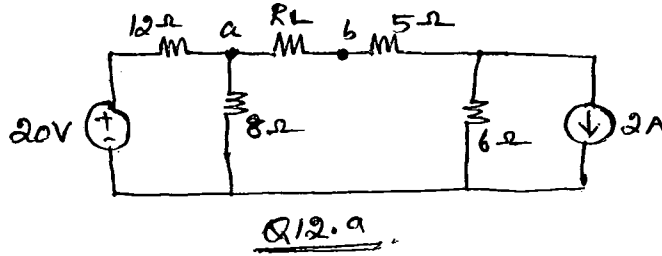
12. a) (i) Find the Thevenin's equivalent circuit for the circuit shown in Q12.a across the terminals a and b. (12)



- (ii) Find the value of R_L in the above circuit for which the R_L will receive maximum power. (4)


OR

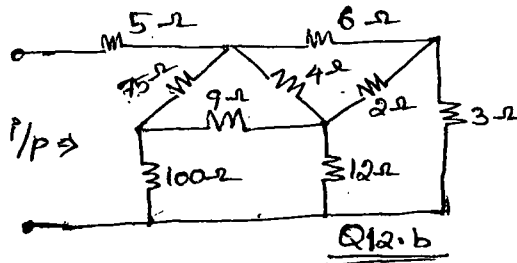- b) (i) Apply Δ -Y and Y- Δ to find the input resistance of the network shown in Q12.b (12)




- (ii) Find the power delivered by a 1V source, connected at the input of the above circuit. (4)

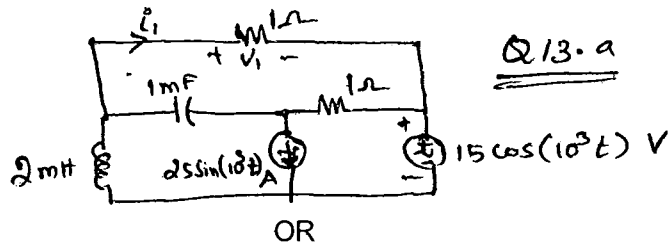- 13.a) Apply steady state analysis and superposition principle in the circuit shown in Q13.a to find $v_1(t)$ due to (i) Voltage source acting alone, (ii) current source acting alone, (iii) both the source are acting together




OR

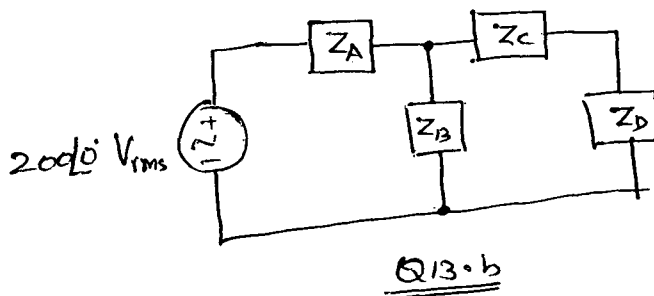- b) Consider the circuit shown in Q13.b and let $Z_A = 5 + j2 \Omega$, $Z_B = 20 - j10 \Omega$, $Z_C = 10 \angle 30^\circ \Omega$ and $Z_D = 10 \angle -60^\circ \Omega$. Find the apparent power and average power delivered to each load and by the source.



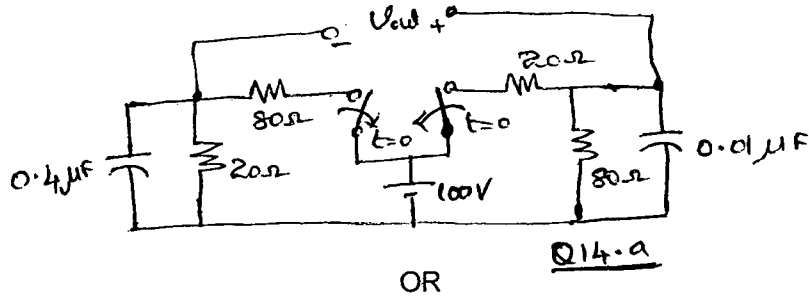14. a) (i) A long time after the circuit Q14.a was assembled, both switches are opened simultaneously at $t=0$ as indicated. (i) obtain the expression for v_{out} for $t>0$ (ii) Obtain the values for v_{out} at time $t=0^+$, $1 \mu s$, $5 \mu s$.




OR

b) (i) Consider a parallel RLC circuit. Derive the formula for resonant frequency and quality factor of the circuit.

(ii) In a parallel RLC circuit, $R=50 \Omega$, $L=2mH$, $C=1\mu F$. Find the resonant frequency and quality factor of the circuit.

15.a) Consider a circuit shown in Q15.a. (i) Write the value of $I_1(\omega)$, $I_2(\omega)$ and $I_3(\omega)$ in terms of ω . (12)

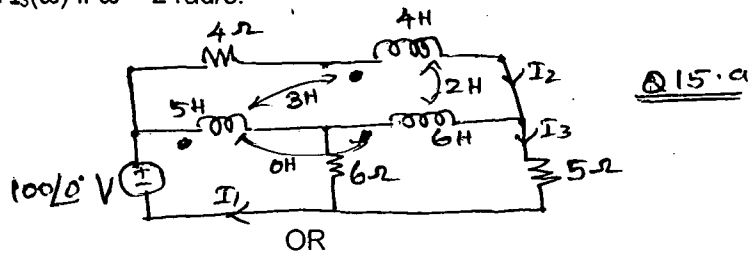(ii) Find the value of $I_3(\omega)$ if $\omega = 2 \text{ rad/s}$. (4)



OR

b) Consider the circuit shown in Q15.b, draw the graph of the network and find the value of V_x and V_y by using the graph.

