



## UNIT – II

- 4) a) Analysis CE amplifier with emitter resistance.  
b) Classify different types of amplifiers.

OR

- 5) a) State and explain Millers theorem and its dual.  
b) Analyze general transistor amplifier circuit using h-parameter model. Derive the Expressions for  $A_i$ ,  $A_v$ ,  $R_i$ ,  $R_o$ ,  $A_{i_s}$ ,  $A_{v_s}$ .

## UNIT – III

- 6) a) Describe the emitter follower at high frequency and also derive that equation for higher cutoff frequency.  
b) Define and explain  $f_\beta$  and  $f_T$ .

OR

- 7) a) Explain the hybrid- $\pi$  model for a transistor in the CE configuration with neat sketch.  
b) Derive the expression for the CE short circuit current gain  $A_i$  with resistive load.

## UNIT – IV

- 8) a) Explain the operation of transformer coupled transistor amplifier?  
b) Compare the three types of coupling used in multi stage amplifiers.

OR

- 9) a) Draw the circuit for Darlington pair and derive the expressions for  $A_v$ ,  $A_i$ ,  $R_i$ , &  $R_o$ .  
b) List the salient features Darlington pair amplifiers.

