



K15F 0174

Reg. No. :

Name :



V Semester B.Tech. Degree (Reg./Sup./Imp. – Including Part Time)
Examination, November 2015
(2006 and Earlier Admn.)

PTEC2K/EC2K 504 : LINEAR INTEGRATED CIRCUITS

Time : 3 Hours

Max. Marks : 100

Instruction : Answer all questions.

PART – A

- I. a) Explain the offset nulling technique used in opamp. 5
- b) Define unity gain bandwidth of an opamp. Also explain the significance of unity gain B.W. 5
- c) List out typical CMOS opamp parameters. 5
- d) Explain the advantage of differential amplifier over single input amplifier. 5
- e) Explain the working of inverting amplifier with proper circuit diagram. 5
- f) Explain the working of 4 quadrant multipliers. 5
- g) Draw the circuit diagram of all pass filter and explain why we need all pass filter. 5
- h) Differentiate : 5
 - 1) Active and passive filters
 - 2) Analog and digital filters.

PART – B

- II. a) Explain and derive the equation for
 - 1) Slew rate
 - 2) CMRR
 - 3) Input offset current. 15

OR

- b) Define input bias current. Derive the equation of output offset voltage due to input bias current. Also explain how to nullify the effect of input bias current. 15



- III. a) Explain the operation of cross coupled pair differential amplifier with neat circuit diagram. Also list out the advantages of cross coupled pair differential amplifier. 15

OR

- b) Explain the working of wide swing constant transconductance differential amplifier with neat circuit diagram. 15

- IV. a) Define oscillator. Explain wein bridge oscillator with neat circuit diagram and derive the equation for f_o (frequency of oscillation) and R_F/R_1 . 15

OR

- b) i) Explain voltage to current converter using proper circuit diagram and equation. 7

- ii) Explain log amplifier with neat circuit diagram and derive the equation for output voltage. 8

- V. a) Derive the equation for transfer function of twin-T notch filter with neat circuit diagram. Also obtain the equation for Q factor. 15

OR

- b) Draw the circuit diagram of a second order Butterworth Sallenkey configuration H.P.F. and derive the equation for transfer function $H(S)$? 15
-