

(DEE 324)

B.Tech DEGREE EXAMINATION, MAY - 2015

(Examination at the end of Third Year)

ELECTRICALS AND ELECTRONICS

Paper - IV : Power Electronics

Time : 3 Hours

Maximum Marks : 75

Answer question No.1 compulsory

(15 × 1 = 15)

Answer ONE question from each unit

(4 × 15 = 60)

- 1) a) Write short notes on TRIAC.
- b) Define freewheeling diode. Explain its significance.
- c) What is natural and forced commutation? Explain.
- d) Draw the voltage and load current waveforms of single phase half wave converter with RLE load at $\alpha = 30^\circ$.
- e) Explain RC half wave firing circuit of SCR.
- f) Discuss briefly about step-up chopper.
- g) What is cyclo converter? What are its applications?
- h) What are the advantages of 120° mode of 3- ϕ inverter.
- i) Explain briefly about CSI.
- j) Explain about digital firing schemes of SCR.
- k) Write short notes on circulating current mode of dual converter.
- l) What is finger voltage? Explain its importance.
- m) Explain about D.C. circuit breakers.

- n) What is pulse width modulation? List the various PWM techniques.
- o) Draw the output voltage and current waveforms of 1- ϕ full controlled converter with RE load at $\alpha = 60^\circ$.

UNIT - I

- 2) a) Explain the theory of operation of SCR.
- b) Explain turn on and turn off methods of SCR.

OR

- 3) Explain various methods of protection of SCR.

UNIT - II

- 4) Describe the working of 1- ϕ full wave converter with R-load. Draw the relevant waveforms. Also derive the expression for R.M.S and average output voltage.

OR

- 5) Describe the working of 3- ϕ half controlled converter for $\alpha = 45^\circ$ with relevant wave forms and derive the expression for average and rms output voltage for R-load.

UNIT - III

- 6) Explain 180° conduction mode of 3- ϕ inverter with relevant waveforms and derive the necessary expressions.

OR

- 7) Describe the operation of parallel Inverter with aid of diagrams. Describe an expression for output frequency, Current and voltages. What are the advantages and disadvantages of parallel inverter?

UNIT - IV

- 8) Discuss the working of a 1- ϕ bridge cycloconverter with R-load for discontinuous waveform operation with neat circuit diagram and output rms voltage and current waveform for $f_o = 3f_s$.

OR

- 9) Describe the principle of step-down chopper. Derive an expression for the average output in terms of input dc voltage and duty cycle.

ΦΦΦ