EC - 605 B.E. VI Semester

Examination, December 2014

VLSI Circuits and Systems

Time: Three Hours Maximum Marks: 70

Note: Attempt only one question from each unit. Each question carry equal marks.

Unit -1

- 1.a) Prove that p MOS pass strong logic' 1' and n-MOS pass strong logic'0'. b) Explain the following:
- i) Regularity ii) Modularity iii) Locality

OR

- 2.a) Explain the implementation of a CMOS positive level sensitive D latch and CMOS positive Edge triggered D Register.
- b) Write an introductory note on Computer Aided Design (CAD) tools.

Unit-II

- 3.a) State the difference between Mealy and Moore machine. Give simple example and draw the state transition diagram for the two.
- b) Explain the following memory elements

i) D flip-flop

ii) T flip-flop

iii) S-R flip-flop

iv) J.K flip-flop

OR

- 4.a) Explain the state minimization of completely specified machine by using tabular method,
- b) Design a circuit which gives o/pz = 1 if x(t) = x(t-2)

Unit-III

- 5.a) Explain secondary state assignment in sequential machines.
- b) Describe in brief critical and non critical races.

OR

- 6.a) Explain hazards in sequential circuits. Explain methods of removal of hazards in sequential circuit design,
- b) A circuit has two inputs x, andx2 and one output z

When $x_1 = 0$ Output $z=x_2$

When $x_{1=1}$

Output remains unchanged

Develop a primitive flow table

Unit - IV

- 7.a) Explain the various blocks of ASM flow charts with the help of a suitable example,
- b) Explain the hardware implementation and algorithm for the addition and subtraction with signed-2's complement data.

OR

- 8.a) What is a controller? Describe the autonomous and nonautonomous controllers with state diagram.
- b) Draw an ASM chart for a comparator and Explain it.

Unit-V

- 9.a) What are faults? Also discuss its types.
- b) What are programmable logic arrays? Implement the following function with PLA F = AB' + AC' + A'B'C

OR

- 10.a) What is FPGA? Describe various types of FPGA with diagram.
- b) Implement a BCD to Excess-3 code converter by using PLA.