



Code No. : 5345/S

(2015M OP)

B. TRAR

FACULTY OF INFORMATICS

B.E. 2/4 (IT) I Semester (Suppl.) Examination, June 2012

MICRO ELECTRONICS

Time : 3 Hours]

[Max. Marks : 75

- Note :** 1) Answer all questions from Part – A.
2) Any five questions from Part – B.

PART – A

(25 Marks)


1. Briefly explain the operation of varactor diode. 3
2. If the voltage across a Ge diode is 0.2 V when the current is 1 mA. Find the reverse saturation current. (Assume $\frac{1}{\eta V_T} = 10$ for Ge). 2
3. Define current amplification factor of BJT in CE configuration. 2
4. Briefly explain different regions of operation of MOSFET. 3
5. Define Loop gain. 2
6. Draw the collector current waveforms of Class – A, Class – B and Class – C amplifiers. 3
7. Derive the expression for voltage gain of the op-amp in the inverting configuration. 3
8. Draw the circuit for analog multiplier using op-amp. 2
9. Draw the voltage transfer characteristic of inverter. 2
10. Briefly explain about CMOS logic. 3



PART – B

(50 Marks)

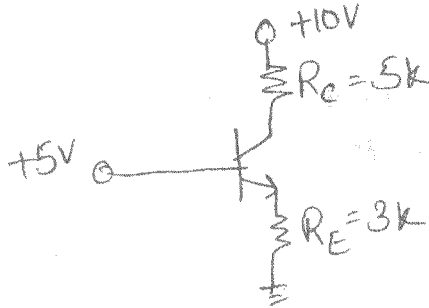- 11. a) Explain the operation of Bridge Rectifier Circuit. 7
- b) Explain about limiting circuits. 3
- 12. a) Explain the physical structure and operation of JFET. 6
- b) Find the node voltages and branch currents in the following circuit. ($\beta = 100$). 4



- 13. a) Explain about the feedback topologies. 5
- b) Explain the operation of class-B amplifiers. 5
- 14. a) Write about the operation of mono-stable multi-vibrator. 6
- b) How an op-amp can be used as VCCS ? 4
- 15. Explain about static and dynamic operation of C-MOS inverter. 10
- 16. a) Discuss about internal capacitances of MOSFET. 4
- b) Write about clamping circuits. 6
- 17. Write short notes on :
 - a) Advantages of negative feedback. 3
 - b) Ideal characteristics of op-amp. 4
 - c) CMOS Implementation of 2-input EX-OR Gate. 3