

THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINATION
DECEMBER 2009

EE 04 305—ELECTRONICS—I

(2004 admissions)

Time : Three Hours

Maximum : 100 Marks

Answer all questions.

Part A

- I. (a) Explain the features of Schottky diode.
(b) Explain the characteristics of JFET.
(c) What is meant by piecewise linear model of a diode.
(d) Explain the working of positive and negative clamper.
(e) Mention the *three* sources of instability of collector current. Define *three* stability factors.
(f) What is cross over distortion and how it can be minimized ?
(g) Explain the selection of bypass capacitor in transistor amplifier.
(h) Distinguish between difference input signal and common mode input signal.

(8 × 5 = 40 marks)

Part B

- II. (a) Explain the charge density in extrinsic semi-conductor. (8 marks)
(b) Explain the electrical characteristics of silicon and germanium. (7 marks)
- Or*
- (c) Explain the characteristics of CE-BJT. (9 marks)
(d) Compare E-MOSFET and D-MOSFET. (6 marks)
- III. (a) Explain with relevant diagrams, the operation of full-wave rectifier. Derive the expression for (i) d.c. current ; (ii) d.c. load voltage ; (iii) a.c. r.m.s. current.

(10 marks)

- (b) What are the merits and demerits of full-wave rectifier. (5 marks)

Or

- (c) Explain the operation of different types of clipper circuits. What are its practical applications ? (15 marks)

- IV. (a) Draw the *h*-parameter equivalent circuit of CE amplifier and derive the expressions for current gain, input resistance, voltage gain and output admittance.

(15 marks)

*Or***Turn over**

- (b) What is a push-pull amplifier ? List out its advantages. (5 marks)
- (c) Draw the circuit of a class B, BJT push-pull amplifier and derive the expression for its collector efficiency. (10 marks)
- V. (a) Explain the frequency response characteristics of an amplifier. (7 marks)
- (b) What is the effect of cascading on gain, frequency response and bandwidth ? (8 marks)
- Or*
- (c) State and explain Miller effect. (7 marks)
- (d) Explain the concept of current source biasing. (8 marks)
- [4 × 15 = 60 marks]