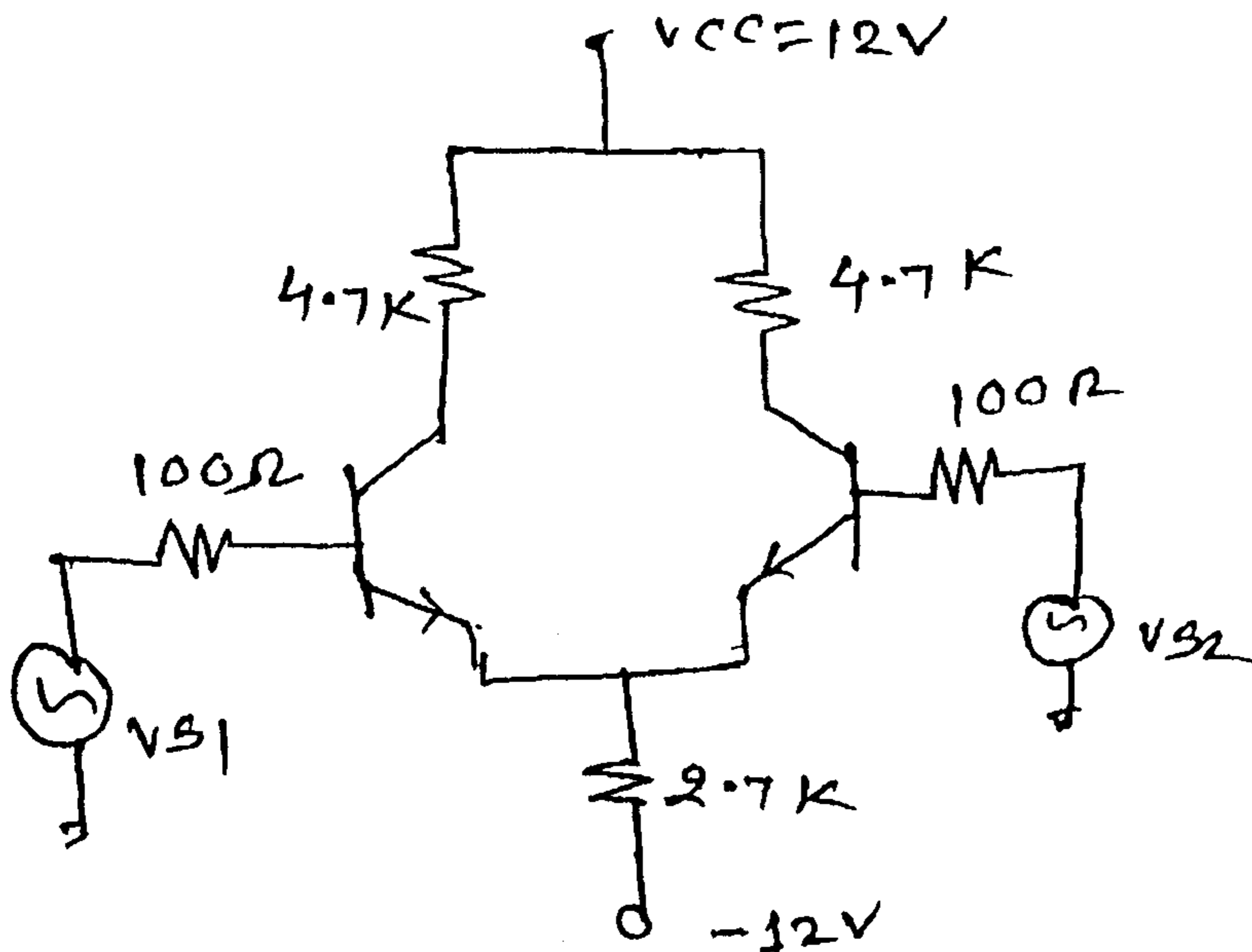


- N.B. :** (1) Question No. 1 is **compulsory**.
 (2) Attempt any **four** questions from remaining **six** questions.
 (3) Draw **neat** labelled diagrams wherever **necessary**.
 (4) Assume **suitable** data if **necessary**.

1. (a) Explain block diagram of op-amp 5
- (b) Explain zero crossing detector 5
- (c) Explain significance of CMRR for a differential amplifier 5
- (d) Explain the basic principle of D to A converter. 5

2. (a) Explain internal block diagram of astable multivibrator using IC 555 and explain the one application of it. 10
- (b) For the differential amplifier find A_d , A_c , CMRR, R_{in} and R_o . 10



$$\beta = \beta_{dc} = \beta_{ac} = 100$$

$$h_{ie} = 1k \Omega$$

42
GS-6243

3. (a) Draw the transfer characteristics of an n-channel JFET with the help of Shockley's expression and explain its significance. 10
- (b) Design a wide bandpass filter for $F_L = 1KHz$ and passband gain equal to 4. Also find quality factor. 10

4. (a) Draw the block diagram of an oscillator and explain the Barkhausen conditions to obtain sustained oscillations. 10
- (b) Design a stable multivibrator using 555 for duty cycle 75% and output frequency 5 KHz. 10

[TURN OVER

Con. 6463-GS-6243-13.**2**

5. (a) Explain the basic requirement for the instrumentation amplifier. Find the expression for output voltage using three op-amp. **10**
- (b) Explain the non-inverting Schmitt trigger and give the Schmitt trigger advantages over the conventional comparators. **10**
6. (a) Design a voltage regulator using I_C 723, $V_O = 5V$, $I_O = 50$ mA, $I_{sc} = 75$ mA, $v_{in} = 15V$. **10**
- (b) Design a R-C phase shift oscillator for output frequency 1 KHz. **10**
7. (a) Explain the averaging amplifier. **5**
- (b) Explain three terminal voltage regulator **5**
- (c) Explain dual slope ADC and state its advantages **5**
- (d) Explain 555 as a voltage controlled oscillator. **5**
-