

OR

Explain Sawtooth generator with the help of circuit diagram using GTO. Also give the wave-forms of the generator. What is the utility of the above in the industrial field.

OR

A three-phase, three-wire fullwave phase control supply of 230 V rms. Calculate the rms output voltage for $\alpha = \frac{\pi}{3}$.

Unit-V

- Explain the working of a triac switch for control low voltage.
 - Draw the circuit of light divider using Diac and Triac.
 - Discuss any industrial application using GTO.
- Write short note on any two of the following:
- Welding cycle
 - Battery charger
 - Induction heating
 - Speed control of dc motor

Unit-II

Roll No

EI-504

B.E. V Semester

Examination, December 2015

Power Electronics

Time : Three Hours

Maximum Marks : 70

- Note:** i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.
- ii) All parts of each questions are to be attempted at one place.
- iii) All questions carry equal marks, out of which part A and B (Max.50 words) carry 2 marks, part C (Max.100 words) carry 3 marks, part D (Max.400 words) carry 7 marks.
- iv) Except numericals, Derivation, Design and Drawing etc.

Unit-I

- Give the complete classification of power semiconductor devices in terms of layers with examples.
 - Draw the cross-sectional view and V-I characteristics of a Power diode.
 - Draw and explain the turn-off characteristics of a thyristor.
 - Discuss the transistor model of an IGBT with appropriate diagram. Also explain its V-I characteristics.

OR

Discuss the working of Triac in all modes of operations.

Unit-II

- What are the limitations of uncontrolled rectifier? How can they be overcome?
- Why is a flywheel diode used in controlled rectifiers?
- Explain the effect of source inductances in the full-wave controlled rectifier with the help of appropriate waveforms.
- Explain the working of a single-phase half-controlled bridge configuration for resistive-inductive load. Derive the expressions for average dc value and rms value.

OR

A three-phase half-wave controlled rectifier is connected to a 230 V ac input with a 100 Ω load resistance. If the desired average output voltage is 50% of the maximum possible average output voltage, calculate the delay angle α .

Unit-III

- Discuss the merits and demerits of transistor and thyristor inverters.
- What do you mean by a switch-mode regulator?
- How is a full-bridge regulator derived from a buck regulator?
- What do you mean by power? Explain the working of a multiple-pulse-width modulation.

OR

A buck regulator has an input of 110 V, the average load voltage is 60 V with an average load current of 30 A. The switching frequency is 25 kHz. The peak-to-peak ripple current is 1.2 A. Calculate the value of the inductor.

Unit-IV

- What is an ac voltage controller? Give its industrial applications.
 - Explain why cycloconverters are more efficient than the dc link converter.
 - Why is the common cathode configuration normally used as compared to other circuit configurations? Explain.
 - Discuss a three-phase to single-phase cycloconverter.

OR

A three-phase, three-wire full-wave phase controller with a star-connected resistive load of $R = 30 \Omega$, is fed from a supply of 230 V rms. Calculate the rms output phase voltage for $\alpha = \pi/3$.

Unit-V

- Explain the working of a triac switch for controlling the low voltage.
 - Draw the circuit of a light divider using Diac and Triac.
 - Discuss any industrial application using GTO.
 - Write short notes on any two of the following:
 - Welding cycle
 - Battery charger
 - Induction heating
 - Speed control of dc motor.