


Con. 3046-11.

(3 Hours)

[Total Marks : 100]

- N.B. :** (1) Question No. 1 is **compulsory**.
 (2) Attempt any **four** questions out of the remaining **six** questions.
 (3) Assume **suitable** data if **necessary**.

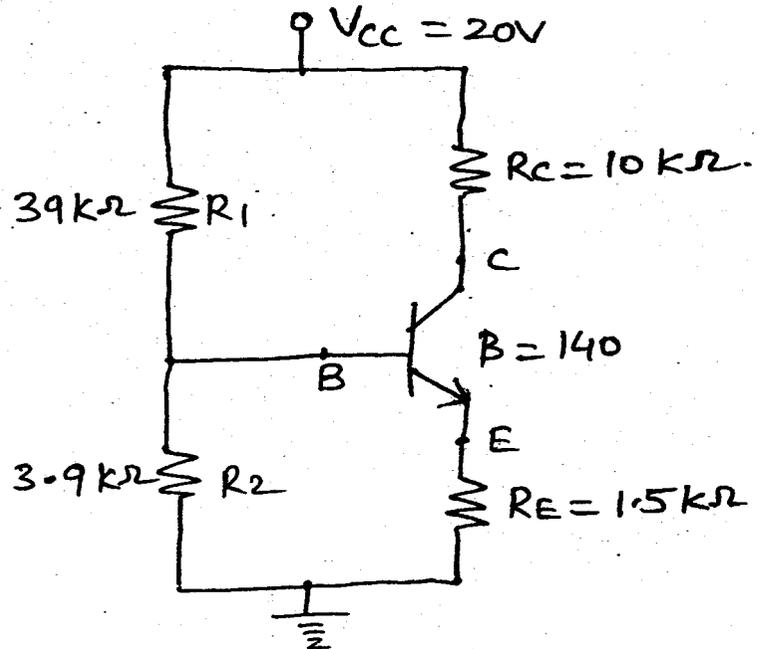1. (a) List the characteristic features of 555 timer. 20
 (b) Explain operational amplifier with a neat block diagram.
 (c) With a neat circuit diagram explain voltage follower and draw input-output waveforms.
 (d) Explain series voltage regulator.
2. (a) Draw small-signal n-parameter model of the BJT and define the terms h_{ie} , h_{re} , h_{fe} and h_{oe} for the same. 8
 (b) Determine the following for the circuit shown in figure below :- 12
 (i) I_{BQ} (ii) I_{CQ} (iii) V_{CEQ} (iv) V_{CQ} (v) V_{EQ} (vi) V_{BQ} .
 Use both, Exact and approximate analysis to solve the same.




3. (a) Derive equations for Z_i , Z_o , A_v for common source configuration using voltage divider network (with unbypassed R_s). 10
 (b) Explain Instrumentation Amplifier using IC 741. Derive the expression for V_o . 10

[TURN OVER

Con. 3046-RK-1263-11.

2

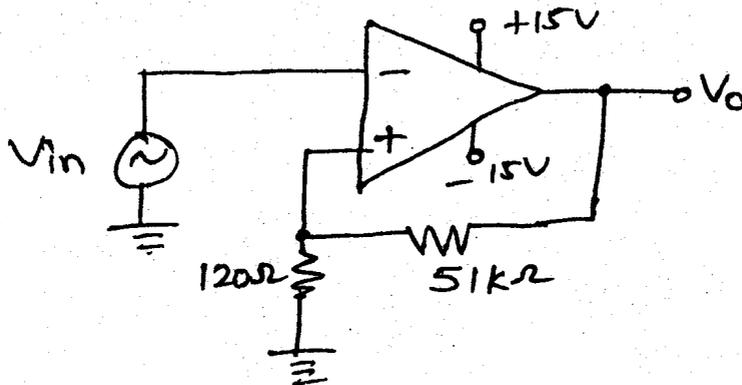4. (a) Explain in detail any two applications of a monostable multivibrator. 10
 (b) Explain the digital ramp ADC with a neat block diagram. 10
5. (a) Design a regulator using IC 723 to meet the following specifications :- 10
 $V_o = 5V$; $I_o = 100 \text{ mA}$
 $V_{in} = 15 \pm 20\%$
 $I_{sc} = 150 \text{ mA}$
 $V_{sense} = 0.7V$
- (b) Explain successive Approximation Resistor A/D converter. 10
6. (a) For a Schmitt trigger shown in the figure, calculate threshold voltage levels 10
 and hysteresis. Assume $V_{sat} = 0.9 V_{cc}$.



- (b) Explain op-amp as an Practical Integrator. 10
7. Write short notes on any two :- 20
 (a) PLL
 (b) Inverting Schmitt trigger
 (c) Zero Crossing Detector
 (d) D/A converter using R-2R resistors.