

(3 Hours)


[Total Marks : 100

- N.B.: (1) Question No. 1 is **compulsory** and solve any **four** questions out of remaining **six**.
 (2) Assume suitable **data** if **necessary** and mention that **assumption** while solving that questions.
 (3) **Figures** to the **right** indicate **full marks**.


1. Any five :—

20

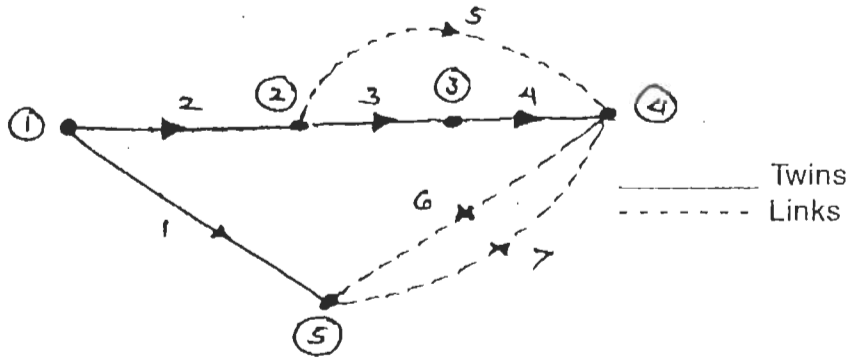
- (a) Following is a tree of graph (shown with firm lines) shown in linear graph of a network obtain fundamental cutset matrix.



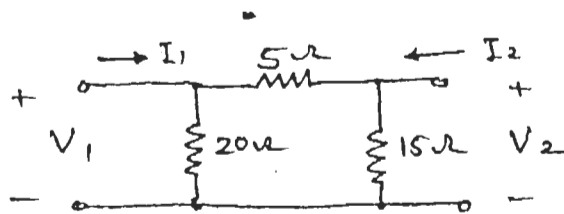- (b) What are the conditions for a rational function $F(s)$ with real coefficients to be "positive real function ?"
 (c) Find the Z-parameters for the circuit shown.



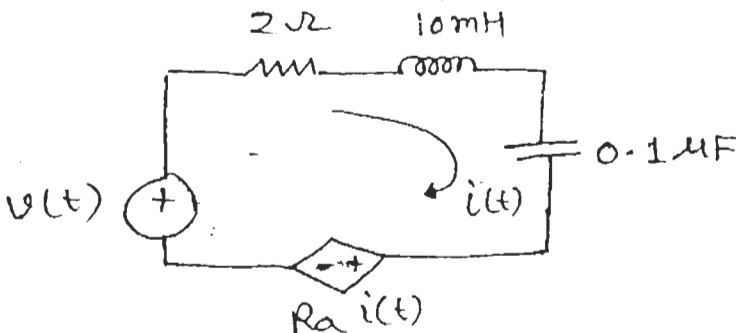- (d) Draw the dual network of the following circuit and prove that it is a dual one.




[TURN OVER

Con. 4773-GN-9320-12.


2

(e) For the network shown find :—

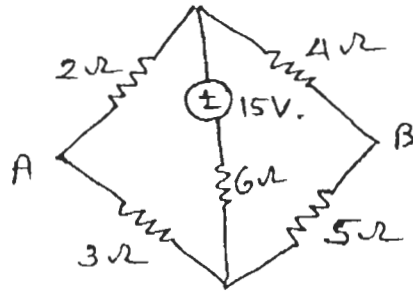- (i) Power from voltage source
- (ii) Voltage across A-B.




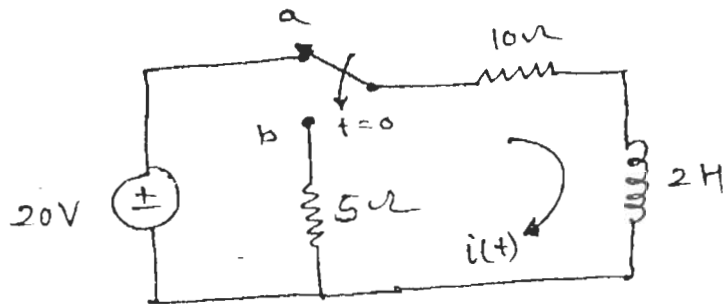(f) The circuit is operating under steady state condition when switch is at position 'a' of at $t = 0$, the switch is moved to position 'b'. Determine current $i(s)$ and $i(t)$.




2. (a) Find V_a , V_b and V_c using Nodal Analysis.

10

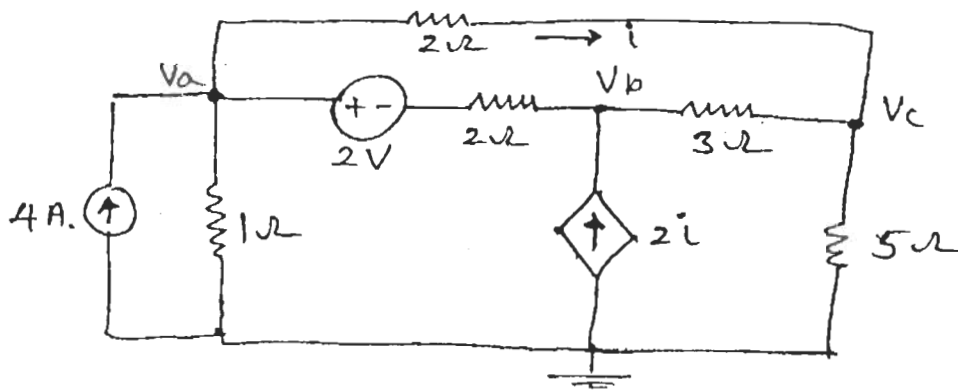

(b) Find the Norton's equivalent circuit across terminals a-b of given circuit and hence the power dissipated in 10Ω resistor.

10

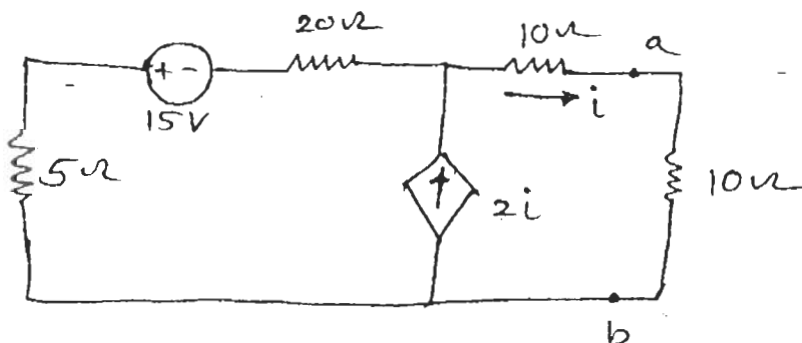

3. (a) State giving appropriate reasons whether the following functions are "positive real functions." 10

$$(i) F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$$

$$(ii) Y_2(s) = \frac{s^3 + 5s}{s^4 + 2s^2 + 1}$$


- (b) Realise :—

10


$$(i) Y(s) = \frac{s^4 + 6s^2 + 4}{2s^3 + 4s} \text{ in Cauer II form.}$$

$$(ii) Z(s) = \frac{4(s^2 + 1)(s^2 + 16)}{s(s^2 + 4)} \text{ in Foster I form.}$$

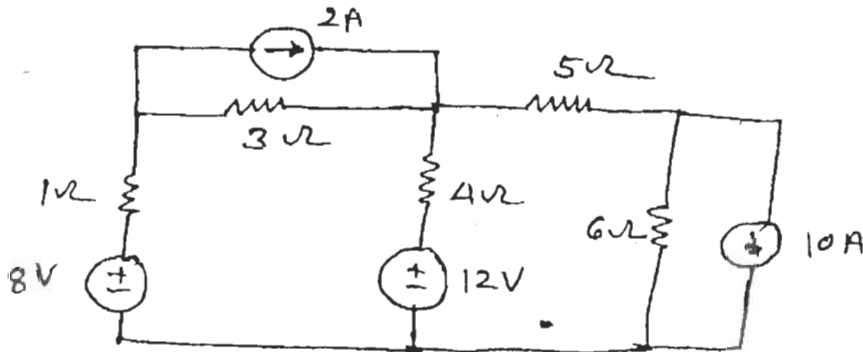4. (a) For the network shown find branch currents and branch voltages using loop current analysis. This is to be solved by graph theory. 10




- (b) Graph of a given network is to be drawn. Also find A_a , A , B and Q matrices for the same. How many trees are possible in the above graph? 10

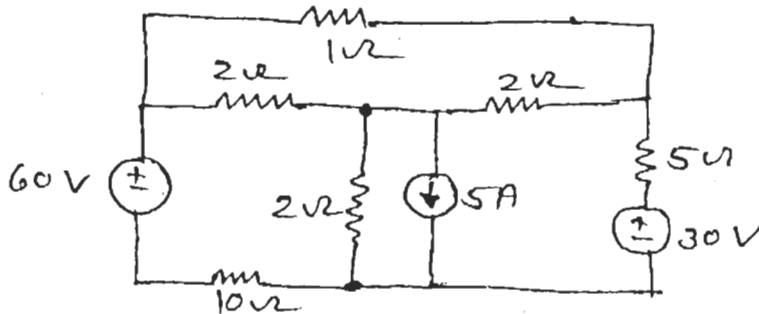



Con. 4773-GN-9320-12.

4

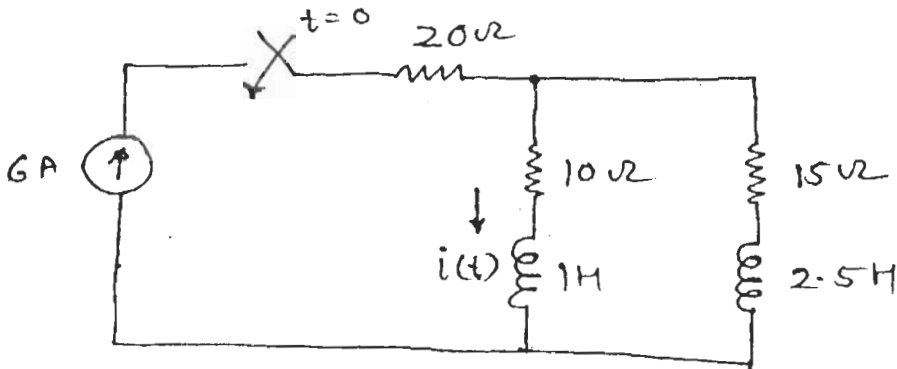
5. (a) Using Laplace transform find $i(t)$ if the switch is closed at $t = 0$. Assume initial conditions to be zero. 10



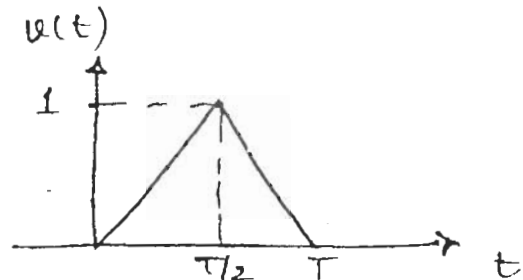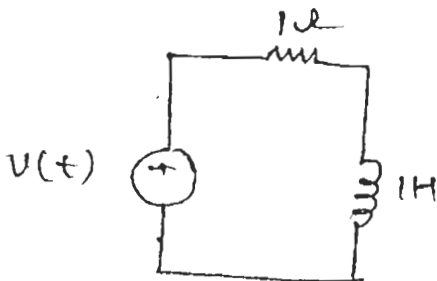- (b) A triangular voltage pulse of duration T and peak value unity is switched in to a series RL circuit which is initially relaxed. Determine $i(t)$. 10



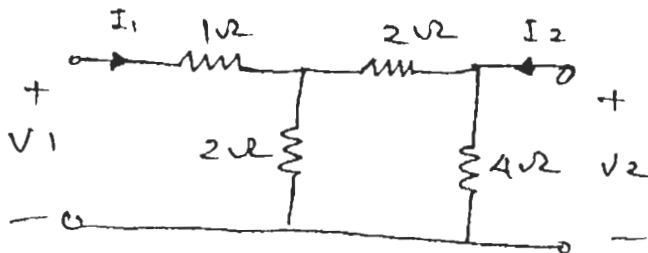6. (a) Two identical sections of this network are in parallel. Obtain Y-parameters for connected network. 10



- (b) Define ABCD parameters and relate them to other parameters as indicated. 10
- A and C in terms of Z
 - B in terms of Y
 - D in terms of H.

Con. 4773-GN-9320-12.

5

7. (a) A series R-L circuit with $R = 10\Omega$ and $L = 1\text{H}$ is applied with constant 20V voltage 10 at $t = 0$. Find the time at which $V_R = V_L$.
- (b) Find i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$ in the following network when the switch is changed 10 from position 1 to 2 at $t = 0$. Steady state condition reached before switching.

